Energy conversion I

Lecture 25:

Topic 6: DC Machines (S. Chapman ch. 8 &9)

- A Simple Rotating Loop between Curved Pole Faces
- Commutation Problems in Real Machine
- The Construction of DC Machine
- The Internal Voltage and Torque Equations of Real DC Machine
- The Equivalent Circuit of a DC Motor
- Power Flow and Losses in DC Machines
- Separately Excited, Shunt, Permanent-Magnet and Series DC Motors
- DC Motor Starter
- Introduction to DC Generators

DC Generators

- Rotating rotor series / parallel conductors
- Flux under poles due to stator winding /Permanent magnets
- Induced voltage in the rotor terminals (through brushes)

$$E_a = K \phi \omega$$


Connecting load to motor terminals leads to armature current

$$T_a = K \phi I_a$$

- Torque balance leads to steady state speed
- Power balance leads to steady state operation

Usually AC generator plus rectifier is used instead of DC generator

Different DC Generators

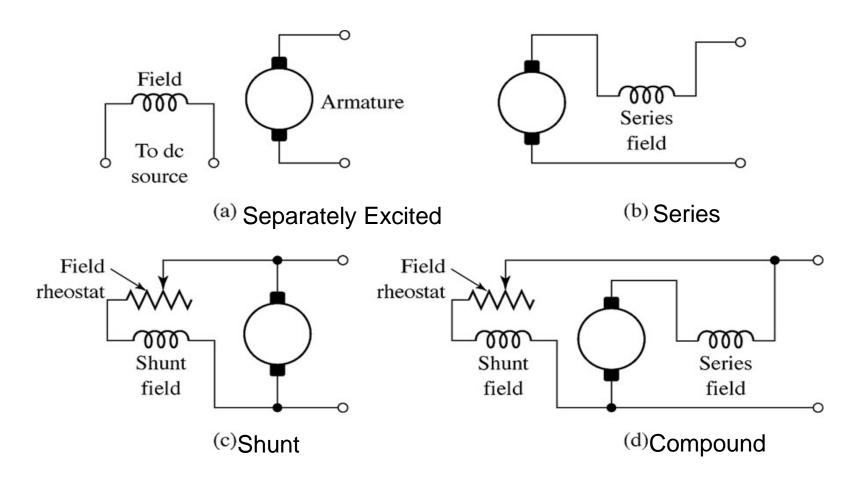

Very similar to DC motors

Separately excited

PM, Shunt, Series, Compound (self excited generators)

3

Voltage Regulation

Voltage drop due to load current:

Armature equivalent resistance (R_a)

Armature reaction

$$VR = \frac{V_{nl} - V_{f1}}{V_{f1}} \times 100\%$$

VR > 0

VR < 0

drooping characteristics

rising characteristics

How rising characteristic can be achieved!

Separately Excited DC Generator

Using modified Armature current

 $V_t \times I_a$: Power delivered to the load

T_A: Induced torque (against prime mover)

 $E_a \times I_a$: Converted power (mechanical to

Electrical)

$$V_t = E_a - R_a I_a$$


E_a: No load Voltage

R_a: slop of voltage drop

How armature reaction affects terminal

characteristics?

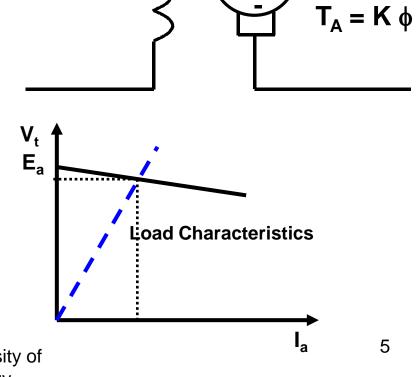EE Course No: 25741 Energy Conversion I Sharif University of Technology



 V_t

Voltage control of Separately Excited DC Generator


$$V_t = E_a - R_a I_a$$

Most effective way to control V_t is through E_a

$$E_a = k \phi \omega$$

φ can be decreased from its rated value decreasing I_f

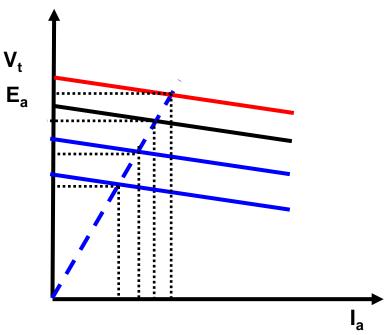 ω can be modified by speed of prime-mover



Armature Reaction

2: Flux weakening

- Armature reaction decrease flux intensity in some parts of the magnetic poles.
- Armature reaction increases flux intensity in some parts of the magnetic poles.
- In linear systems the changes compensate each other.
- In saturated machines the increase is less than increase in flux.




Reduced equivalent pole flux φ




Reduced induced voltage & higher speed motor

Energy Conversion I

Snarir University of Technology

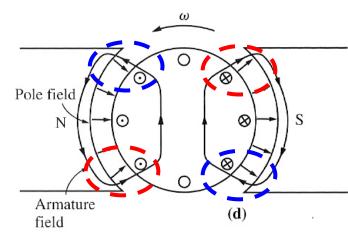

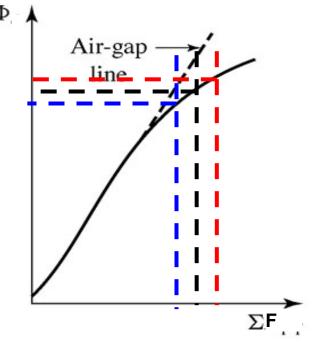

(a)

Armature Reaction Modeling

Armature reaction reduces ϕ

Can be modeled as a reduction in
$$\phi$$
 \longrightarrow E_a

Can be modeled as a reduction in
$$I_f \longrightarrow \emptyset \longrightarrow E_a$$

$$F_{net} = N_F I_F - F_{AR}$$
open circuit
$$I_F^* = I_F - F_{AR} / N_F \qquad \qquad E_a$$

The same approach can be used for DC motors!!

Example

A Separately excited DC generator is rated at 172 kW, 400 A, 1800 RPM with a given magnetizing characteristics.

$$R_a=0.05~\Omega,~R_F=20~\Omega,~V_F=430~V,~N_F=1000~turns/pole,~R_{adj}=0~to~300~\Omega$$
 for $R_{adj}=63~\Omega$ and n = 1600 RPM

A: what is the no-load voltage?

B: What is the generator voltage if $I_a = 360 \text{ A}$ (neglecting AR)

C: Repeat B if AR equivalent MMf@360 A is 450 Aturns.

D: What adjustment could lead to have the no-load voltage while

loaded

Solution:

A:

$$I_F = V_F / R_F = 430 / (63 + 20) = 5.2 A$$

From magnetizing characteristics E_a (@1800RPM) = 430 V

$$E_a = 430 *1600 /1800 = 382 V$$

B:

$$V_T = E_a - R_a I_a = 382 - 360 \times 0.05 = 364 V$$

C:

AR is modeling using its equivalent MMF:

$$I_F^* = I_F - F_{AR} / N_F = 5.2 - 450/1000 = 4.75 A$$

From Mag Ch.: for $I_F = 4.75$ Ea(@1800RPM) = 410 V

And therefore : Ea = $1600 / 1800 \times 410 = 364 \text{ V}$

$$Vt = 364 - 360 \times 0.05 = 346 V$$

D:

The voltage drop can be compensated by increasing Ea

$$E_{a,reg} = 382 + 360 \times 0.05 = 400 \text{ V}$$

The voltage can be calculated @ 1800 RPM:

$$E_{a,reg,1800rpm} = 400 \times 1800 / 1600 = 450 V$$

From Mag Ch. : $I_F = 6.5 \text{ A (neglecting AR)}$

This can be achieved reducing R_{adj} to 50 Ω

Printed Circuit Board DC Motors

Disk shape, nonmagnetic rotor printed in copper armature winding



Low rotor inertia, Small armature inductance

Axial flux by PM Radial current




Induced torque

Small Elect and mech Time constant



Quick motion response

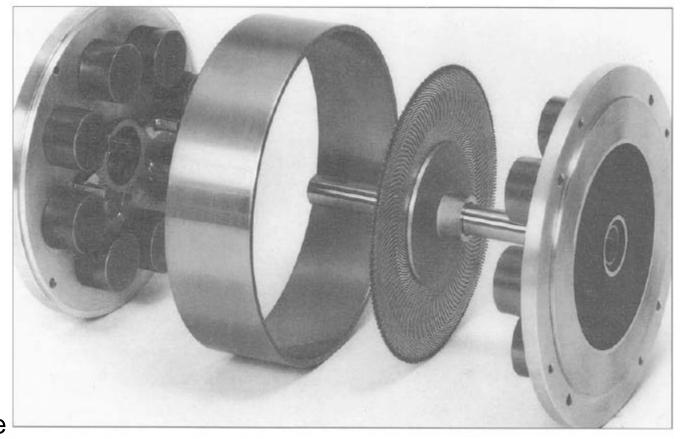


Sharif University of Technology

Printed Circuit Board DC Motors

Technology



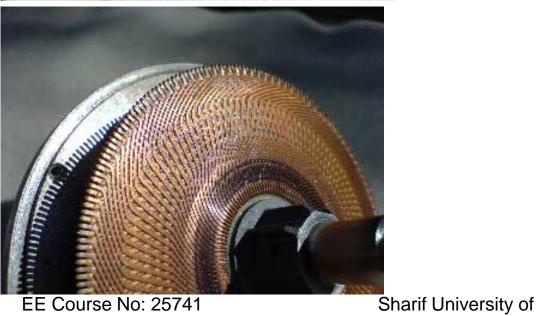







Brushless DC Motors (BLDC)

Technology

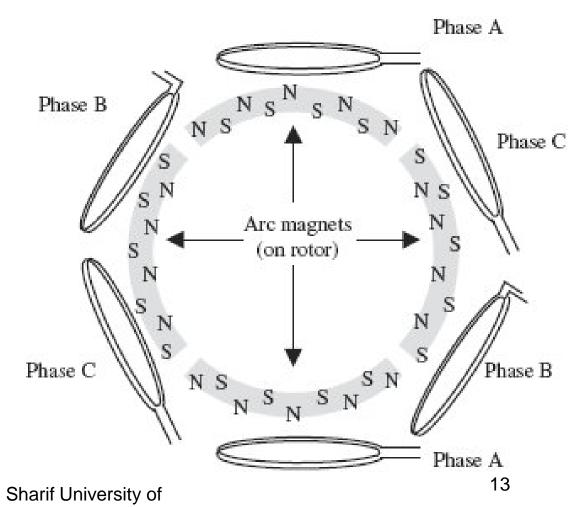- Inside out PM DC motor (rotating PM, fixed armature winding)
- Concentrated three phase winding
- Fixed armature winding
- Rotating PMs induced AC voltage in armature winding
- Electronic converter to rectify induced voltage and commutate current in the stator winding




Brushless DC Motors (BLDC)

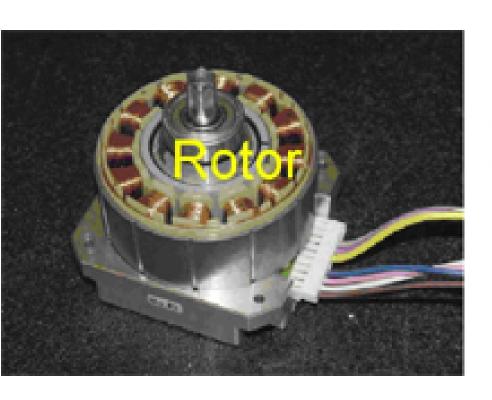



Induced voltages in BLDC Motors

2E

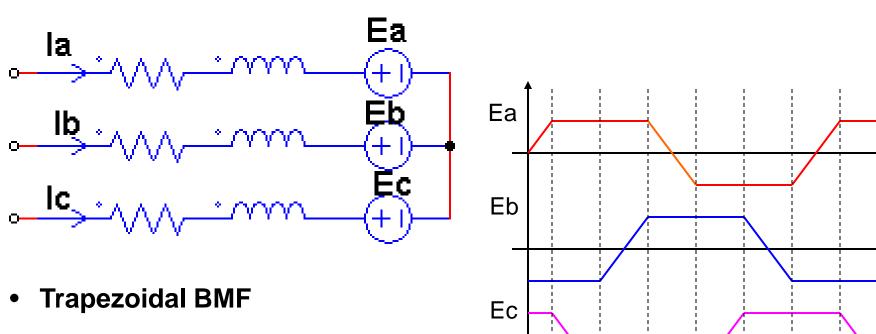


•
$$E = K\phi \times \omega = K_b \times \omega$$

•
$$T=(E_a \times I_a + E_b \times I_b + E_c \times I_c) / \omega$$

How torque can be constant?

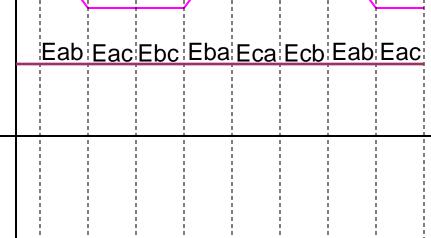EE Course No: 25741 Sharif University of Energy Conversion I Technology




Torque in BLDC Motors

$$T=(E_a\times I_a + E_b\times I_b + E_c\times I_c)/\omega$$

Induced voltage is a function of rotor position

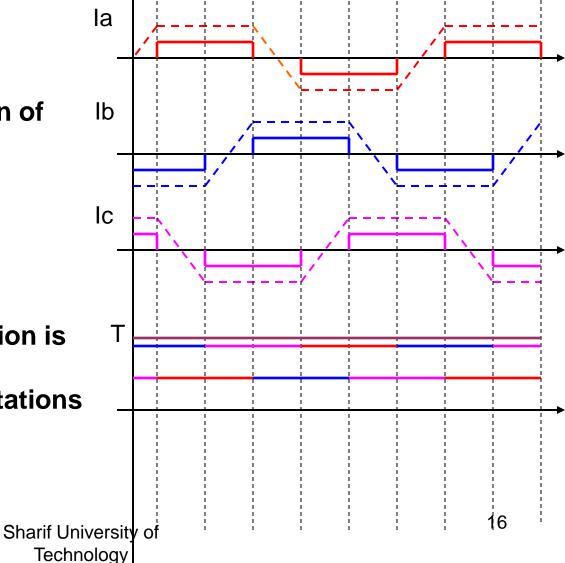- Rotor position is required
- Armature current commutation is required
- Voltage and current commutations are synchronous



BLDC Motor Drive

