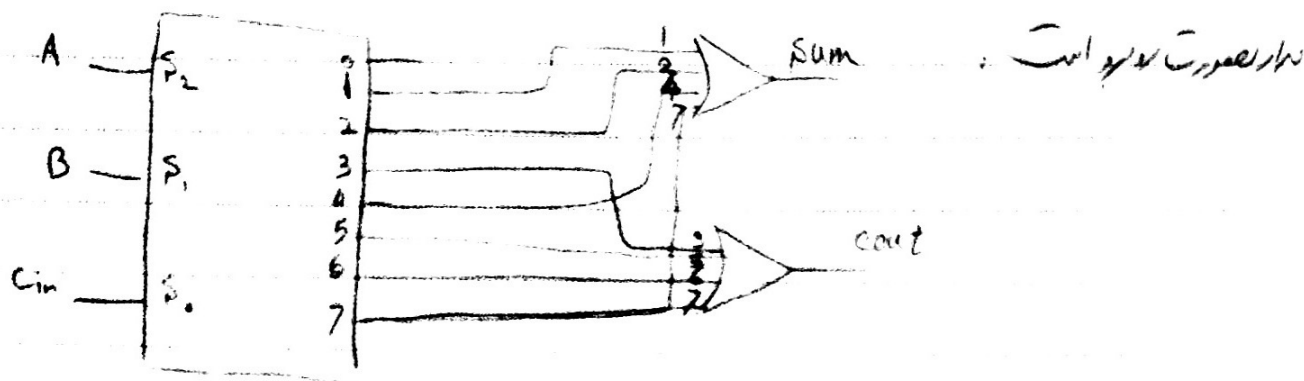


Subject:

Year: Month: Date: ( )


۹۲۱۰۲۸۵۶۷

۱- یک دیکد ۳ به ۸ ولت های منفرد یک full adder طراحی کنید.




۲- تابع  $f(x_1, x_2, x_3, x_4) = \sum(2, 3, 6, 9, 10, 13, 15) + d(0, 12, 14)$  را با یک mux

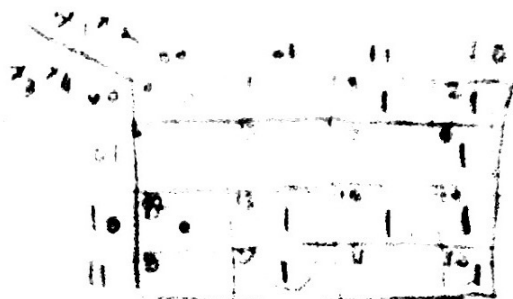۴ به ۱ و درخت تصمیمات به صورت طراحی کنید.


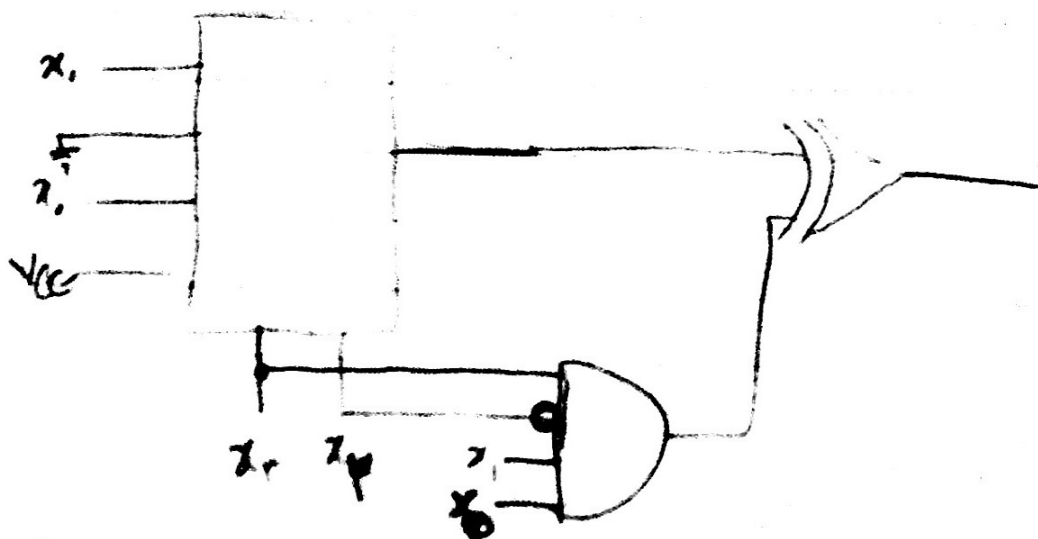
$$f = x_1 \bar{x}_2 + x_2 x_3 \bar{x}_4 + x_1 \bar{x}_3 \bar{x}_4 + x_1 x_2 x_3$$






3 decoder و 8 ویت های

3- تابع  $f(x_1, x_2, x_3) = \sum(0, 1, 3, 4, 6, 7)$


| ab | 00 | 01 | 10 | 11 |
|----|----|----|----|----|
| c  | 0  | 1  | 1  | 0  |
| 1  | 1  | 0  | 1  | 1  |



نتیجه طراحی کتبی
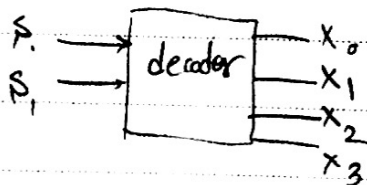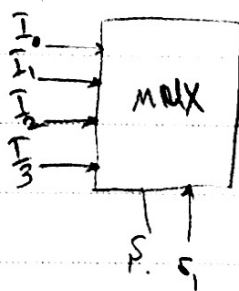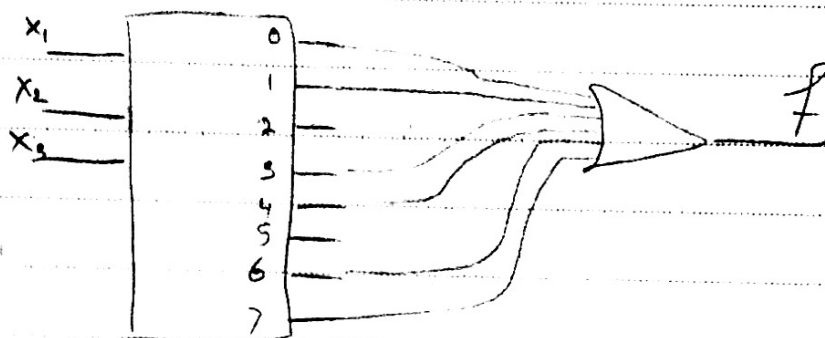
$$f = \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{b}\bar{c} + ac$$


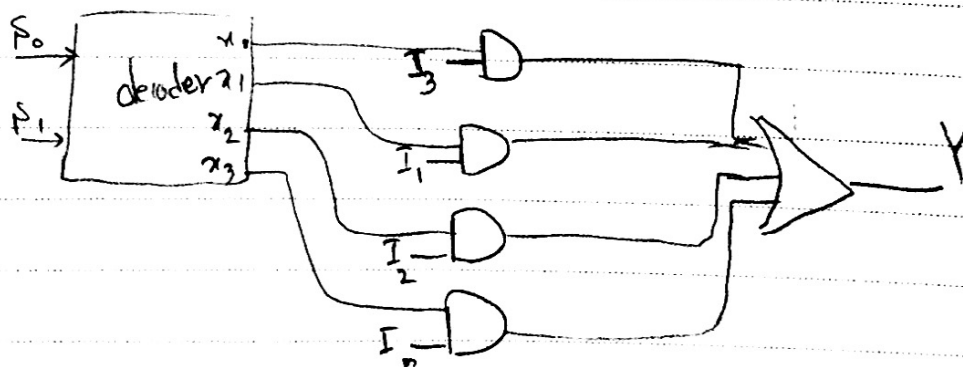
$$f = x_0 I_0 + x_1 I_1 + x_2 I_2 + x_3 I_3$$



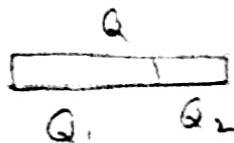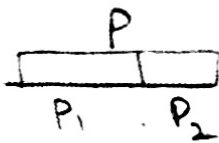

- a


$$P_1 > Q_1 \quad P_1 = Q_1 \quad P_2 > Q_2 \quad P_2 = Q_2 \quad P > Q \quad P = Q \quad P < Q$$

|   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |


$$P < Q = (\overline{P < Q}) (\overline{P = Q})$$

$$P = Q = (P_1 = Q_1) (P_2 = Q_2)$$

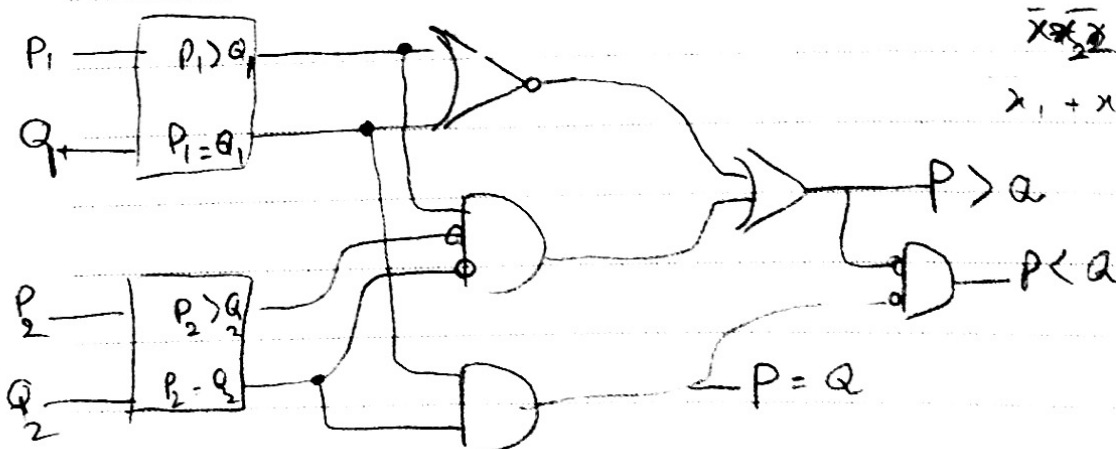
$$P > Q = (\overline{P_1 > Q_1}) (\overline{P_1 = Q_1}) + (P_1 = Q_1) (\overline{P_2 > Q_2}) (\overline{P_2 = Q_2})$$



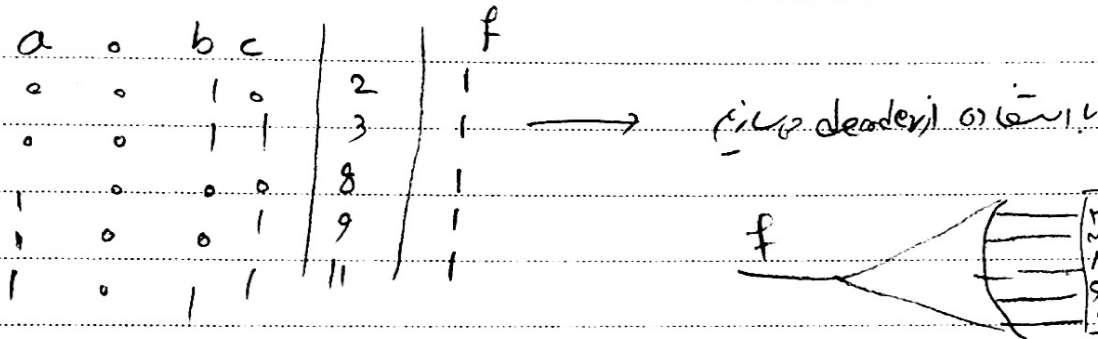6) 1) a)  $f(a, b, c) = \sum m(2, 3, 8, 9, 11)$



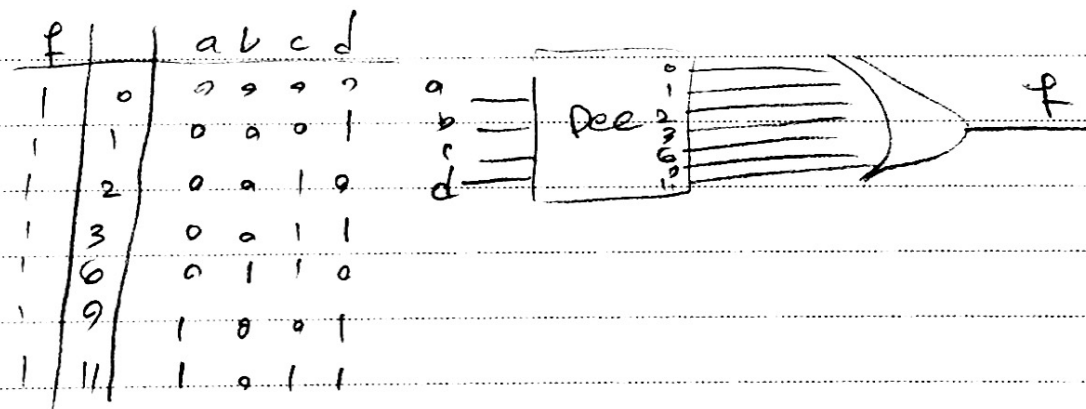2) a)  $f(a, b, c, d) = \sum m(0, 1, 2, 3, 6, 9, 11)$




1) b)  $f = \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + a\bar{b}\bar{c} + a\bar{b}c + abc = ab\bar{c} + a\bar{b} + \bar{a}b$

→ Implementation using OR, NOT, AND gates

2) b)  $f = \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}d + \bar{a}b\bar{c}d + \bar{a}b\bar{c}d$

$= \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}d = \bar{a}\bar{b} + \bar{a}b\bar{c}d + \bar{a}b\bar{c}d$

1) c)

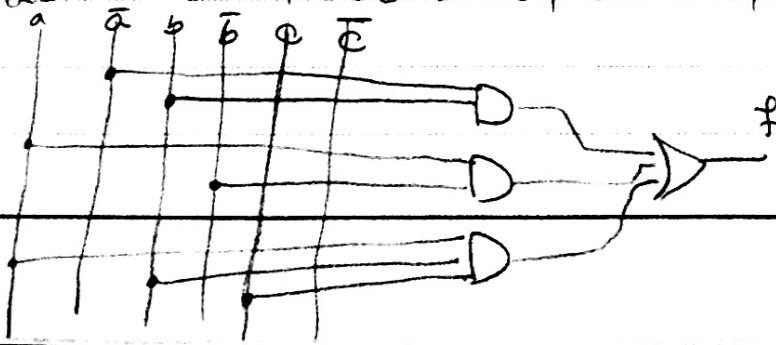

Subject:

Year. Month. Date. ( )

2) c)

