

Homework 5

Common Base

- 1- Derive T-Model from hybrid- π model for common base stage.

Darlington Pair:

- 2- Determine the dc collector currents in Q_1 and Q_2 , and then the input resistance and voltage gain for the Darlington emitter follower of Fig. 1. Neglect r_o . Assume that $V_{BE(on)} = 0.7V$. Check your answer with SPICE and also use SPICE to determine the output resistance of the stage.

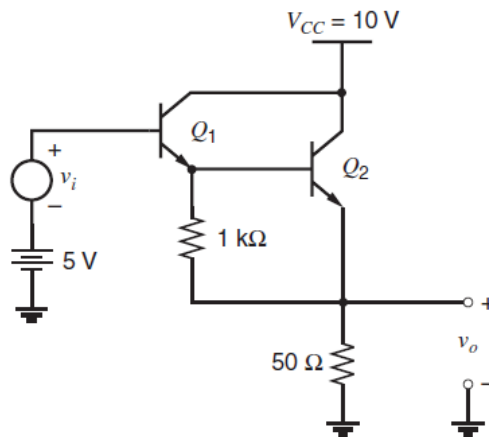


Figure 1. Circuit for Problem 1

- 3- Calculate the output resistance r_{co} of the common-emitter Darlington transistor of Fig. 2 as a function of I_{BIAS} . Do not neglect either r_{o1} or r_{o2} in this calculation. If $I_{C2} = 1mA$, what is r_{co} for $I_{BIAS} = 1mA$? For $I_{BIAS} = 0$?


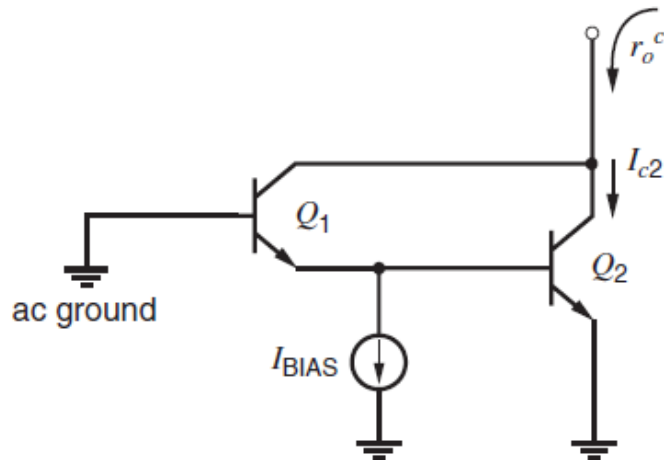


Figure 2. Circuit for Problem 2

Homework 5

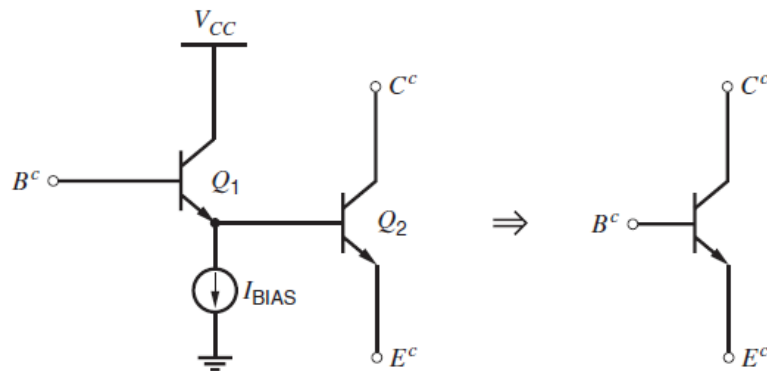- 4- Find the parameters of an equivalent transistor, known as composite transistor for CC-CE or CC-CC connections



Hint: study Section 3.4 of Gray Book, 5th Edition.

- 5- Due to a manufacturing error, a parasitic resistor has appeared in the following cascode circuits. Determine the output resistance in each case.

