

Subject :


Year :

Month :

Date :


Diff input res

Common Emitter

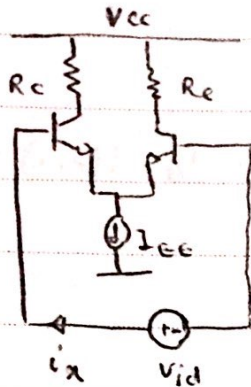

$$R_{in} = \frac{V_{id}}{i_x}$$

Small Signal

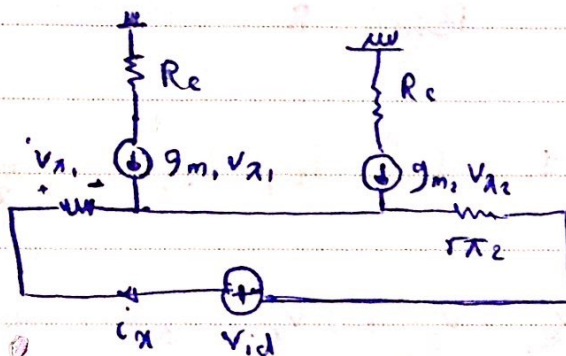


$$-v_{\pi 2} + r_{\pi 1} i_x + r_{\pi 2} i_x = 0 \Rightarrow \frac{v_{\pi 2}}{i_x} = r_{\pi 1} + r_{\pi 2} = 2r_{\pi}$$

match

output Diff res


Common Emitter

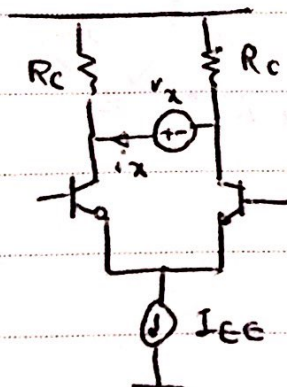

Small Signal

$$R_{out} = \frac{v_{\pi}}{i_x} \Big|_{v_{in} = 0}$$


\Rightarrow

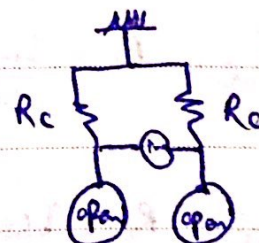

$$\Rightarrow R_{out} = 2R_{EE}$$

R_{in} : Common Mode


Input Port :

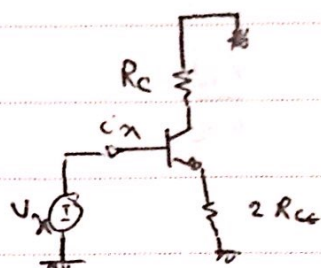

$$\Rightarrow R_{in} = r_{\pi} + (\beta + 1) \times 2R_{EE}$$

Com Code diff pair

Bias :

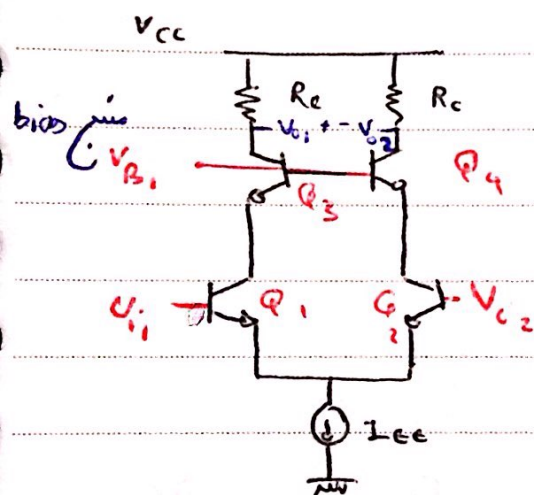

$$I_{C1} = I_{C2} = I_{C3} = I_{C4} = \frac{I_{EE}}{2}$$

$$V_{E1} = V_{E2} = -V_{BE(ON)} = -0.7$$

$$V_{B3} = V_{B4} = V_{B1} \rightarrow \text{Bias}$$

$$\Rightarrow V_{E3} = V_{E4} = V_{B1} - 0.7 = V_{C1} = V_{C2}$$

$$\Rightarrow V_{C1} = V_{C2} = V_{B1} - V_{BE(ON)} + V_{BE(ON)} = V_{B1}$$

$$V_{C3} = V_{C4} = V_{CC} - R_c \times \frac{I_{EE}}{2}$$

$$\Rightarrow V_{C3} = V_{C4} = V_{CC} - R_c \times \frac{I_{EE}}{2} - (V_{B1} - V_{BE(ON)})$$


subject: _____

Year: _____

★ Month: _____

☺ Date: _____

A_{vdm} : - o half circuit

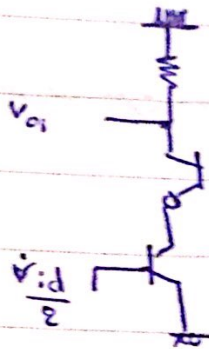

$$a_v : -g_m R_C$$

$$A_{vdm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}}$$


single ended

$$\frac{V_{o1}}{V_{id}/2} = -g_m R_C \Rightarrow \frac{V_{o1}}{V_{id}} = -\frac{1}{2} g_m R_C$$

$$A_{vd} = \frac{V_{o1} - V_{o2}}{V_{id}} = \frac{-\frac{1}{2} g_m R_C V_{id}}{V_{id}} - \frac{\frac{1}{2} g_m R_C V_{id}}{V_{id}} = -g_m R_C$$

★ Same as Common Emmitter ★


A_{vem} - o half circuit

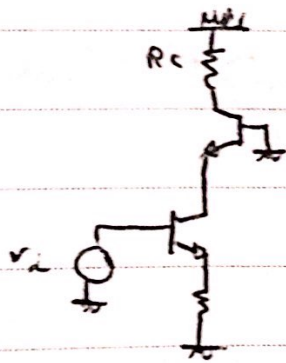

$$A_{vem} = \frac{-R_C}{2R_E + 1/g_m}$$


$$* A_{vdm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}} *$$

max output Swing

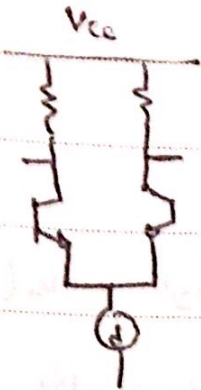

$$V_{CC} \rightarrow V_{CE(sat)}$$
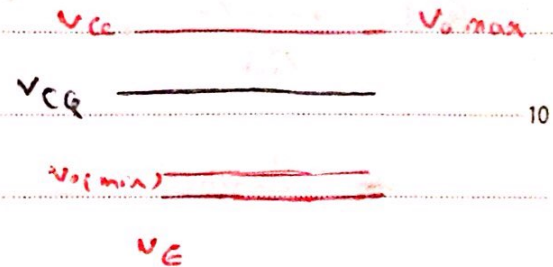
$$\Rightarrow V_{out, min} = V_E + V_{CE(sat)}$$



$$\text{max out swing} : V_{CE} = \frac{V_E + V_{CE(sat)} + V_{CC}}{2}$$

$$\Rightarrow \text{max swing } P.P = \frac{V_{CC} - V_{min}}{2} \quad \text{where } V_{min} = V_E + V_{CE(sat)}$$