

مسائل: 9.9, 9.22, 9.68, 9.77, 9.82, 9.89, 9.100, 9.103 از کتاب Irwin

- 9.9** Find the average power absorbed by the resistor in the circuit shown in Fig. P9.9 if $v_1(t) = 10 \cos(377t + 60^\circ)$ V and $v_2(t) = 20 \cos(377t + 120^\circ)$ V.

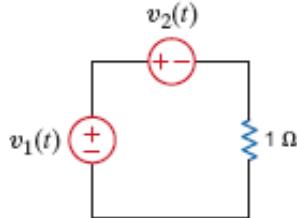


Figure P9.9

- 9.22** Calculate the average power absorbed by the $1\text{-}\Omega$ resistor in the network shown in Fig. P9.22.

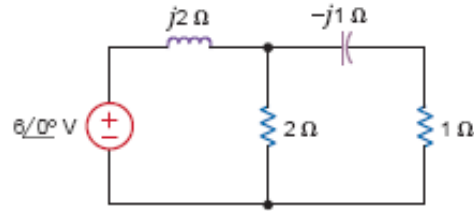


Figure P9.22

- 9.77** In the circuit shown in Fig. P9.77, calculate V_s , the complex power supplied by the source, and the power factor of the source.

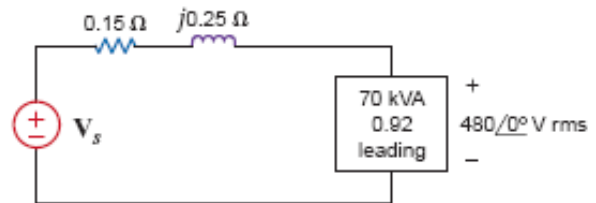


Figure P9.77

- 9.68** The power company supplies 80 kW to an industrial load. The load draws 220 A rms from the transmission line. If the load voltage is 440 V rms and the load power factor is 0.8 lagging, find the losses in the transmission line.

- 9.82** Given the network in Fig. P9.82, determine the input voltage V_s .

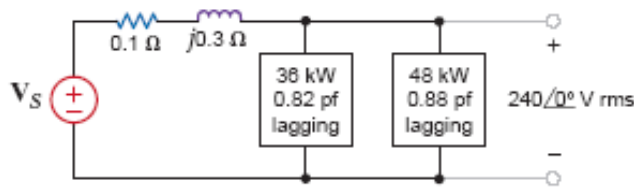


Figure P9.82

- 9.89** A particular load has a pf of 0.8 lagging. The power delivered to the load is 40 kW from a 270-V rms 60-Hz line. What value of capacitance placed in parallel with the load will raise the pf to 0.9 lagging?

- 9.103** A single-phase three-wire 60-Hz circuit serves three loads, as shown in Fig. P9.103. Determine I_{aA} , I_{nN} , I_c , and the energy use over a 24-hour period in kilowatt-hours.



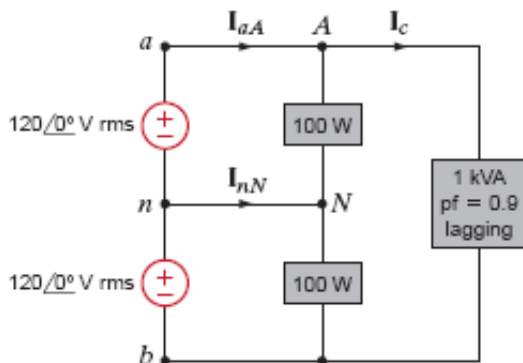


Figure P9.103

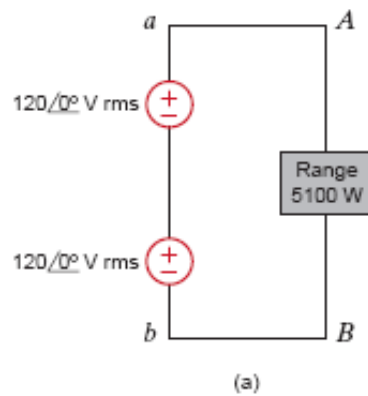- 9.100** A 5.1-kW household range is designed to operate on a 240-V rms sinusoidal voltage, as shown in Fig. P9.100a. However, the electrician has mistakenly connected the range to 120 V rms, as shown in Fig. P9.100b. What is the effect of this error?



(a)

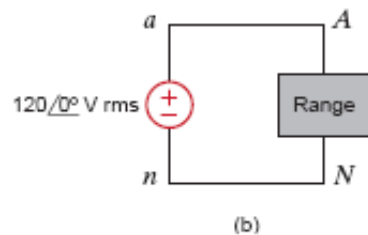

(b)

Figure P9.100