

2. Draw an oriented graph whose node-to-branch incidence matrix  $A_a$  is given by

$$A_a = \begin{bmatrix} 1 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & 0 & -1 & 0 & 1 & 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

3. Consider the oriented graph shown in Fig. P9.3

- Write the node-to-branch incidence matrix.
- Specify which of the following sets of branches are cut sets and justify your answer:  $\{1,9,5,8\}$ ,  $\{1,9,4\}$ ,  $\{6,8\}$ ,  $\{1,9,4,7,6\}$ , or  $\{3,4,5,6\}$ .

4. Consider the oriented graph shown in Fig. P9.4.

- Write equations corresponding to the cut sets indicated.
- Are these cut-set equations linearly independent?

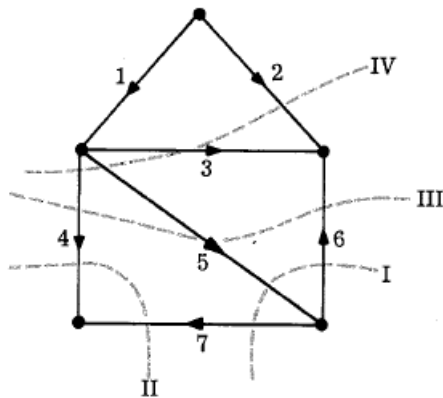


Fig. P9.4

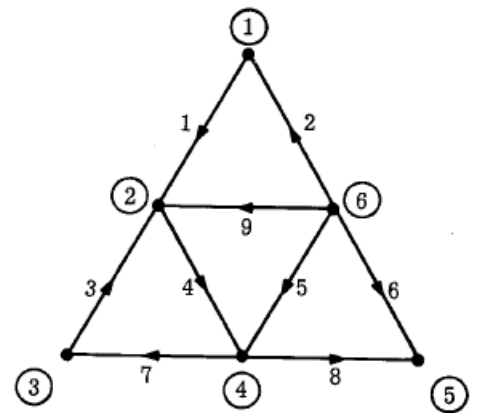


Fig. P9.3

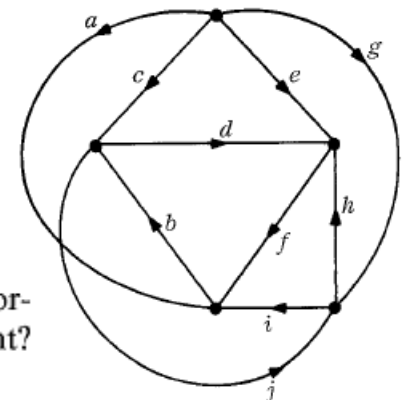


Fig. P9.5

5. Consider the graph shown in Fig. P9.5. Are the loop equations corresponding to loops  $abc$ ,  $bdf$ ,  $cde$ ,  $aei$ ,  $cehj$ , and  $bcgi$  linearly independent? Justify your answer.

Tellegen's  
theorem

7. The network  $\mathcal{N}$  shown in Fig. P9.7 is made of  $n - 2$  linear time-invariant resistors. Voltage and current measurements were taken for two values of  $R_2$  and the input. The measurements are tabulated in the figure. Determine the value  $\hat{v}_2$ .

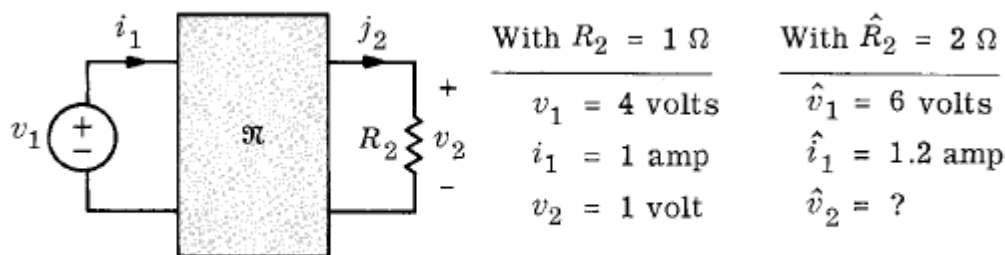


Fig. P9.7

Tellegen's  
theorem

9. Consider the sinusoidal steady-state measurements performed on a linear time-invariant  $RLC$  network, shown in Fig. P9.9. In both instances the same voltage source is used (same frequency and same phasor). Show that  $\hat{J}_1 = J_2$ . (Hint: Show that  $V_2 \hat{J}_2 + V_1 \hat{J}_1 = \hat{V}_2 J_2 + \hat{V}_1 J_1$ .)

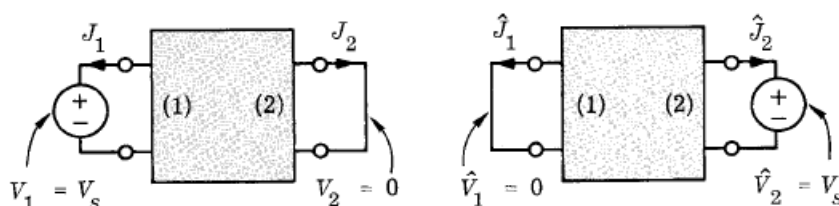


Fig. P9.9

10. Your technician measures the driving-point impedance (or admittance) at a fixed frequency  $\omega_0$  of a number of linear time-invariant networks made of passive elements. In each case, state whether or not you have any reasons to believe his results (in ohms or in mhos).

- $RC$  network:  $Z = 5 + j2$
- $RL$  network:  $Z = 5 - j7$
- $RLC$  network:  $Y = 2 - j3$
- $LC$  network:  $Z = 2 + j3$
- $RLC$  network:  $Z = -5 - j19$
- $RLC$  network:  $Z = -j7$

Whenever you accept a measurement as plausible, assume  $\omega_0 = 1$  rad/sec, and give a linear time-invariant passive network which has the specified network function.