

Introduction to Hardware Description Language (Verilog)

Kamyar Mirzazad
kammirzazad@ee.sharif.edu

Fall 2014

Digital vs. Analog Design

❖ Digital Design Advantages:

- More noise reliability
- Provides a perfect vehicle for digital signal processing
- Allows modular chip design
- Allows coding to achieve higher performance
- Allows encryption for higher security
- Can be verified on programmable devices before tape-out
- Enjoys the benefit of advanced sophisticated CAD tools

Digital Systems Components

❖ Printed Circuit Board (PCB)

❖ Software Oriented

- Microprocessor (general purpose)
- Microcontroller
- Digital Signal Processor (DSP)

Computer Structure /
Microprocessor

DSP Lab

❖ Programmable Logic Devices

- Simple Programmable Logic Device (SPLD)
- Complex Programmable Logic Device (CPLD)
- Field Programmable Gate Arrays (FPGAs)

Logic Circuits

❖ Application Specific Integrated Circuits (ASICs)

ASIC/FPGA
Chip Design

HDL Coding

- ❖ HDL allows us to describe the functionality of a logic circuit in a language that is
 - Easy to understand
 - Easy to share
 - Hides complicated implementation details
- ❖ Designer more concerned about the design functionality than the detailed design

Synthesis

❖ Synthesis tool:

- ❖ Analyzes a piece of Verilog code and converts it into optimized logic gates
- ❖ This conversion is done according to the “**language semantics**”
- ❖ **Input :**
 - HDL Code
 - “**Technology library**” file -> Standard cells (known by transistor size)
 - Basic gates (AND , OR , NOR , ...)
 - Macro cells (Adders , Muxes , Memory , Flip-Flops , ...)
 - Constraint file (Timing , area , power , loading requirement , optimization Algorithms)
- ❖ **Output:**
 - A gate-level “**Netlist**” of the design
 - Timing files (.sdf)

Introduction: Why HDL?

❖ Schematic entry not feasible for large designs:

- Time consuming to draw the schematic for millions of gates
- Subject to mistakes
- Difficult design entry and sharing
- Different design entry tools to learn
- Lack of Vendor independency : Tools not compatible (hard to convert the design from one to another)
- Not easy to modify

❖ Solution:

- Describe the design in text -> Hardware Description Language
- Just describe the design “**behavior**” not the detailed gate-level logic
- Gate-level logic is generated automatically by a “**synthesis**” tool

Advantages of HDL Coding

- ❖ Designer describes what the hardware should do without actually describing the hardware itself
- ❖ HDL Coding allows designers to separate behavior from implementation (*abstraction*)
- ❖ Designers develop an executable functional specification that documents the exact behavior of all the components and their interfaces
- ❖ Designers can make decisions about cost, performance, power, and area earlier in the design process

HDL is **NOT** a Software Programming Language

❖ Software Programming Language

- Language which can be translated with **compiler** into machine instructions (*assembly*) and then executed on a computer

❖ Hardware Description Language

- A specialized computer language used to describe the structure, design and operation of digital logic circuit , translated with **synthesizer** into executable specifications of H/W
- Includes an explicit notion of time

Hardware Description Language

❖ Verilog

- Introduction
- Language Fundamentals
- Modeling Combinational & Sequential Logic Circuits
- Modeling Finite State Machines
- Verilog Operations

HDL Coding

- ❖ A hardware Description Language is a high-level programming language that offers special constructs, used to model microelectronic circuits
- ❖ Two standard HDLs:
 - VHDL (Very high- speed integrated circuit HDL)
 - Verilog
- ❖ Verilog:
 - Developed by Philip Moorby in 1985 as a proprietary language
 - Open to public by Cadence Design Systems in 1990
 - IEEE Standard in 1995 and revised in 2001

Abstraction Levels in Verilog

❖ Three are types of Verilog Coding:

- **Behavioral:** *(Most Descriptive)*
 - Describes a system by the flow of data between its functions Blocks
 - Defines signal values when they change
- **RTL (Register Transfer Level):** *(Somehow descriptive)*
 - Describe how data transfers between registers and input/outputs
 - Describes a system by the flow of data and control signals between and within its functional blocks
- **Structural:** *(Least Descriptive)*
 - Shows detailed design components, nets, and interconnects
 - Uses technology-specific, low-level components
 - Used to pass netlist information between design tools

Behavioral Coding

- ❖ The behavioral level describes the behavior of a design without implying any specific internal architecture:
 - You use high level constructs, such as @, case, if, repeat, wait, while
 - You can use any behavioral constructs of the HDL in your **testbench**
 - Synthesis tools accept only a **limited subset** of these behavioral constructs

- ❖ This behavioral model defines the behavior of the design as seen at its port

```
1 module initial_fork_join();
2 reg clk,reset,enable,data;
3
4 initial begin
5     $monitor("%g clk=%b reset=%b enable=%b data=%b",
6         $time, clk, reset, enable, data);
7     fork
8         #1   clk = 0;
9         #10  reset = 0;
10        #5   enable = 0;
11        #3   data = 0;
12    join
13    #1 $display ("%g Terminating simulation", $time);
14    $finish;
15 end
16
17 endmodule
```

RTL Coding

- ❖ The RTL (functional) level describes the design architecture in sufficient detail that a synthesis tool can construct the circuit
- ❖ RTL coding is the closest one to the actual hardware implementation
- ❖ RTL code includes a subset of all Verilog syntax
 - Not all Verilog syntax are synthesizable

```
7 module decoder_using_case (  
8   binary_in    , // 4 bit binary input  
9   decoder_out  , // 16-bit out  
10  enable       // Enable for the decoder  
11 );  
12 input [3:0] binary_in ;  
13 input  enable ;  
14 output [15:0] decoder_out ;  
15  
16 reg [15:0] decoder_out ;  
17  
18 always @ (enable or binary_in)  
19 begin  
20     decoder_out = 0;  
21     if (enable) begin  
22         case (binary_in)  
23             4'h0 : decoder_out = 16'h0001;  
24             4'h1 : decoder_out = 16'h0002;  
25             4'h2 : decoder_out = 16'h0004;  
26             4'h3 : decoder_out = 16'h0008;  
27             4'h4 : decoder_out = 16'h0010;  
28             4'h5 : decoder_out = 16'h0020;  
29             4'h6 : decoder_out = 16'h0040;  
30             4'h7 : decoder_out = 16'h0080;  
31             4'h8 : decoder_out = 16'h0100;  
32             4'h9 : decoder_out = 16'h0200;  
33             4'hA : decoder_out = 16'h0400;  
34             4'hB : decoder_out = 16'h0800;  
35             4'hC : decoder_out = 16'h1000;  
36             4'hD : decoder_out = 16'h2000;  
37             4'hE : decoder_out = 16'h4000;  
38             4'hF : decoder_out = 16'h8000;  
39         endcase  
40     end  
41 end  
42  
43 endmodule
```

Structural Coding

- ❖ Synthesis tools produce a purely structural design description.
- ❖ The structural level is also appropriate for small library components:
 - You can use built-in Verilog primitives, such as the **and** gate
 - You can describe your own User Defined Primitives (UDPs)
- ❖ This structural model instantiates predefined library components


```
module some_logic_component (c, a, b);  
    // declare port signals  
    output c;  
    input a, b;  
    // declare internal wire  
    wire d;  
    //instantiate structural logic gates  
    and a1(d, a, b); //d is output, a and b are inputs  
    not n1(c, d);    //c is output, d is input  
endmodule
```

Verilog Fundamentals

- ❖ Module
- ❖ Signals
 - ❖ Signal Type
 - ❖ Signal Range
 - ❖ Signal Name
- ❖ Parameters
- ❖ Memories
- ❖ Operators
- ❖ Statements
 - ❖ Concurrent Statements
 - ❖ Procedural Statements


Verilog Fundamentals: Module

 - ❖ Any circuit or subcircuit is declared as a “module” in Verilog.
- ❖ Each module may have:
 - Ports (Three possibilities)
 - Input
 - Output
 - Inout
 - Signals (main or intermediate)
 - Body-code
(statements for module description)



```
module DUT ( A , B , C );  
    input  A;  
    output B;  
    inout C;  
  
    Signals  
  
    Body-Code  
  
endmodule
```


Verilog Fundamentals: Signals

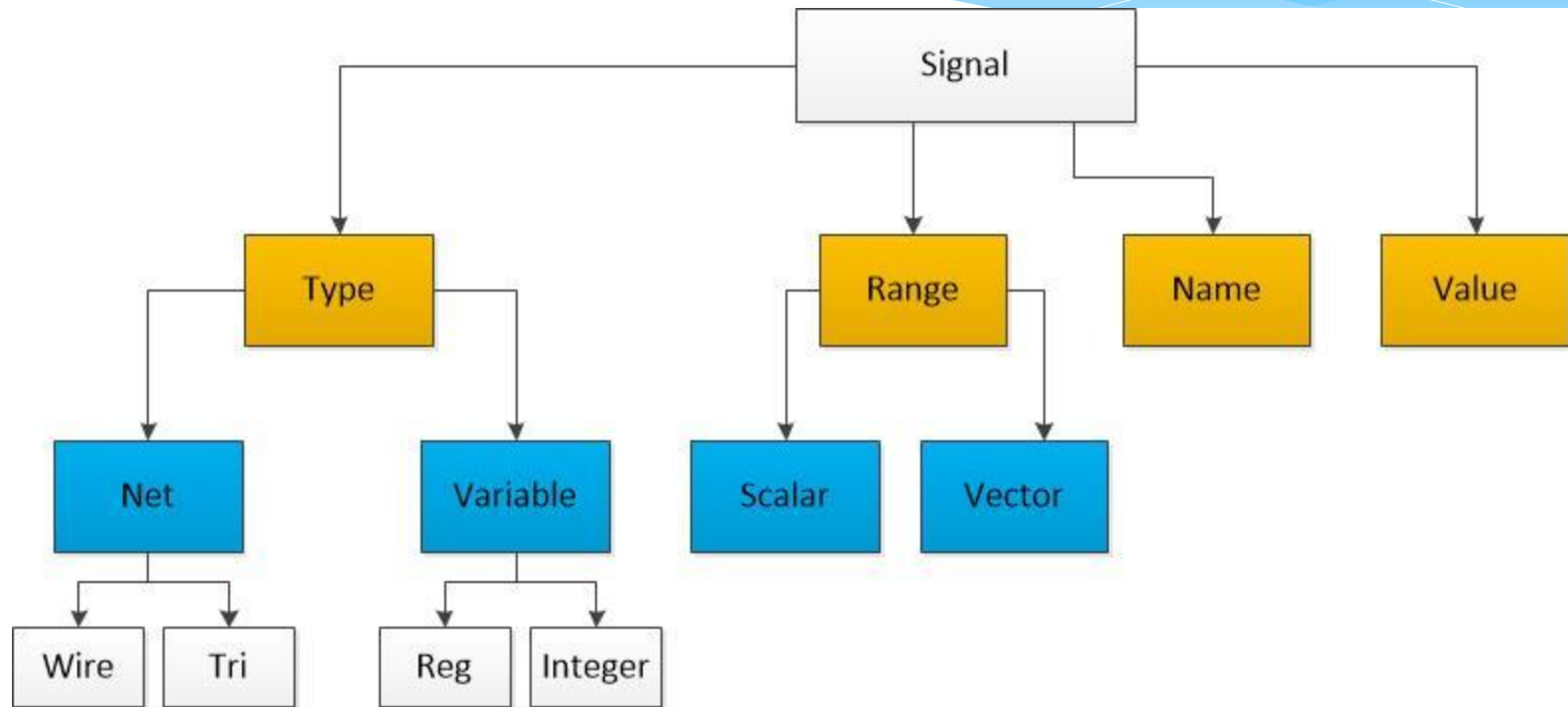

Verilog Fundamentals : Signal Type

❖ Net


- wire:
 - For interconnecting logic elements (LEs)
 - To connect an output of a logic element to the input of another LE
- Tri:
 - Circuit nodes that are connected in a tri-state fashion

❖ Variable

- reg (*unsigned in general*)
 - Corresponds to a circuit node (*not necessarily a register!*)
 - Allow a circuit to be described in terms of its behavior
 - Retains its value until it is overwritten by a subsequent assignment
- integer (*signed in general*)
 - Used for loop counters



Verilog Fundamentals : Signal Type

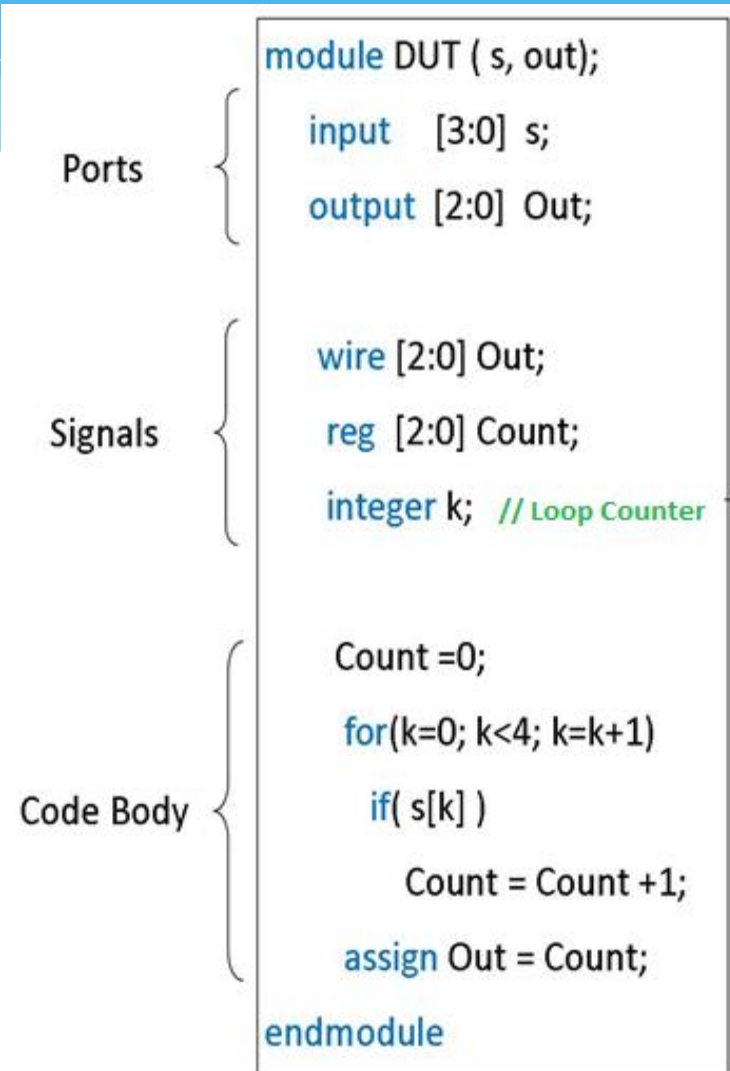- ❖ The “wire” declarations are not necessary as Verilog assumes that signals are nets by default.
- ❖ The “reg” declaration is required.
- ❖ Don’t forget to use semicolon after module definition



Reg Type

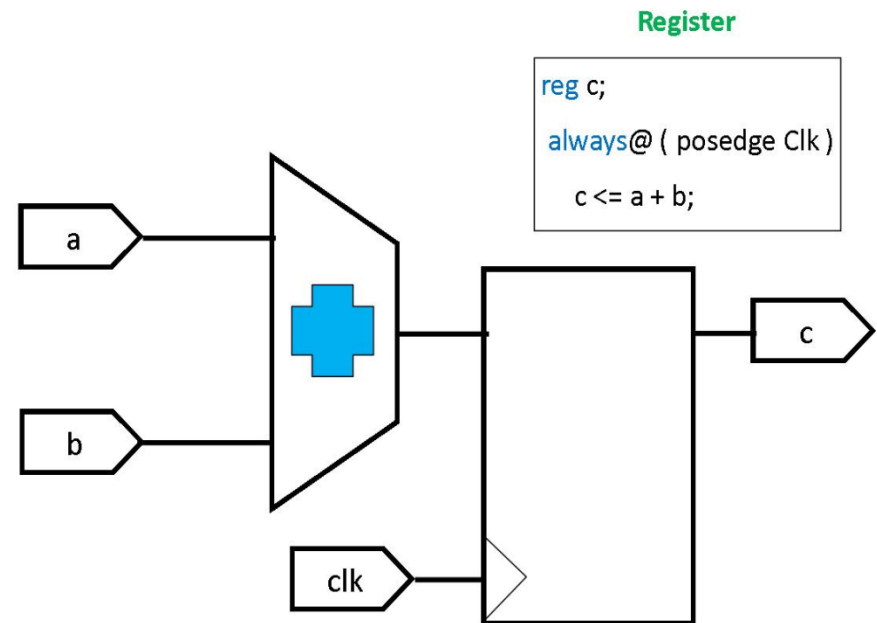 - ❖ The keyword “reg” does NOT necessarily denote a storage element or register.
- ❖ “reg” only models the behavior of a circuit.
- ❖ May or may not be synthesized as a register.



Verilog Fundamentals : Signal Range

❖ Signals in Verilog can be:

- **Scalar** : representing a node

```
reg C;
```

```
wire B;
```

- **Vector** : representing a bus

```
reg [10:0] Data;
```

```
reg [ 0:6] S;
```

```
wire [ 7:4] B;
```

❖ Each element of a bus can be accessed

```
assign a = Data[8];
```

Verilog Fundamentals: Signal Name

❖ Signal name may consist of:

- Any letter
- Any digit
- Underscore () and \$ sign

❖ DON'Ts:

- Should not start with a digit
- Should not be a Verilog keyword

Legal

A_m

B1_signal

My\$

Illegal

1xb

wire

R&z

Verilog Fundamentals: Signal Value

❖ Scalar: each scalar signal can have four possible values:

- 0 : Logic Value “0”
- 1 : Logic Value “1”
- Z(z) : Tri-State (high impedance) (such as open-circuit)
- X(x) : Unknown value (such as conflict)

❖ Vector: <# of bits> <base> < number>

- <# of bits> : number of bits for representation
- <base> : “d” Decimal / “b” Binary / “h” Hexadecimal / “o” Octal
- <number> : signal value in base

Verilog Fundamentals: Signal Value

❖ Example

- $A = 8'hag \rightarrow A = 1010\ 1001$
- $B = 4'd3 \rightarrow B = 0011$
- $C = 4'b100 \rightarrow C = 0100$
- $D = 'b10x \rightarrow D = (32\text{-bit})\ 10X$
- $E = -16'd47 \rightarrow E = 1111\ 1111\ 1101\ 0001$

Verilog Fundamentals : Parameters

- ❖ A parameter is used as a “constant” to facilitate coding
 - Example:

```
module DUT ( s , Out );  
  
    parameter n = 3;  
    parameter So = 4'b1010;  
    input  [n-1:0] s;  
    output [ n:0] Out;  
    wire   [n:0] Out;  
    assign Out = So;  
  
endmodule
```

Verilog Fundamentals : Memories

❖ Memory:

- A two dimensional array of bits
- Declared in Verilog as a two-dimensional variable (reg)
- Example: A 4-byte memory

reg [7:0] R [3:0] ;

└───┘ └───┘
8-bit 4 rows (cell)

	0	1	2	3	4	5	6	7
R[0]	R[0][0]							
R[1]						R[1][5]		
R[2]				R[2][3]				
R[3]								R[3][7]

Verilog Fundamentals : Memories

- ❖ A three-dimensional array may also be declared.
 - Example : `reg [7:0] M [3:0][1:0];`
- ❖ If an 8-bit A is declared then the legal assignment is:
 - `reg [7:0] A → A = M[3][0];`

Verilog Fundamentals : Operators

❖ Bitwise

Operation	Result
1010 & 1100	1000
1010 1100	1110
~ 1010	0101
1101 ^ 0100	1001

❖ Logical

Operation	Result
1010 && 1100	1
2'b11 2'b00	1
! 0010	0
2'b1X && 2'b11	X

If any operand is X/Z, result is Z

Verilog Fundamentals : Operators

❖ Reduction

Operation	Result
$\& 1100$	0
$ 111$	1
$\wedge 0100$	1

❖ Relational

Operation	Result
$2'b10 == 2'b10$	1
$2'b10 == 2'b11$	0
$2'b10 === 2'b1x$	0
$2'b10 <= 2'b11$	1

$==$ Used only with 0 and 1

$===$ Used with x and z

Verilog Fundamentals : Operators

❖ Logical Shift

$A = 6'b001100$

Operation	Result
$A \gg 1$	000110
$A \ll 2$	110000
$A \gg 3$	000001

❖ Concatenation

$A = 2'b11$
 $B = 3'b010$


Operation	Result
$\{A, B\}$	5'b11010
$\{3\{A\}\}$	6'b111111
$\{B, B\}$	6'b010010
$\{\{3\{A\}\}, \{2\{B\}\}\}$	12'b111111010010

Verilog Fundamentals : Operators

❖ Conditional : (?, :)


`D = S ? B : C;`

 $D = \begin{cases} B & \text{if } S=1; \\ C & \text{if } S=0; \end{cases}$



`D = ({ S1 , S1 } == 2'b00) ? F :
 ({ S1 , S2 } == 2'b01) ? E :
 ({ S1 , S2 } == 2'b10) ? C : B ;`
 default
 
`D = ({ S1 , S1 } == 2'b00) ? F :
 ({ S1 , S2 } == 2'b01) ? E :
 ({ S1 , S2 } == 2'b10) ? C :
 ({ S1 , S2 } == 2'b11) ? B : B ;`
 default



Verilog Fundamentals : Operators

Type Of Operators	Symbols					
Concatenate & Replicate	{}	{{}}				
Unary	!	~	&	^	^~	
Arithmetic	*	/	%			
	+	-				
Logical Shift	<<	>>				
Relational	<	<=	>	>=		
Equality	==	!=	===	!==		
Binary bit-wise	&	^	^~			
Binary logical	&&					
Conditional	?:					

Verilog Fundamentals : Module-Revisited

❖ Any circuit or subcircuit is declared as a “module” in Verilog

❖ There are three types of ports:

- input → type “wire”
- output → type “wire” or “reg”
- inout → type “wire”

```
module DUT ( A , B , C)
```

```
input  A;
```

```
output [3:0] B;
```

```
inout  C;
```

```
wire  A;      // Optional
```

```
wire  C;
```

```
reg   [3:0] B ; // Mandatory
```

```
// reg declaration can be combined  
with port declaration
```

Signals

Body-code

```
endmodule
```


Verilog Fundamentals : Module Ports*

❖ Inside view of the module

- inout : wire
- input port : wire
- **output port : wire or reg**

❖ Outside view of the module

 - inout : wire
- **input port : wire or reg**
- output port : wire



Verilog Fundamentals : Module-Revisited

- ❖ In Verilog-2001 the port list can directly follow the module declaration

- ❖ Body-code consist of some “**statements**”

```
module DUT ( A , B , C );  
  input  A;  
  output [3:0] B;  
  inout  C;  
  wire   A;  
  wire   C;  
  reg    [3:0] B;  
  
  Signals  
  
  Body-code  
  
endmodule
```



```
module DUT ( input A ,  
             output [3:0] B ,  
             inout C );  
  
  wire   A;  
  wire   C;  
  reg    [3:0] B;  
  
  Signals  
  
  Body-code  
  
endmodule
```

- ❖ Statements describe the circuit/module functionality

Verilog Fundamentals : Statements

❖ Programming languages:

- **High-Level Language (HLL)** : C, Pascal, Matlab
- **Hardware Description Language (HDL)** : Verilog, HDL

❖ In HLL programming all statements are sequential (procedural)

- Statements evaluated in the order and one-by-one

❖ Verilog Statements

- **Procedural** : evaluated sequentially (Order **IS** important)
- **Concurrent** : evaluated in parallel (Order is **NOT** important)

```
always@ ( x , y )  
begin  
    s = x^y;  
    c = x&y;  
end
```


→ assign s = x^y;

→ assign c = x&y;

→ assign out = x|y;

Verilog Fundamentals : Concurrent Statements

 - ❖ Evaluated in parallel
- ❖ Each statement describes part of the circuit, thus concurrent
- ❖ Most popular:
 - **Continuous statements** : realized as connection or **wire** in the design
 - **Format :**



`wire [1:3] A, B, C;`
`assign C = A & B;`

↔

`assign C[1] = A[1] & B[1];`
`assign C[2] = A[2] & B[2];`
`assign C[3] = A[3] & B[3];`

- **assign** used only for nets (to be synthesizable)

Concurrent Statements

❖ Example : Full Adder, same circuit, two descriptions:

```
module Adder ( Cin, x, y, S, Cout );
```

```
  input  x, y, Cin;
```


```
  output S, Cout;
```

```
  wire   S, Cout;
```

```
  assign S = x ^ y ^ Cin;
```

```
  assign Cout = (x&y) | (x&Cin) | (y&Cin)
```

```
endmodule
```

 

```
module Adder ( Cin, x, y, S, Cout );
```

```
  input  x, y, Cin;
```

```
  output S, Cout;
```

```
  wire   S, Cout;
```

```
  assign { Cout , S } = x + y + Cin;
```

```
endmodule
```


X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

Concurrent Statements

- ❖ In Verilog “+” declares unsigned addition
- ❖ Signed addition has to be explicitly specified using the sign extension
- ❖ **Example:** Signed vs. unsigned addition


```
module Adder_sign ( X, Y, S_unsigned, S_signed );  
    input  [3:0] X, Y;  
    output [4:0] S_unsigned, S_signed;  
    assign S_unsigned = X + Y ;  
    assign S_signed   = {{X[3]},X} + {{Y[3]},Y} // Sign Extension  
endmodule
```

 X = 0100 (unsigned 4) or (signed +4)
Y = 1100 (unsigned 12) or (signed -4)




```
module Adder_sign ( X, Y, S_unsigned, S_signed );  
    parameter n = 4;  
    input  [n-1:0] X, Y ;  
    output [n:0] S_unsigned , S_signed ;  
    assign S_unsigned = X + Y;  
    assign S_signed   = {{X[n-1]} , X} + {{Y[n-1]} , Y};  
endmodule
```

 S_unsigned = 10000 (unsigned 16)
S_signed = 00000 (signed 0)



Procedural Statements

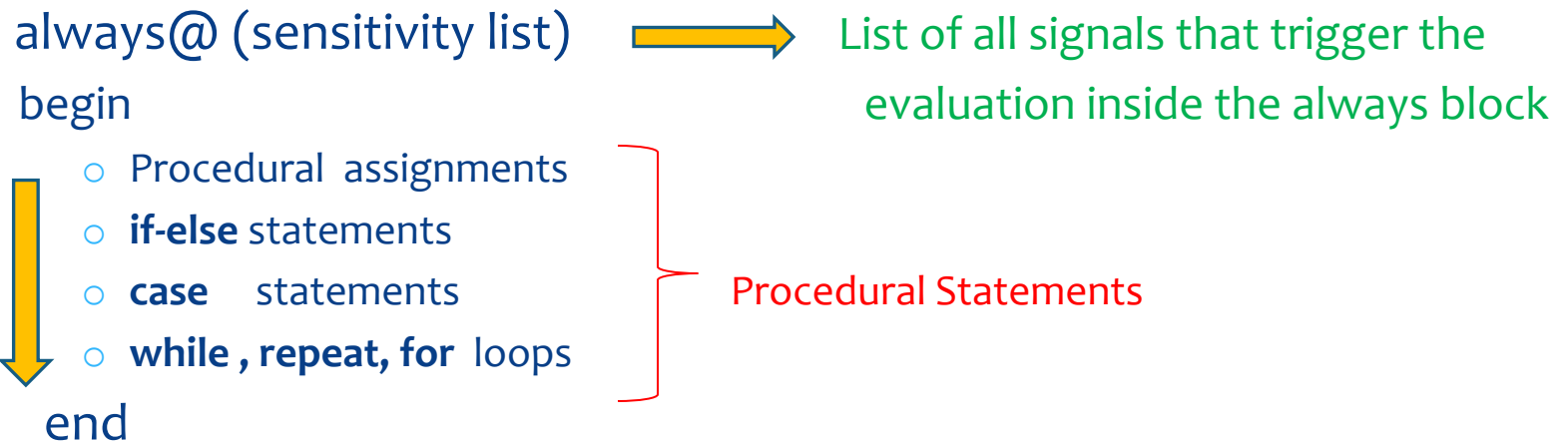- ❖ Evaluated in the order in which they appear in the code (sequential)
- ❖ Should be inside an **“always”** block
- ❖ An **“always”** block contains one or more procedural statements



Procedural Statements : Half Adder

- ❖ Anything on the RHS should be on the sensitivity list
 - always @(*) → Automatically considers all signals on the RHS in sensitivity list
- ❖ Any signal assigned inside an always block has to be a variable of **reg** or **integer** type

```
module Adder ( x, y, S, C);  
    input  x,y;  
    output S,C;  
    reg    S,C; // Variable inside always  
    block should be of reg type  
    always@ (x,y)  
    begin  
        S = x ^ y;  
        C = x & y;  
    end  
endmodule
```



```
module Adder ( x, y, S, C,)  
    input x, y;  
    output S, C;  
    wire S, C;  
    assign S = x ^ y;  
    assign C = x & y;  
endmodule
```

Always block

- ❖ The always construct requires begin-end only if there are multiple statements in the block

```
always@ (x,y,z)
```

```
begin
```

```
z = x;
```

```
if (x==1)
```

```
z = y;
```

```
end
```

Correct

```
always@ (x,y,z)
```

```
z = x;
```

```
if( x== 1)
```

```
z = y;
```

Incorrect

Not part of the always block

- ❖ A given variable should never be assigned a value in more than one always block because **always** blocks are **concurrent** with respect to **one another**

```
always@ (x,y)
```

```
a <= x;
```

```
always@ (x,y)
```

```
a <= y;
```

Incorrect

```
always@ (x,y)
```

```
begin
```

```
a <= x;
```

```
a <= y;
```

```
end
```

↔ always@ (x,y)
a <= y;

Correct

Procedural Assignments


❖ Used inside an always block and are of two types:

- Blocking: denoted by “=” token
 - Evaluation within the always block is “blocked” until this assignments is completed
- Non-blocking: denoted by “<=” token
 - Nothing is hold or blocked (parallel evaluation)

Blocking vs. Non-Blocking Assignments

❖ Blocking

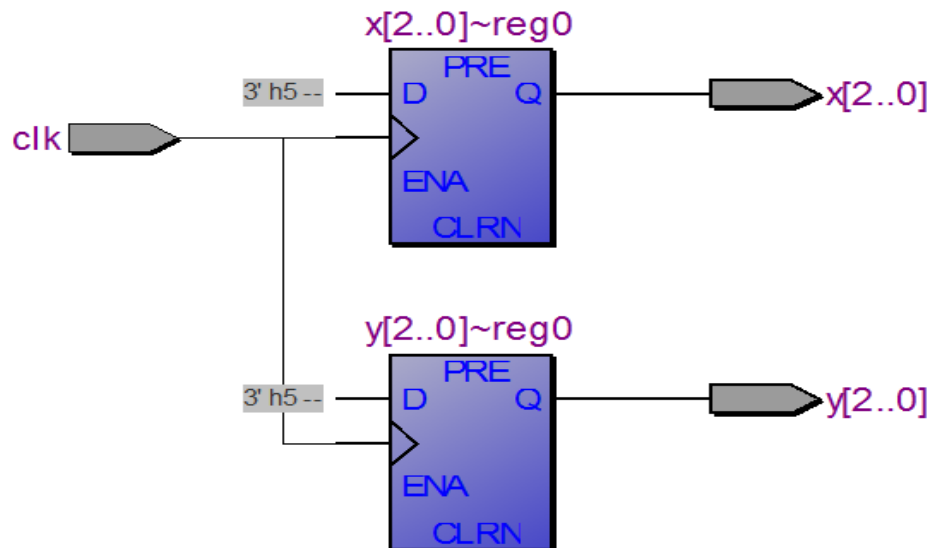- Evaluated and assigned in a single step
- Sequential nature
- Assignment **ordering IS important**
- S=5 “blocks” y=x to be executed
 - y=x has to wait for x=5 to be executed first



assume x=2 then

```
always@ (*)
```

```
begin
```

```
    x = 5;
```

```
    y = x;
```

```
end
```




x = 5 & y = 5

(sequential)

Blocking vs. Non-Blocking Assignments

- ❖ What happens if we change order of two blocking assignments in previous slide?

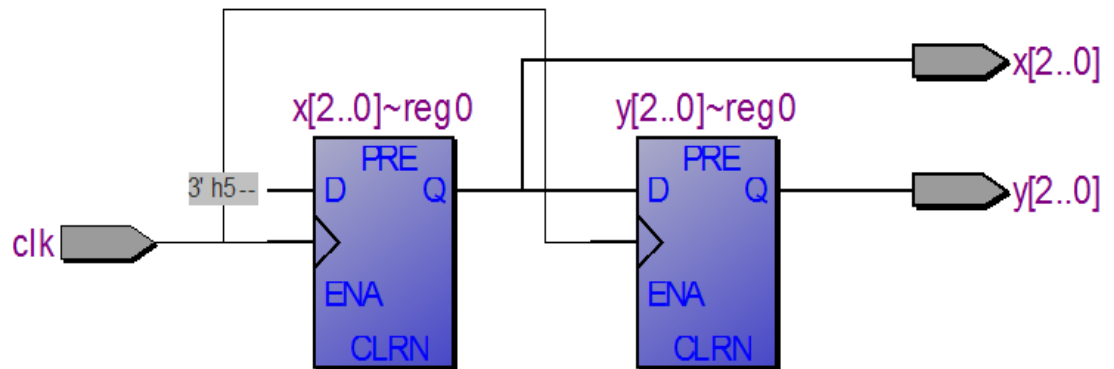
```
assume x= 2 then  
always@(*)  
begin  
    y = x;  
    x = 5;  
end
```



Blocking vs. Non-Blocking Assignments

❖ Non-Blocking

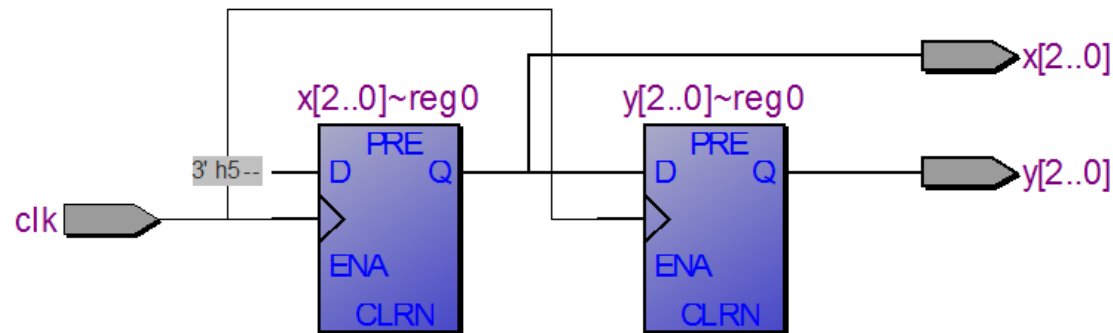- Evaluated and assigned in two steps
 1. All RHSs are evaluated in parallel
 2. Assignments to LHS are performed together
- They all are executed all at once
- Assignment ordering is **NOT** important
- $y \leq x$ and $x \leq 5$ executed in parallel



assume x=2 then

`always@ (*)`

begin

`x <= 5;`

`y <= x;`

end




`x = 5 & y = 2`

(parallel)

Blocking vs. Non-Blocking Assignments

❖ **Example:** Swap bytes in words

 

Blocking

```
always @(*)
```

```
begin
```

```
  B[15:8] = B[ 7:0] ;
```

```
  B[ 7: 0] = B[15:8] ;
```

```
end
```

Incorrect

Non-Blocking

```
always @(*)
```



```
begin
```

```
  B[15:8] <= B[ 7:0] ;
```

```
  B[ 7: 0] <= B[15:8] ;
```

```
end
```

Correct

  

Description of some common logic circuits in Verilog

- * Decoder
- * Encoder
- * Multiplexer
- * Demultiplexer
- * Parity Generator
- * Arithmetic & Logic Unit (ALU)

Decoder

```
module decoder_structural( input wire en , input wire [2:0] in , output wire [7:0] out );

    and bit0(out[0], !in[2], !in[1], !in[0] , en ); // 000
    and bit1(out[1], !in[2], !in[1], in[0] , en ); // 001
    and bit2(out[2], !in[2], in[1], !in[0] , en ); // 010
    and bit3(out[3], !in[2], in[1], in[0] , en ); // 011
    and bit4(out[4], in[2], !in[1], !in[0] , en ); // 100
    and bit5(out[5], in[2], !in[1], in[0] , en ); // 101
    and bit6(out[6], in[2], in[1], !in[0] , en ); // 110
    and bit7(out[7], in[2], in[1], in[0] , en ); // 111

endmodule
```

```
module decoder_rtl( input wire en , input wire [2:0] in , output wire [7:0] out );
```

```
    reg [7:0] val;
```

```
    always@(*)
```

```
        case (in)
```

```
            3'b000: val = 8'b00000001;
```

```
            3'b001: val = 8'b00000010;
```

```
            3'b010: val = 8'b00000100;
```

```
            3'b011: val = 8'b00001000;
```

```
            3'b100: val = 8'b00010000;
```

```
            3'b101: val = 8'b00100000;
```

```
            3'b110: val = 8'b01000000;
```

```
            3'b111: val = 8'b10000000;
```

```
        endcase
```

```
    assign out = (en)? val : 8'b0 ;
```

```
endmodule
```

Encoder

```
module encoder_structural( input wire [7:0] in , output wire valid , output wire [2:0] out );

    and bit2( out[2] , in[1] , in[3] , in[5] , in[7] );
    and bit1( out[1] , in[2] , in[3] , in[6] , in[7] );
    and bit0( out[0] , in[4] , in[5] , in[6] , in[7] );

    assign valid = |out;

endmodule

module encoder_rtl( input wire [7:0] in , output wire valid , output wire [2:0] out );

    reg [2:0] val;

    always@(*)
        case (in)
            8'b00000001 : val = 3'b000;
            8'b00000010 : val = 3'b001;
            8'b00000100 : val = 3'b010;
            8'b00001000 : val = 3'b011;
            8'b00010000 : val = 3'b100;
            8'b00100000 : val = 3'b101;
            8'b01000000 : val = 3'b110;
            8'b10000000 : val = 3'b111;
        endcase

    assign out    = val;
    assign valid = |out;

endmodule
```

Multiplexer

```
module multiplexer_structural( input wire [2:0] sel , input wire [7:0] in , output wire out );

    wire [7:0] mins;

    and min0( mins[0] , !sel[2] , !sel[1] , !sel[0] , in[0] ); // 000
    and min1( mins[1] , !sel[2] , !sel[1] , sel[0] , in[1] ); // 001
    and min2( mins[2] , !sel[2] , sel[1] , !sel[0] , in[2] ); // 010
    and min3( mins[3] , !sel[2] , sel[1] , sel[0] , in[3] ); // 011
    and min4( mins[4] , sel[2] , !sel[1] , !sel[0] , in[4] ); // 100
    and min5( mins[5] , sel[2] , !sel[1] , sel[0] , in[5] ); // 101
    and min6( mins[6] , sel[2] , sel[1] , !sel[0] , in[6] ); // 110
    and min7( mins[7] , sel[2] , sel[1] , sel[0] , in[7] ); // 111

    assign out = |mins;

endmodule

module multiplexer_rtl( input wire [2:0] sel , input wire [7:0] in , output wire out );

    reg val;

    always@(*)
        case (sel)
            3'b000: val = in[0];
            3'b001: val = in[1];
            3'b010: val = in[2];
            3'b011: val = in[3];
            3'b100: val = in[4];
            3'b101: val = in[5];
            3'b110: val = in[6];
            3'b111: val = in[7];
        endcase

    assign out = val;

endmodule
```

Demultiplexer

```
module demultiplexer_structural( input wire in , input wire sel , output wire [1:0] out );  
  
    and bit0( out[0] , !sel , in ); // 0  
    and bit1( out[1] , sel , in ); // 1
```

```
endmodule
```

```
module demultiplexer_rtl( input wire in , input wire sel , output wire [1:0] out );
```

```
    reg [1:0] val;
```

```
    always@(*)
```

```
        begin
```

```
            if( sel == 1'b0 )
```

```
                val[0] = in;
```

```
            else
```

```
                val[0] = 0;
```

```
            if( sel == 1'b1 )
```

```
                val[1] = in;
```

```
            else
```

```
                val[1] = 0;
```

```
        end
```

```
    assign out = val;
```

```
endmodule
```

Parity Generator

```
module parity_gen_structural( input wire [3:0] in , output wire even_parity , output wire odd_parity );  
  
    xor xor1( even_parity , in[3] , in[2] , in[1] , in[0] );  
  
    assign odd_parity = !even_parity;  
  
endmodule  
  
module parity_gen_rtl( input wire [3:0] in , output wire even_parity , output wire odd_parity );  
  
    reg  val;  
  
    always@(*)  
        if( ^in )  
            val = 1'b1;  
        else  
            val = 1'b0;  
  
    assign odd_parity = !val;  
    assign even_parity = val;  
  
endmodule
```

Arithmetic and Logic Unit

```
module alu_structural( input wire sel , input wire [1:0] a , input wire [1:0] b , output wire [1:0] c );

    wire [1:0] a_or_b, a_or_b_and_sel;
    wire [1:0] a_and_b, a_and_b_and_sel;

    or or0 (a_or_b[0],a[0],b[0]);
    or or1 (a_or_b[1],a[1],b[1]);

    and and0 (a_and_b[0],a[0],b[0]);
    and and1 (a_and_b[1],a[1],b[1]);

    and and2 (a_or_b_and_sel[0],a_or_b[0],sel);
    and and3 (a_or_b_and_sel[1],a_or_b[1],sel);

    and and4 (a_and_b_and_sel[0],a_and_b[0],!sel);
    and and5 (a_and_b_and_sel[1],a_and_b[1],!sel);

    or or2 (c[0],a_or_b_and_sel[0],a_and_b_and_sel[0]);
    or or3 (c[1],a_or_b_and_sel[1],a_and_b_and_sel[1]);

endmodule

module alu_rtl( input wire sel , input wire [1:0] a , input wire [1:0] b , output wire [1:0] c );

    reg [1:0] val;


    always@(*)
        if(sel)
            val = a | b;
        else
            val = a & b;

    assign c = val;

endmodule
```

Overall Code Parallelism

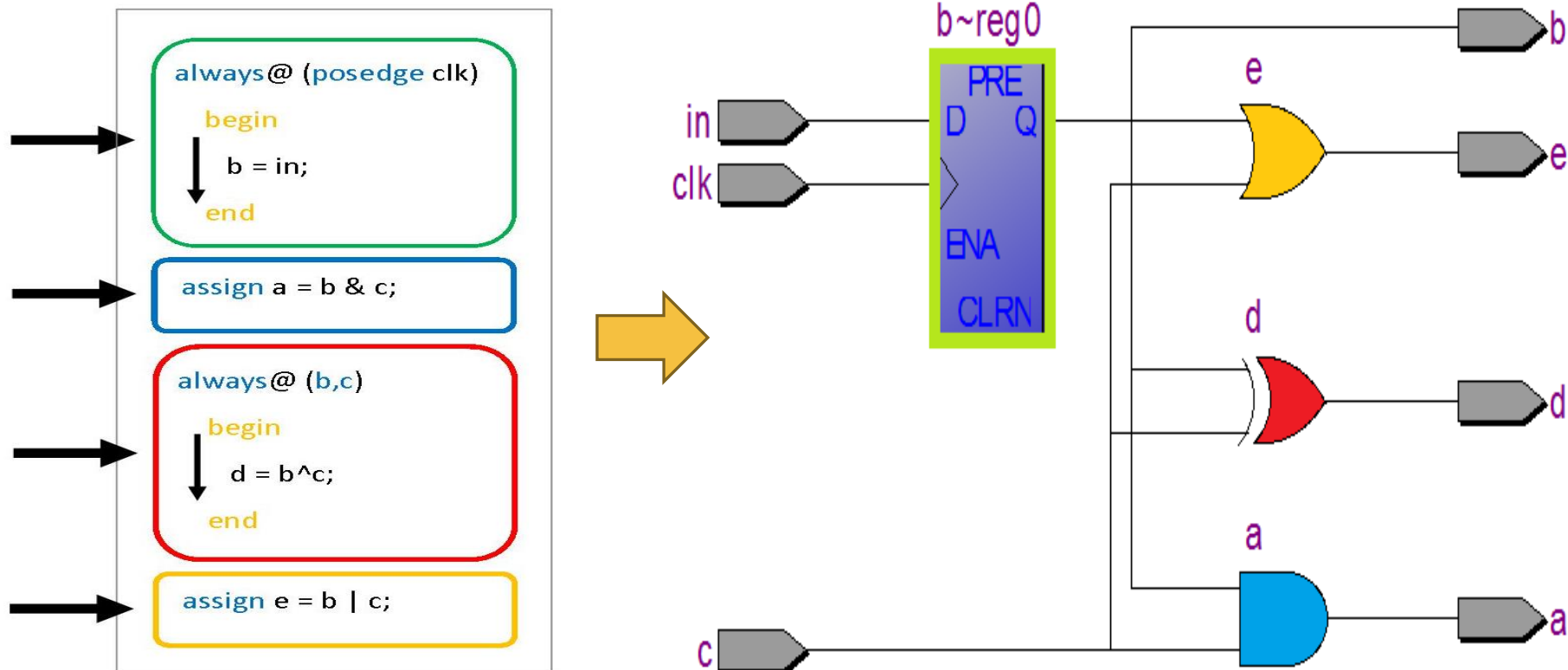- ❖ Statements inside an always block are evaluated sequentially
- ❖ However, all always blocks are evaluated concurrently
- ❖ All continuous assignments are evaluated concurrently too



Verilog Assignments

❖ Procedural

Inside an always block

- Blocking (=)

- Non-Blocking (<=)

- ❑ **Left** side of **procedural** assignment should be variable of **reg** or **integer** type

❖ Continuous

Using assign statement (**assign**)

- ❑ **Left** side of **continuous** assignment should be variable of **net** type

Logic Circuits Category

❖ **Combinational Logic:** (realized by **assign** and **always**)


- Output depends on inputs
- Inputs propagates to the output through some gates with delay
- for example : adder, mux , multiplier, all logic gates

❖ **Sequential Logic:** (realized only by **always**)

- Output depends on inputs and history circuit
- Circuit history is kept using flip-flops, registers or latches
- for example : Finite State Machines (FSM) , shift registers, Flip Flops
- is divided into two groups:
 1. **Synchronous** : all registers controlled by a global clock
 2. **Asynchronous** : based on the handshaking process

Logic Circuits Category

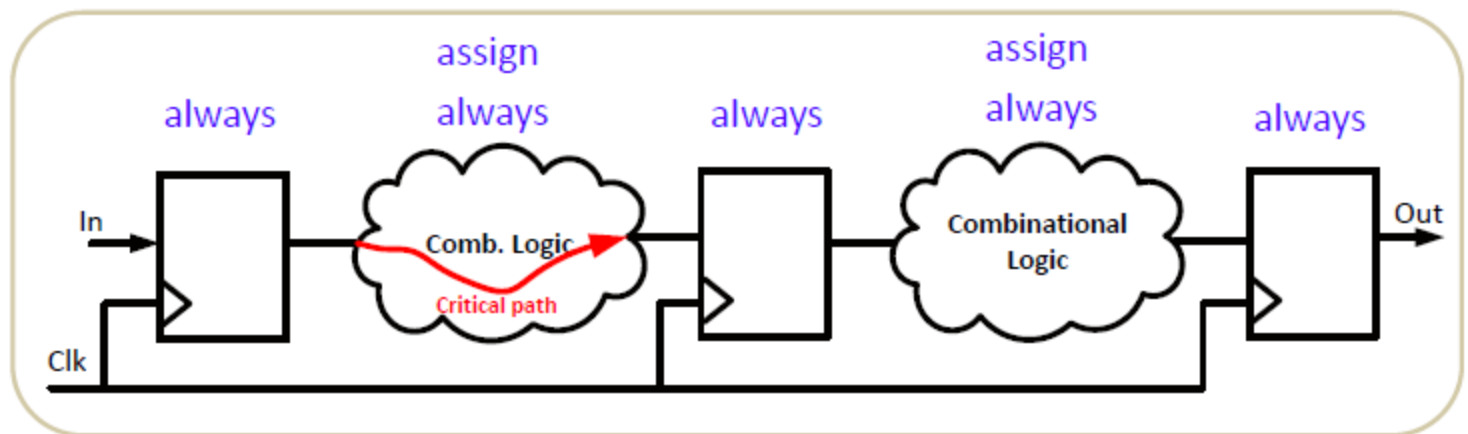- ❖ A general system consists of both combinational and sequential circuits



- ❖ Critical path of the Comb. Logic determines the max operating frequency
- ❖ Combinational logic can be realized using **assign** and **always** constructs
- ❖ Sequential logic can only be realized using **always** blocks

Combinational Logic

- ❖ When using always block for Com. Logic, “blocking” assignments are used
- ❖ When using an always block, time instant changes when one of the sensitivity list variables changes
- ❖ Example:
Half Adder

```
module Adder (x, y, S, C);  
    input x, y;  
    output reg S, C;  
    always@ (x,y)  
        begin  
            S = x ^ y;  
            C = x & y;  
        end  
endmodule
```



```
module Adder (x, y, S, C);  
    input x, y;  
    output wire S, C;  
    assign S = x ^ y;  
    assign C = x & y;  
endmodule
```

Blocking Assignment for Combinational Logic

- ❖ Use only **blocking** assignments for **combinational** logic.
- ❖ In **multiple concurrent non-blocking** assignments to a variable, the **last one** executes
- ❖ Example: Accumulator (Initial value of Count is zero)

```
always @(*)  
begin  
    for( k=0; k<4; k=k+1 )  
        Count = Count + k;  
end
```



```
Count = Count + 0;  
Count = 0 + 1;  
Count = 0 + 1 + 2;  
Count = 0 + 1 + 2 + 3;  
Result : Count = 6
```

Correct

```
always @(*)  
begin  
    for( k=0; k<4; k=k+1 )  
        Count <= Count + k;  
end
```




```
Count <= Count + 0;  
Count <= Count + 1;  
Count <= Count + 2;  
Count <= Count + 3;  
Result : Count = 3
```

Incorrect

Combinational Logic

- ❖ Procedural assignments update the value of **reg**. The value will remain unchanged till another procedural assignment updates the variable. This is the main difference with continuous assignments in which the **right** hand expression is **constantly** placed on the **left** side
 
```
module DUT( input wire x, y,  
            output reg _xor ,  
            output wire _xnor );  
  
    always@(x,y)  
        _xor = x ^ y;  
  
    assign _xnor = ~_xor;  
  
endmodule
```




always vs. assign for describing combinational logic

- ❖ When Combinational Logic involves high complexity, it is preferred to use always block to describe it, because **always** block provides powerful statements like *if-else* , *case* and loop constructs
- ❖ Always block comes with more clarity and more concise description than **assign**

Sequential Logic

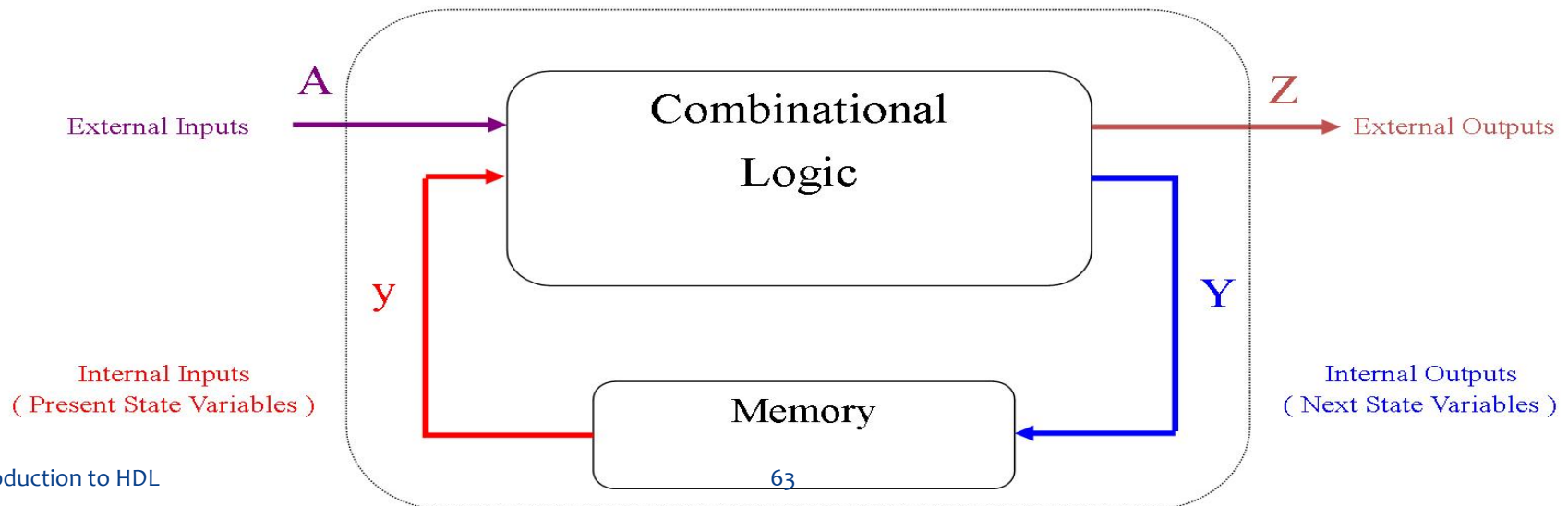- ❖ Sequential logic is a type of logic circuit whose output depends not only on the present value of its input signals but on the past history of its inputs
- ❖ Current state is held in memory and the next state is computed through the combinational logic
- ❖ In a synchronous system, global clock signal organizes the flow of the data and the sequence of events





Sequential Logic

- ❖ Sequential logic can only be realized using an **always** block
- ❖ Consist of
 - Flip flops that are normally controlled by:
 - Positive edge of the clock (**posedge**)
 - Negative edge of the clock (**negedge**)
 - Latches
 - Transfers input to output when clock is “1” and otherwise stores the value
 - Finite State Machine (**FSM**)
- ❖ When using the always block for the sequential logic , “**Non-blocking**” assignments are used

Sequential Logic



❖ Flip-flop with **asynchronous** Reset:
  
```
always@(posedge Clk, negedge Reset)
  if (Reset==0)
    Q <= 0;
  else
    Q <= D;
```



❖ Flip-flop with **synchronous** Reset:

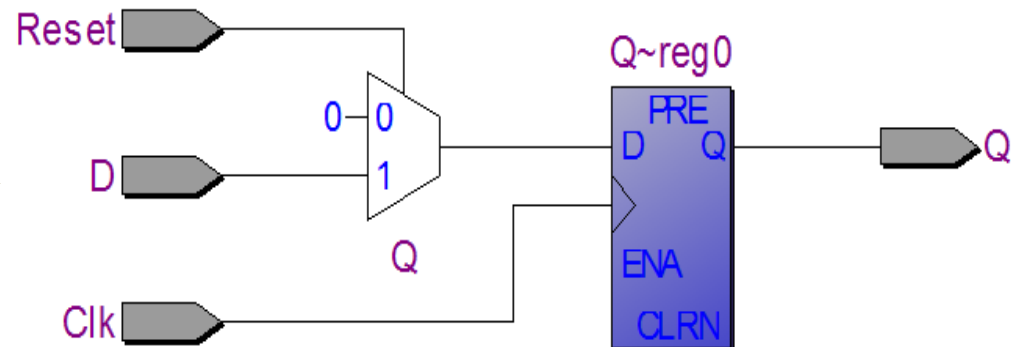 
```
always@(posedge Clk)
  if (Reset==0)
    Q <= 0;
  else
    Q <= D;
```



Sequential Logic

❖ D-Latch
 
```
always@ ( D , Clk )  
  if (Clk)  
    Q <= D;
```



❖ What happens if we remove **D** from sensitivity list?

Nothing , this results in **same** latch with **warning** saying D is not in the sensitivity list

Verilog Registers


- ❖ The keyword “reg” does NOT necessarily denote a storage element or register.
- ❖ In digital design , registers represent memory elements
- ❖ Registers in Verilog should not be confused with hardware registers , the term register (reg) simply means a variable that can hold a value
- ❖ Verilog registers don't need a clock and don't need to be driven like a net.

Verilog Registers

- ❖ May or may not be synthesized as a register


Not Register

```
always@ (a , b)  
C = a + b;
```

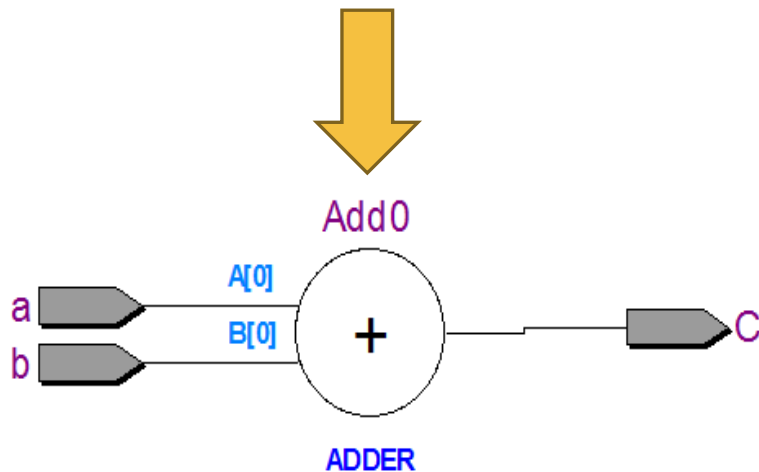

Register
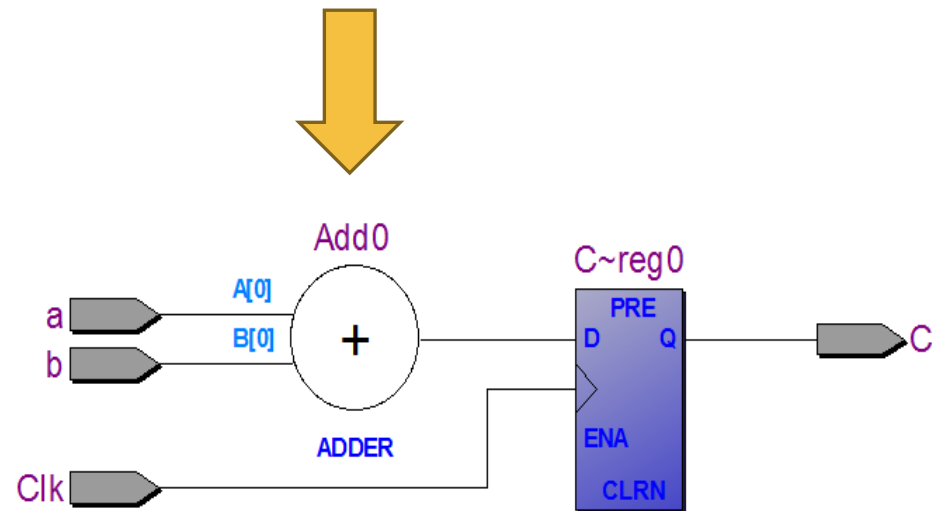
```
always@ (posedge Clk)  
C = a + b;
```




Sequential Logic

- * When describing sequential logic using always block, “Non-Blocking” assignments are used.




```
integer k;  
reg    [3:0] A;  
assign Shift_Out = A[3];
```
 
```
always@(posedge Clk)  
begin  
    A[0] = Shift_In;  
    for(k=1;k<4;k=k+1)  
        A[k] = A[k-1];  
end
```



```
integer k;  
reg    [3:0] A;  
assign Shift_Out = A[3];
```
 
```
always@(posedge Clk)  
begin  
    A[0] <= Shift_In;  
    for(k=1;k<4;k=k+1)  
        A[k] <= A[k-1];  
end
```



If-else statements

❖ Used only inside always block

❖ Format:

```
if ( expression1 )  
    statement1;  
else if ( expression2 )  
    statement2;  
else  
    statement3;
```


Single statement no need for **begin-end**
Multiple statements , **begin-end** is needed



```
module Mux21(input  wire in1,in2,s,  
             output reg  out);
```

```
always@(in1,in2,s)  
    if(s==0)  
        out = in1;  
    else  
        out = in2;
```

```
endmodule
```

 

```
module Mux21(input  wire in1,in2,s,  
             output reg  out);
```


```
always@(in1,in2,s)  
begin  
    out = in1;  
    if(s==1)  
        out = in2;  
end
```

```
endmodule
```


If-else statements

- ❖ If-else construct inside an always block have a sequential nature when used by blocking assignments.
- ❖ This means ordering is important
 
```
always@(*)  
begin  
    out = in1;  
    if(s==1)  
        out = in2;  
end
```


 
```
always@(*)  
begin  
    if(s==1)  
        out = in2;  
    out = in1;  
end
```



Case Statements

❖ Used only inside an **always** block

❖ Format:

```
case ( expression )  
  option1 : statement1;  
  option2 : begin  
              statement2;  
            end  
  default : statementn;  
endcase
```

← Single statement no need for **begin-end**

← Multiple statements , **begin-end** is needed

❖ Example :

```
module Mux21(input  wire in1,in2,s,  
             output reg  out);
```

```
  always@(in1,in2,s)  
    case (s)  
      1'b0: out = in1;  
      1'b1: out = in2;  
    endcase
```

```
endmodule
```



```
module Mux21(input  wire in1,in2,s,  
             output reg  out);
```

```
  always@(in1,in2,s)  
    case (s)  
      1'b0 : out = in1;  
      default: out = in2;  
    endcase
```

```
endmodule
```


Case Statements

- ❖ Example: Combinational logic using both **assign** and **always** block

```
module HalfAdder(input wire x,y,
                 output wire Cout,S);

    assign S      = x^y;
    assign Cout   = x&y;

endmodule
```



```
module HalfAdder( input wire x,y,
                  output reg Cout,S);

    always@(x,y)
    begin
        case ( {x,y} )
            2'b00: {Cout,S} = 2'b00;
            2'b01: {Cout,S} = 2'b01;
            2'b10: {Cout,S} = 2'b10;
            2'b11: {Cout,S} = 2'b11;
        endcase
    end

endmodule
```

Case Statements

- ❖ In case statements, each alternative is compared for an exact match
- ❖ Synthesis tools are only concerned about matching of “0” and “1” while “Z” and “X” are not important.
- ❖ If for simulation purposes, “X” or “Z” are needed to be added, **casex** is used which treats them as don't care.
- ❖ Example: 4-to-2 priority encoder

w3	w2	w1	w0	y1	y0	f
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1



```
module PriorityEncoder(input  wire [3:0] W,
                      output wire f,
                      output reg  [1:0] Y);

    assign f = (W!=0);
    always@ (W)
    begin
        casex(W)
            4'b1xxx: Y=3;
            4'b01xx: Y=2;
            4'b001x: Y=1;
            default: Y=0;
        endcase
    end

endmodule
```

Latch Inference in Combinational Logic

- ❖ When realizing combinational logic with always block using if-else or case constructs care has to be taken to avoid latch inference after synthesis
- ❖ The latch is inferred when “incomplete” if-else or case statements are declared
- ❖ This latch is “unwanted” as the logic is combinational not sequential
- ❖ A variable assigned within an **always** block that is **not fully** specified in all branches will infer a latch

Latch Inference in Combinational Logic

- ❖ To avoid latch inference make sure to specify all possible cases “explicitly”
- ❖ Two practical approaches to avoid latch inference:
 - For if-else construct:
 - 1) Initialize the variable **before** the **if-else** construct
 - 2) Use **else** to explicitly list all possible cases
 - For case constructs:

Use **default** to make sure all cases are covered.

Avoid Latch Inference in If-else Statements


✗ Latch Inference

```
module DUT1(input wire A,B,S,
            output reg out);

    always@(*)
    begin
        if(S==1)
            out = A;
        end

endmodule
```

out\$latch

 

No Latch

```
module DUT2(input wire A,B,S,
            output reg out);


    always@(*)
    begin
        out = B;
        if(S==1)
            out = A;
        end

endmodule
```

```
module DUT3(input wire A,B,S,
            output reg out);

    always@(*)
    begin
        if(S==1)
            out = A;
        else
            out = B;
        end

endmodule
```

 


Avoid Latch Inference in Case Statements

✗ Latch Inference

```
module DUT1(input  wire A,B,
            input  wire [1:0]S,
            output reg  out);

    always@ (A,B,S)
    begin
        case (S)
            2'b00: out=A;
            2'b01: out=B;
        endcase
    end

endmodule
```

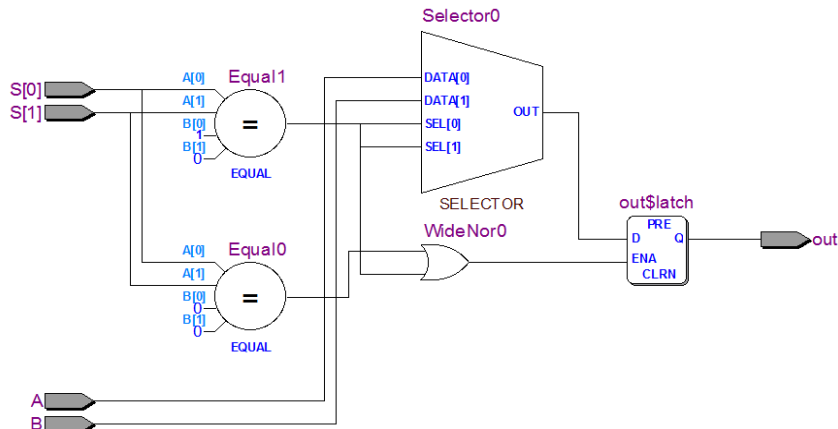


✓ No Latch

```
module DUT2(input  wire A,B,
            input  wire [1:0]S,
            output reg  out);

    always@ (A,B,S)
    begin
        case (S)
            2'b00: out=A;
            2'b01: out=B;
            default: out=1'b0;
        endcase
    end

endmodule
```

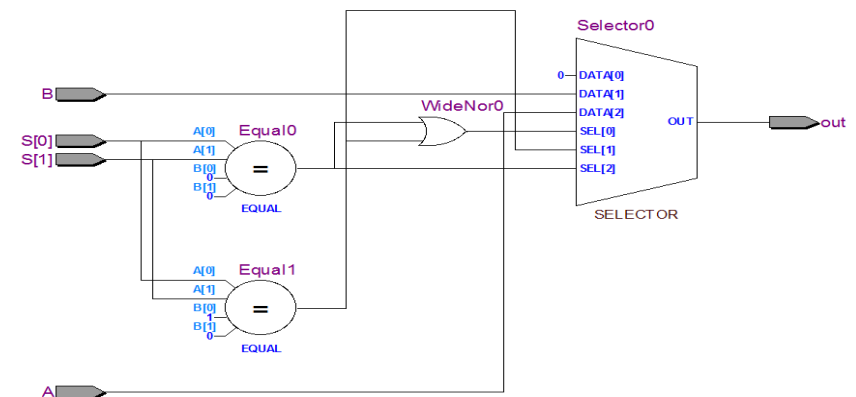

Using Sub-modules

- ❖ A design can use multiple sub-modules or a module multiple times
- ❖ Using a module in another is called “instantiation”
- ❖ Top-level module: the module that has not been instantiated
- ❖ To use a module inside another, it should be explicitly instantiated
- ❖ There are some built-in primitive logic gates in Verilog that can be instantiated
 - Built-in primitives means there is no need to define a module for these gates
 - and , nand , nor , or , xor , xnor , buf , not

Using Sub-modules

```
module Myand ( input wire in1 , in2 , output out );  
  
    and myand ( out , in1 , in2 );           // instantiate  
  
    assign out = in1 & in2;                 // assign  
  
    reg out ;  
    always@ ( in1 , in2 )                   // always block  
        out = in1 & in2;  
  
endmodule
```


Sub-modules Instantiation

- ❖ To instantiate a module , two things have to be clearly specified
 - module's ports
 - module's parameters (considered as default if not specified)

- ❖ Format:

```
Module_name #(parameter_value) instance_name ( .port_name(port-connection)  
, .port_name(port_connection), ... )
```



```
Module_name instance_name ( .port_name(port-connection),  
.port_name(port_connection), ... )  
defparam instance_name.parameter_name = parameter_value
```

- ❖ If port connections are in the same order as the original module
“**.port_name**” is not needed in the port list.

Sub-modules Instantiation

```
module Full_Adder ( input  wire Cin , x , y ,  
                   output wire S , Cout );  
  
    assign S      = x ^ y ^ Cin;  
    assign Cout = (x & y) | ( x & Cin ) | ( y & Cin );  
endmodule
```

```
module RippleCarryAdder ( input  wire [n-1:0] X , Y , input wire Cin ,  
                        output wire [n-1:0] S      , output wire Cout );  
  
    parameter n = 4;  
    wire [n-1:0] C;  
  
    Full_Adder stage0 ( Cin , X[0] , Y[0] , S[0] , C[1] );  
    Full_Adder stage1 ( Cin , X[1] , Y[1] , S[1] , C[2] );  
    Full_Adder stage2 ( Cin , X[2] , Y[2] , S[2] , C[3] );  
    Full_Adder stage3 (.Cout(Cout), .Cin(C[3]), .x(X[3]), .y(Y[3]), .S(S[3]));  
  
endmodule
```

Sub-modules Instantiation


```
module Add_Sub_Byte ( input  wire [7:0] X , Y , input wire Op ,  
                      output wire [8:0] S      );  
    // Subtract Y from X if Op = 1 otherwise add X + Y  
    wire Cout;  
    wire Y_2 [5:0] = Y ^ { 8'b111111};  
  
    defparam  moduleo.n = 6;  
    Full_Adder moduleo( .Cin(op) , .x(X) , .y(Y) , .S(S[7:0]) , .Cout(S[8]) );  
  
endmodule
```

Priority Logic


- ❖ The order in which assignments are written in an always block may affect the logic that is synthesized.

- ❖ Example:
 
```
always@(s0,s1,d0,s1)
begin
  Q = 0;
  if(s0) Q = d0;
  else if (s1) Q = d1;
end
```


 
```
always@(s0,s1,d0,s1)
begin
  Q = 0;
  if(s1) Q = d1;
  else if (s0) Q = d0;
end
```



Counter

4-Bit Unsigned Down Counter With Synchronous Set


```
module D_counter ( input  Clk , S ,  
                   output [3:0]Q);  
  
    reg [3:0] tmp;  
    always@(posedge Clk)  
    begin  
        if( S )  
            tmp <= 4'b1111;  
        else  
            tmp <= tmp -1'b1;  
        end  
    assign Q = tmp;  
  
endmodule
```

4-Bit Unsigned Down Counter With Synchronous Set

```
module D_counter ( input  Clk , S ,  
                   output [3:0]Q);  
  
    reg [3:0] tmp;  
    always@(posedge Clk or negedge Rst)  
    begin  
        if( Rst == 0)  
            tmp <= 4'b0000;  
        else  
            tmp <= tmp +1'b1;  
        end  
    assign Q = tmp;  
  
endmodule
```


Finite State Machine (FSM)

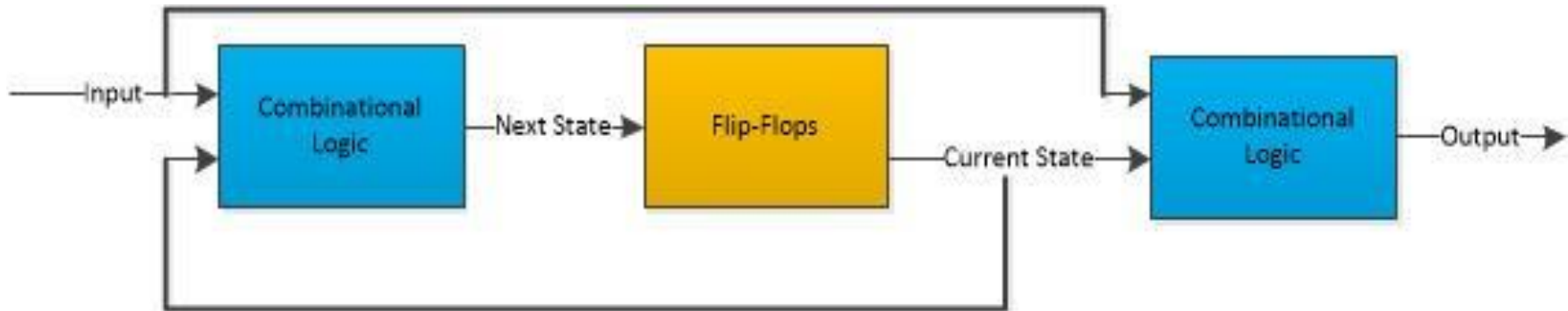- ❖ An abstract machine that can be in one of a finite number of states. The machine is in only one state at a time (current state)
- ❖ Two types :
 - Mealy: Output depends on the “current state” and the “input”



Finite State Machine (FSM)

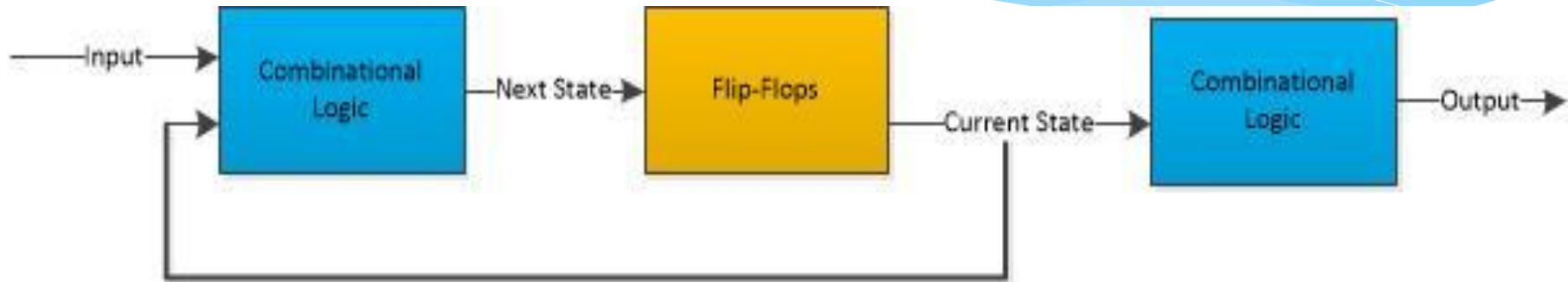
- ❖ Moore: Output depends **only** on the “**current state**”



- ❖ A FSM can be described in terms of its
 - Current State
 - Next State
 - Output


FSM Code Structure

Mealy

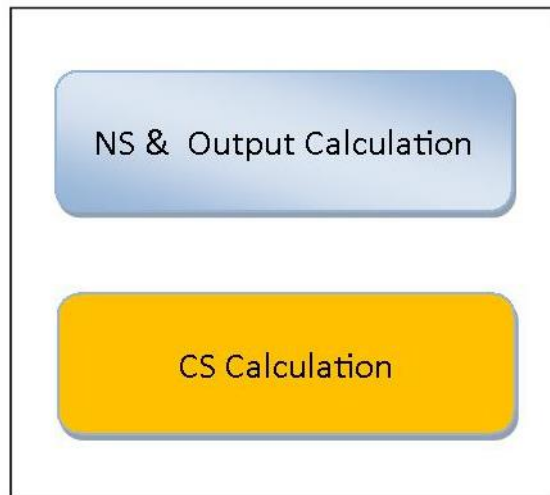

- ❖ NS & Output Calculation mainly implemented using blocking assignments & case struct inside always block


Moore

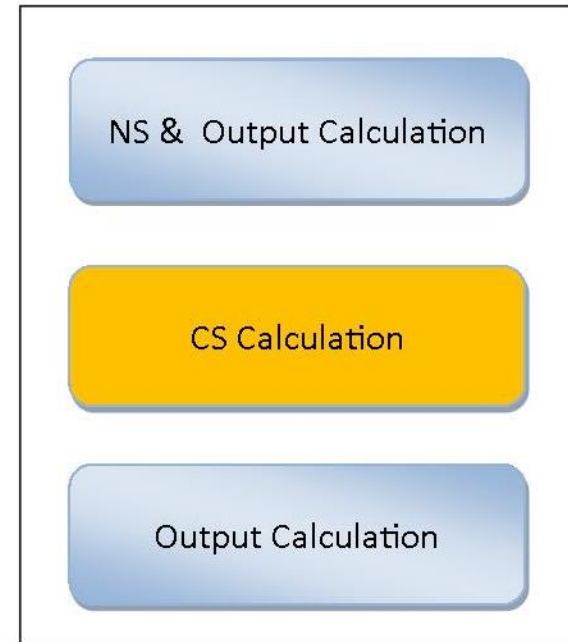


- ❖ NS Calculation mainly implemented using blocking assignments & case struct inside always block
- ❖ Output Calculation mainly implemented using assign statements

Mealy Machine

❖ State Diagram

 

❖ RTL View

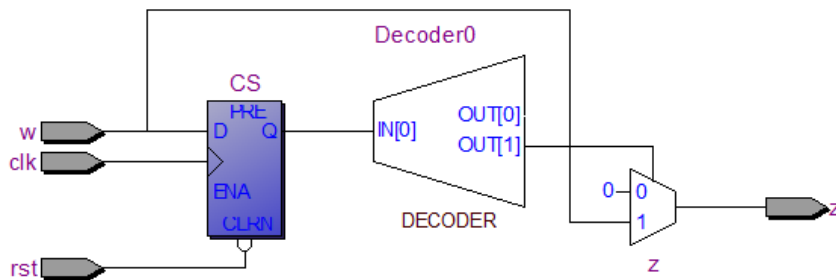

```


module mealy(input wire clk, w, rst,
             output reg z);
    reg CS , NS;
    parameter A=1'b0, B=1'b1;

    // NS & Output Calculation ( Combinational )
    always@(w,CS)
    case (CS)
        A: if(w==0)
            begin
                NS = A; z = 0;
            end
        else
            begin
                NS = B; z = 0;
            end
        B: if(w==0)
            begin
                NS = A; z = 0;
            end
        else
            begin
                NS = B; z = 1;
            end
    endcase

    // CS Calculation ( Sequential )
    always@(posedge clk, negedge rst)
    if( rst == 0 )
        CS <= A;
    else
        CS <= NS;
endmodule
  
```

Moore Machine

❖ State Diagram

 

```
module mealy(input wire clk, w, rst,
             output wire z);
    reg [1:0] CS, NS;
    parameter A=2'b00, B=2'b01, C=2'b10, D=2'b11;

    // NS Calculation ( Combinational )
    always@(w,CS)
        case (CS)
            A: NS = (w)? B : A;
            B: NS = (w)? C : B;
            C: NS = (w)? D : C;
            D: NS = (w)? A : D;
        endcase

    // CS Calculation ( Sequential )
    always@(posedge clk, negedge rst)
        if( rst == 0 )
            CS <= A;
        else
            CS <= NS;

    // Output Calculation
    assign z = ( CS == D );

endmodule
```

Verification

* Testbench

- * An **unsynthesizable** Verilog module that instantiates main Verilog design and examines behavior and output of design by applying predetermined inputs to it.
- * High-level unsynthesizable keywords such as `initial` , `$display` , `$stop` , `$fopen` , `$readmem`, are available for debugging purposes
- * Define **time unit** and **precision** by ``timescale` at the beginning of testbench
 - * Time unit specifies time amount #1 refers to
 - * Examples: ``timescale 1ns / 1ns` - ``timescale 1ns / 100ps`
- * Testbench module usually has **no ports**

Verification

- * Value of signal “a” at time “t “ after start of simulation can be specified by initial #t a = val
- * In more general form “#t” can be used to specify delay in any assignment
- * Statement above can be used to generate clock with desired period to be applied to sequential design

```
reg clk;
```

```
initial clk = 1'b0;
```

```
always #T clk = ~ clk;
```

- * These generate clk with period equal to 2T whose initial value is 0.
- * Do not forget to initialize clk : If not initialized, clk value will be undefined (X) in simulation start and will persist through simulation

Simulation commands

- * Register array used as memory can be initialized by variants of command `$memread ($memreadb - $memreadh)`
- * `$display` command can be used anywhere inside `always` block or after initial statement to print signal
 - * Arguments of command `$display` are **same** as those of `printf` in C
 - * Example : `$display(“ Clk value is %b” , clk);`
- * Command `$stop` can be used to stop simulation at any time
 - * Example: To stop simulation at time 1000 => `initial #1000 $stop;`

Verification

```
`timescale 1 ns / 1 ns

module parity_gen_tb();

    reg [3:0] data_in;
    wire      even_parity, odd_parity;

    parity_gen_rtl pg0(.in(data_in),.even_parity(even_parity),.odd_parity(odd_parity));

    always@(*)
    begin
        if( ($time == 5) && ( ( even_parity != 1'b0 ) || ( odd_parity != 1'b1 ) ) )
            $display(" data in = %b , even parity = %b , odd parity = %b " , data_in , even_parity , odd_parity );

        if( ($time == 15) && ( ( even_parity != 1'b1 ) || ( odd_parity != 1'b0 ) ) )
            $display(" data in = %b , even parity = %b , odd parity = %b " , data_in , even_parity , odd_parity );
    end

    initial #0 data_in = 4'b1010;
    initial #10 data_in = 4'b1011;

    initial #50 $display( " Done verifying parity generator! ");
    initial #50 $stop;

endmodule
```

References

- * Dr.Shabany's Slides for ASIC/FPGA Chip Design
 - Available online at ee.sharif.edu/~asic
- * Introduction to Verilog
 - ee.mut.ac.th/course/eeet0413/ppt/Chapter10%20Verilog.ppt
- * Asic - World Website
 - asic-world.com
- * Wikipedia : Various Articles