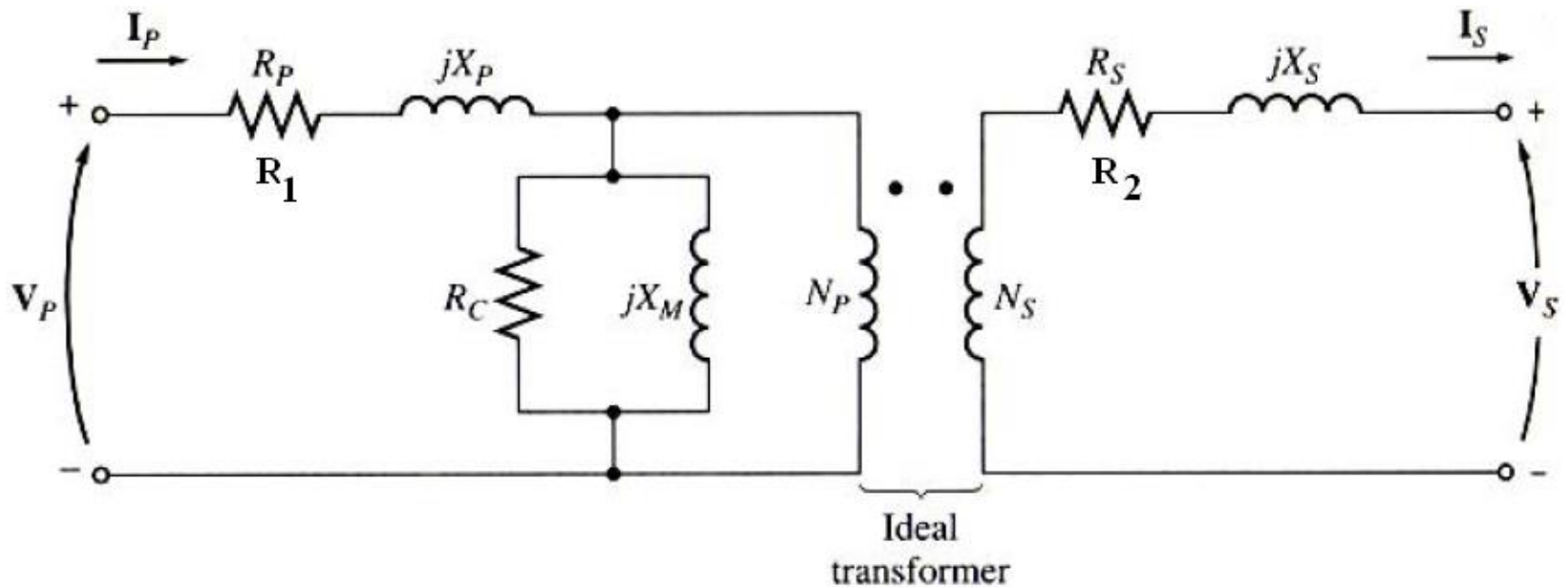


Transformer Modeling


The equivalent circuit




Transformer Modeling

The equivalent circuit

Referred to primary

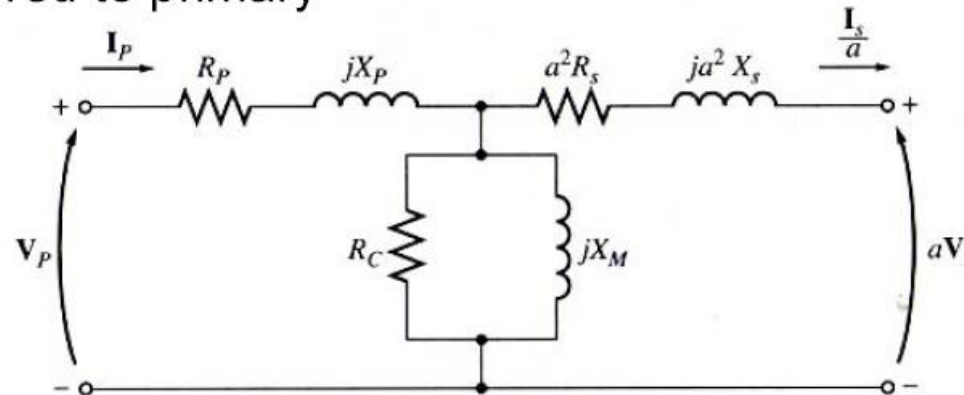

Referred to secondary

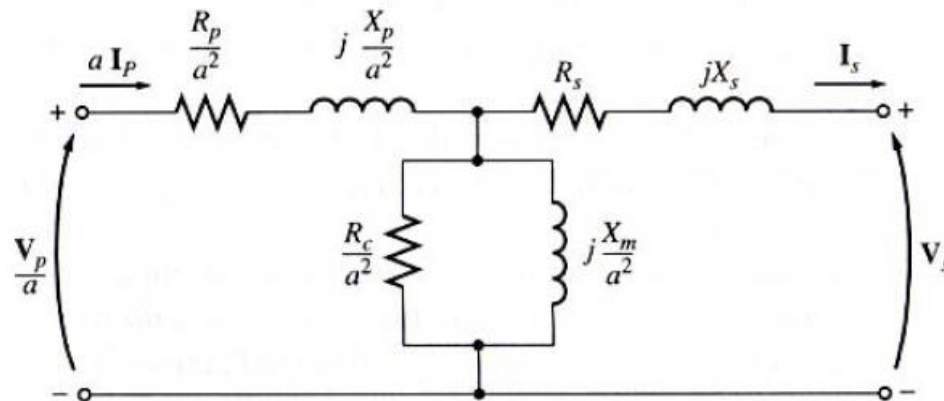


Magnetizing current


Recall the Hysteresis curve B versus H

At a sufficiently high H the core saturates and B is essentially constant.

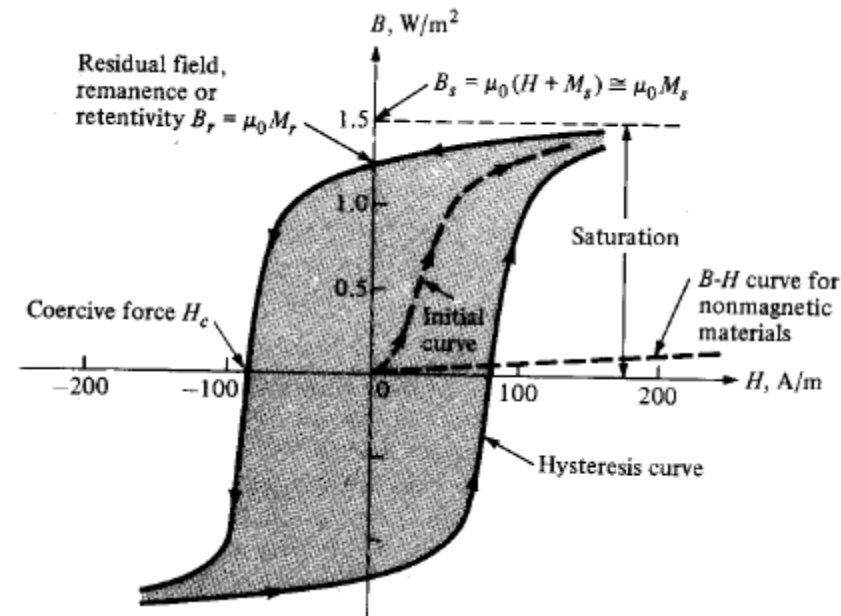The usual design principle is to have $B = B_{sat}$ at the voltage peaks in the primary. (This minimizes the amount of iron needed in the core)





Magnetizing current

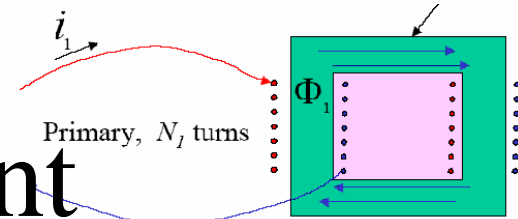

$$v_{1,\max} = - \frac{d\Phi_{1,\max}}{dt}$$


$$v_{1,\text{peak}} = \omega B_{\text{sat}} A$$

$$i_1 = \frac{H l_{\text{core}}}{N_1}$$

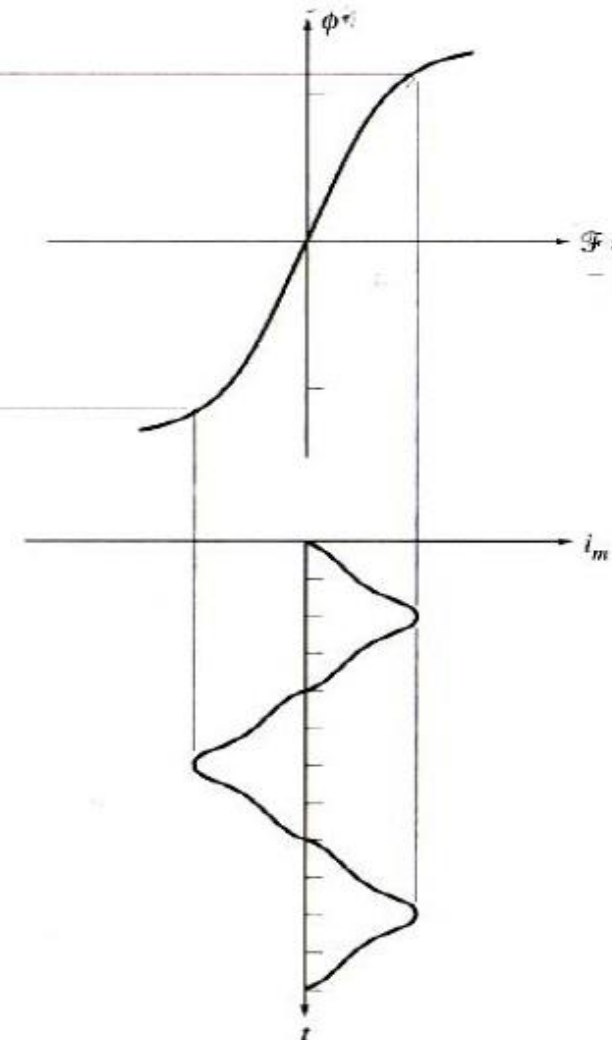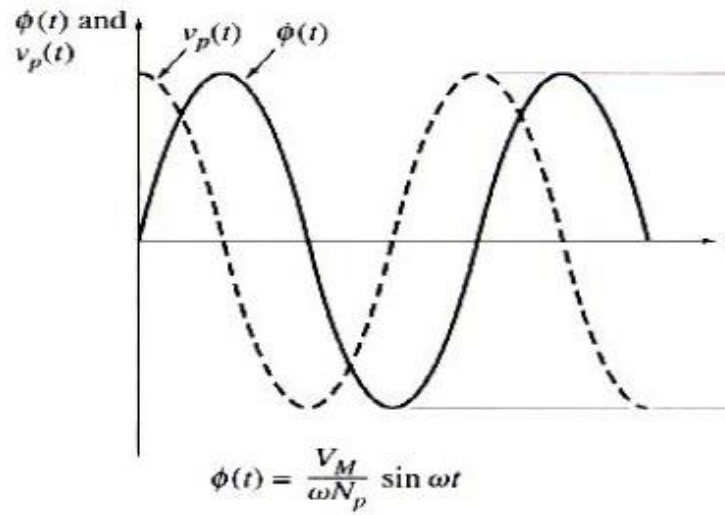


If v_1 goes beyond this range, however, H is above H_{sat} , and the effective inductance seen at the primary becomes small. The flux is also not well-confined to the core. Because of the reduced inductance, the current in the primary becomes large in these peak parts of the cycle.

Magnetizing current

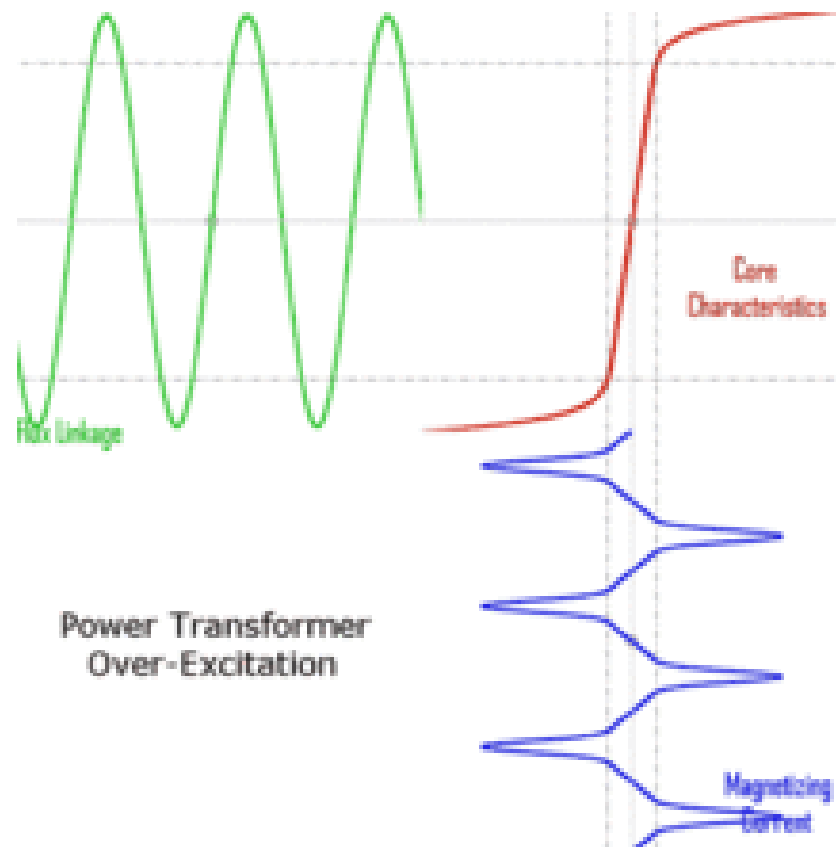



Excitation current

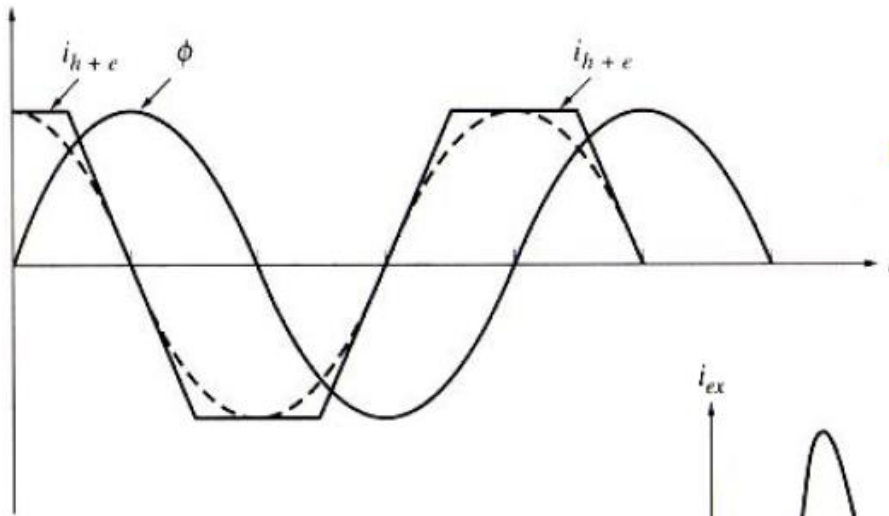

■ Core-loss current





Total excitation current

$$i_{ex} = i_m + i_{h+e}$$

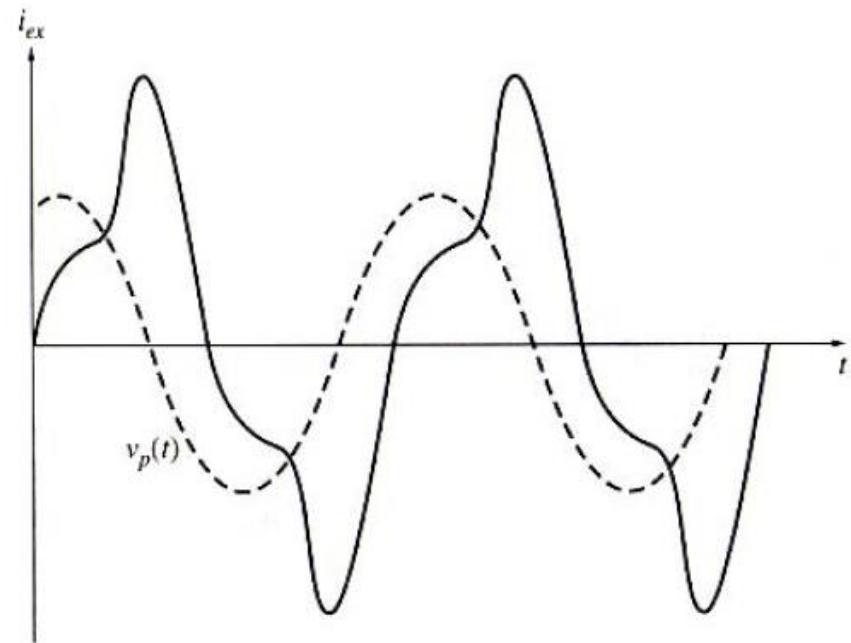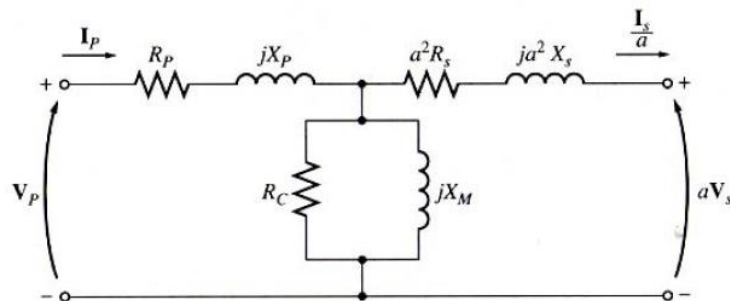

Transformer Modeling


Approximate equivalent circuits

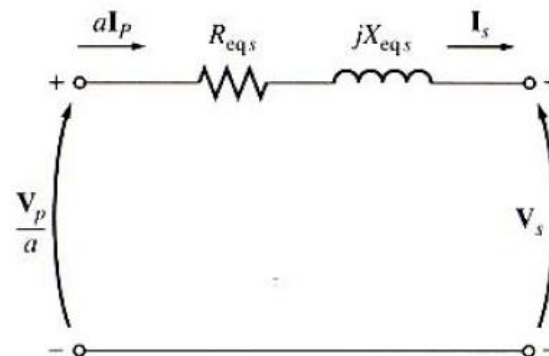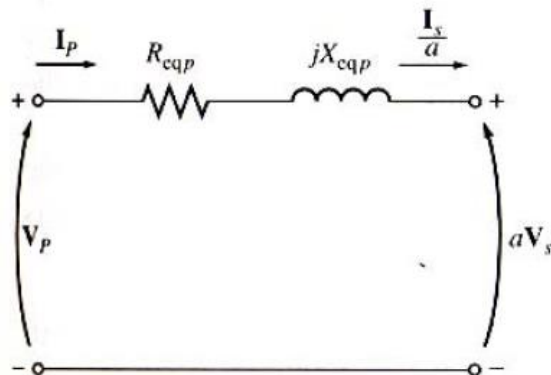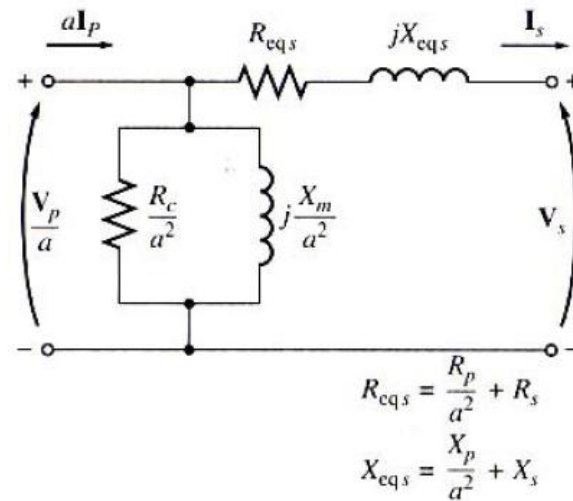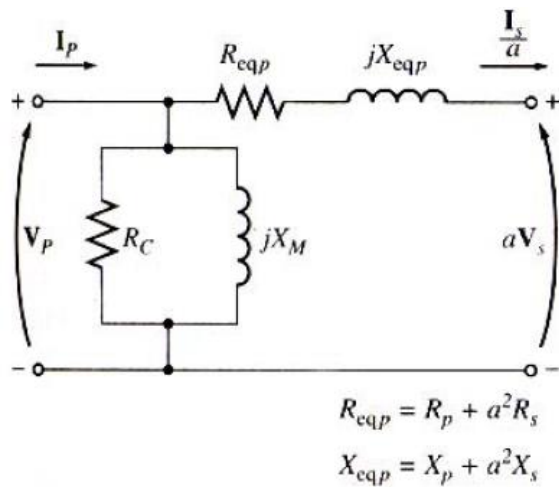

Determination of Equivalent Circuit

1-D.C. test

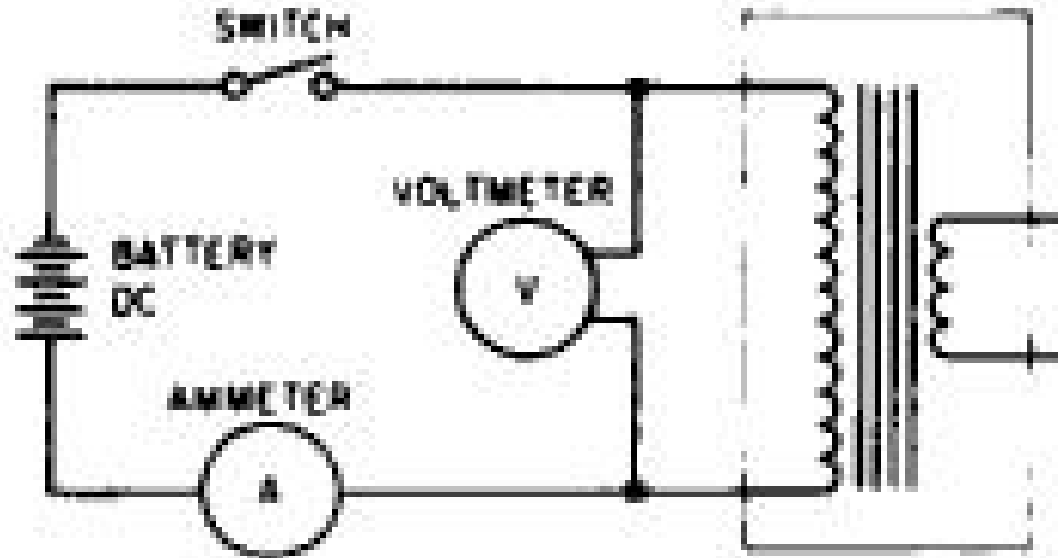
- This test is carried out to measure the resistance of each winding
- The resistance of each winding is obtained from the Ohms Law $R = E/I$



Determination of Equivalent Circuit

2- Open Circuit Test

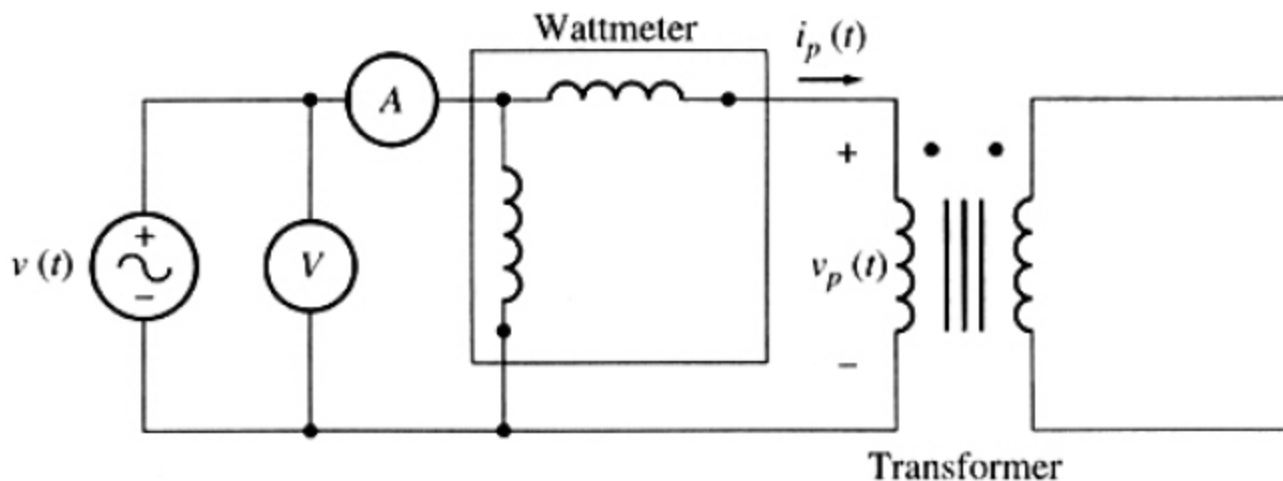- The secondary winding is left open
- The primary winding is connected to a full-rated voltage
- Measure V , I , P
- Want to find R_C and X_M



Determination of Equivalent Circuit

2- Open Circuit Test

- Conductance of the core-loss resistor

$$G_C = 1 / R_C$$

- Susceptance of the magnetizing inductor


$$B_M = 1 / X_M$$

- Total admittance

$$Y_E = G_C - jB_M = \frac{1}{R_C} - j \frac{1}{X_M}$$

- The admittance magnitude

$$|Y_E| = \frac{I_{OC}}{V_{OC}}$$

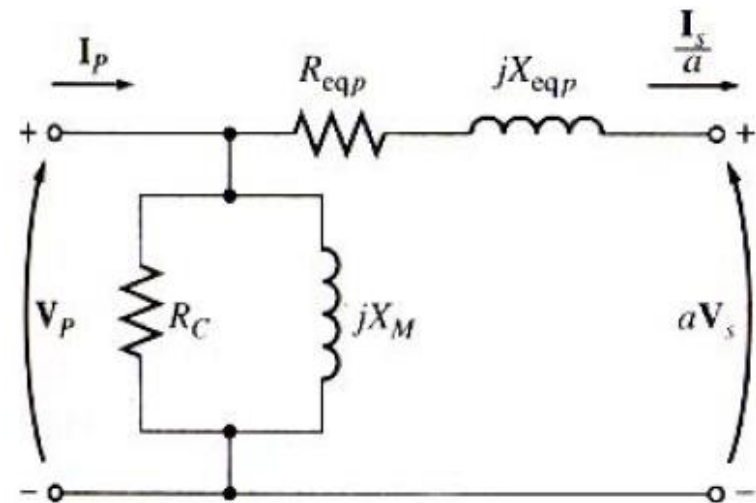

$$R_{eqp} = R_p + a^2 R_s$$

$$X_{eqp} = X_p + a^2 X_s$$

Determination of Equivalent Circuit

2- Open Circuit Test

- The angle

- First we find power factor $PF = \cos \theta = \frac{P_{oc}}{V_{oc} I_{oc}}$
- Then the power-factor angle is given by

$$\theta = \cos^{-1} \left(\frac{P_{oc}}{V_{oc} I_{oc}} \right)$$

- In a real transformer, the PF is always lagging


$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta = \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1} PF$$

- The values of R_C and X_M can be determined

Determination of Equivalent Circuit

3- Short Circuit Test

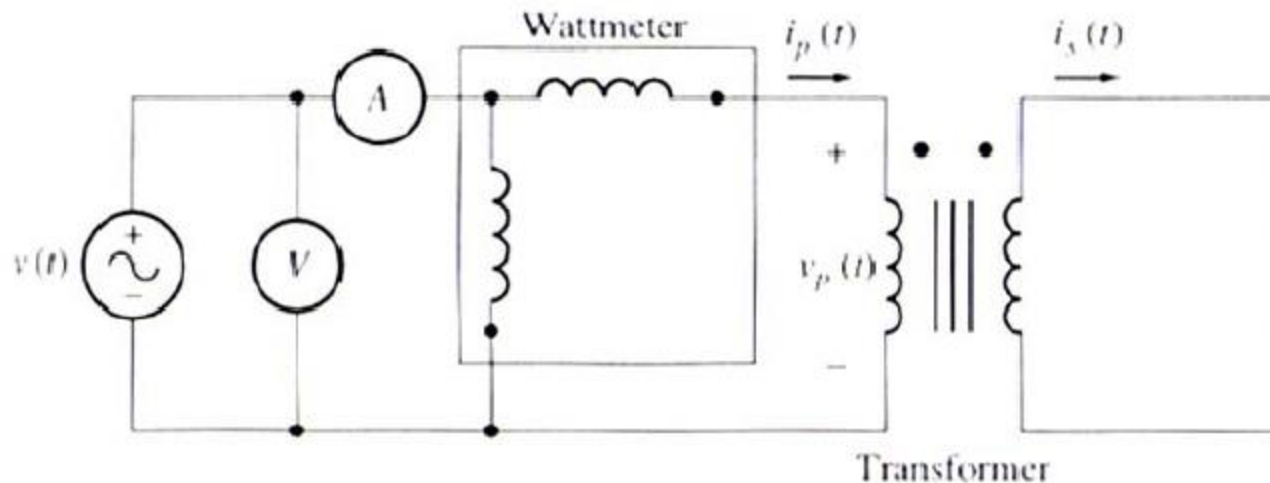- The secondary terminals are shorted
- The input voltage is adjusted until the current is equal to its rated value
- Measure V, I, P
- Want to find R_{eq} and X_{eq}



Determination of Equivalent Circuit

3- Short Circuit Test

- Series impedance referred to primary

$$|Z_{SE}| = \frac{V_{SC}}{I_{SC}}$$

- Power factor


$$PF = \cos\theta = \frac{P_{SC}}{V_{SC}I_{SC}}$$

- The impedance angle

$$Z_{SE} = \frac{V_{SC} \angle 0^\circ}{I_{SC} \angle -\theta^\circ} = \frac{V_{SC}}{I_{SC}} \angle \theta^\circ$$





- and

$$Z_{SE} = R_{eq} + jX_{eq}$$

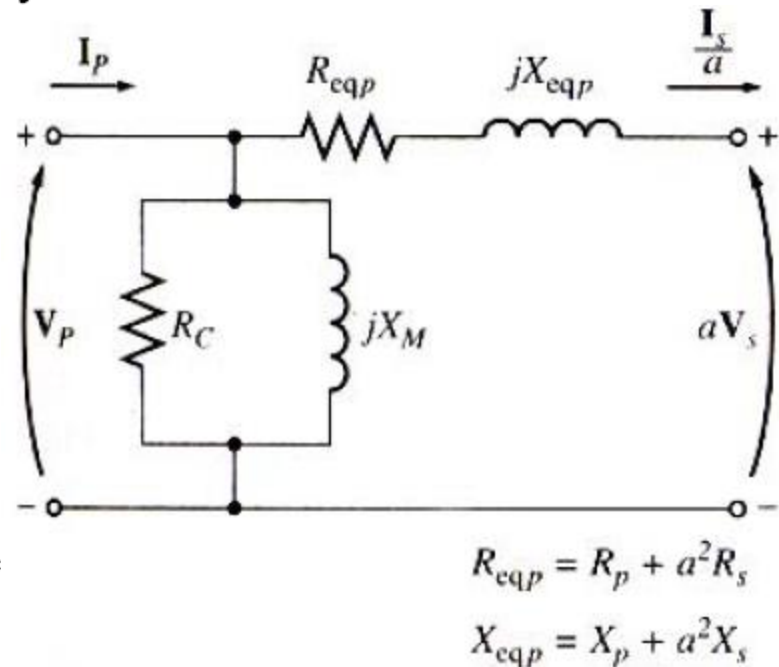

Determination of Equivalent Circuit

Approximate equivalent circuits

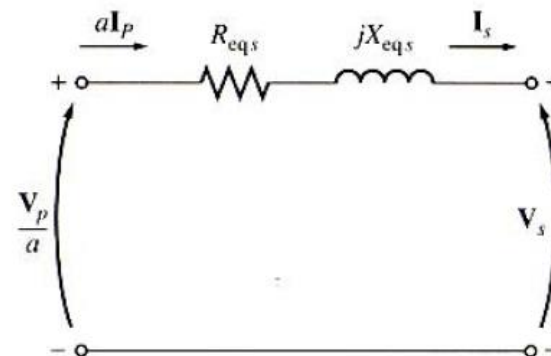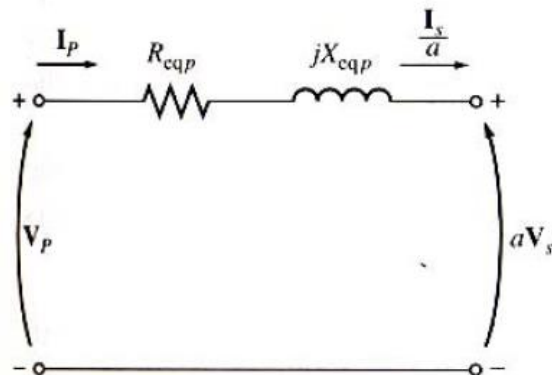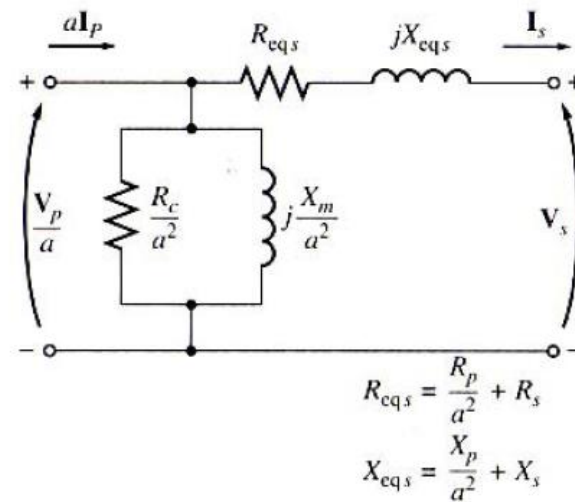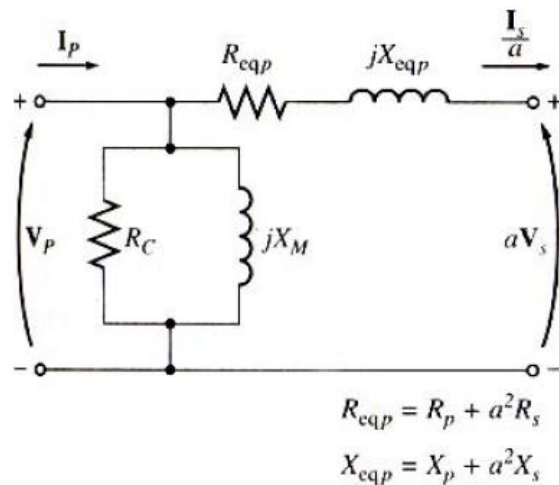

Determination of Equivalent Circuit

Example

- A 20 kVA, 8000/240 V, 60 Hz transformer has been tested with the following data

Open-circuit test (on primary)	Short-circuit test (on primary)
$V_{oc} = 8000 \text{ V}$	$V_{sc} = 489 \text{ V}$
$I_{oc} = 0.214 \text{ A}$	$I_{sc} = 2.5 \text{ A}$
$P_{oc} = 400 \text{ W}$	$P_{sc} = 240 \text{ W}$

- Find the equivalent circuit referred to the primary side

Determination of Equivalent Circuit

Example

■ Open-circuit test

□ Power factor

$$PF = \cos \theta = \frac{P_{oc}}{V_{oc} I_{oc}} = \frac{400\text{W}}{(8000\text{V})(0.214\text{A})} = 0.234 \text{ lagging}$$

□ Excitation admittance

$$\begin{aligned} Y_E &= \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1} PF = \frac{0.214}{8000} \angle -\cos^{-1} 0.234 \\ &= 0.0000063 - j0.0000261 = \frac{1}{R_C} - j \frac{1}{X_M} \end{aligned}$$

□ Therefore

$$R_C = 159 \text{ k}\Omega$$

$$X_M = 38.4 \text{ k}\Omega$$

Determination of Equivalent Circuit

Example

- Short-circuit test

- Power factor

$$PF = \cos\theta = \frac{P_{sc}}{V_{sc}I_{sc}} = \frac{240W}{(489V)(2.5A)} = 0.196 \text{ lagging}$$

- Series impedance

$$\begin{aligned} Z_{SE} &= \frac{V_{sc}}{I_{sc}} \angle \cos^{-1} PF = \frac{489}{2.5} \angle 78.7 \\ &= 38.4 + j192 \end{aligned}$$

- Therefore

$$R_{eq} = 38.4 \, \Omega$$

$$X_{eq} = 192 \, \Omega$$

Determination of Equivalent Circuit

Example

- The equivalent circuit

