


به نام خدا

پیش گزارش آزمایش ۴

بردیا برائی نژاد (۹۲۱۰۱۶۶۹)

۱.


```
module com(a,b,c,aBTb,bBTa,aETb);
    //a , b are 4bit numbers and c is cascade
    //aBTb means a>b,bBTa means b>a,aETb means a=b
    input [3:0] a,b;
    input [2:0] c;
    output aBTb, bBTa, aETb;
    wire [3:0] w1;
    wire [2:0] w2;
    wire w3;
    assign w1[0] = a[0] ^ b[0],
    w1[1] = a[1] ^ b[1],
    w1[2] = a[2] ^ b[2],
    w1[3] = a[3] ^ b[3],
    w3 = w1[0] & w1[1] & w1[2] & w1[3],
    w2[0] = w3 & c[0],
    w2[1] = w3 & c[1],
    w2[2] = w3 & c[2];
    assign aETb = w2[0],
    aBTb = (a[3] & ~b[3]) | (w1[3] & a[2] & ~b[2]) | (w1[3] & w1[2] & a[1] & ~b[1]) | (w1[3] & w1[2] & w1[1] & a[0] & ~b[0]) | w2[1],
    bBTa = w2[2] | ~(aETb|aBTb);
endmodule
```

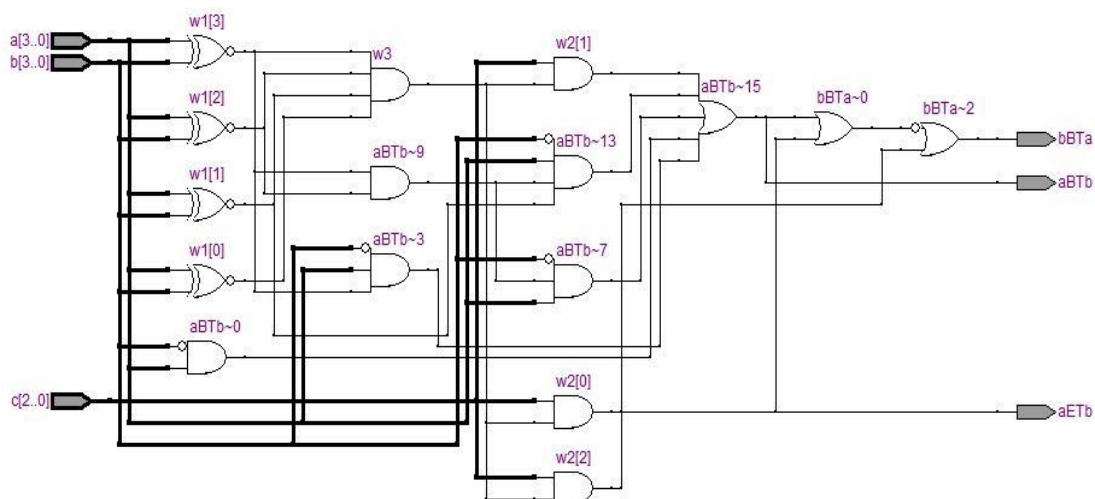


```

module com(a,b,c,aBTb,bBTa,aETb);
    //a , b are 4bit numbers and c is cascade
    //aBTb means a>b,bBTa means b>a,aETb means a=b
    input [3:0] a,b;
    input [2:0] c;
    output reg aBTb, bBTa, aETb;
    always @(*)
    begin
        if (a>b)
            {aETb, aBTb, bBTa} = 3'b010;
        else if (a<b)
            {aETb, aBTb, bBTa} = 3'b001;
        else if (a==b)
            begin
                case(c)
                    1: {aETb, aBTb, bBTa} = 4;
                    2: {aETb, aBTb, bBTa} = 2;
                    4: {aETb, aBTb, bBTa} = 1;
                endcase
            end
        end
    end
endmodule

```

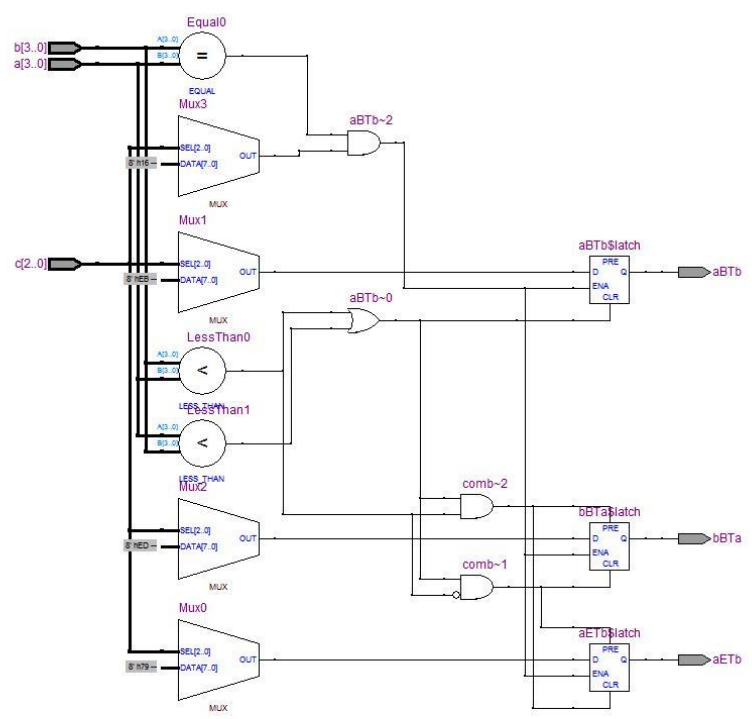


	Name	Value at 80.0 ns	0 ps	10.0 ns	20.0 ns	30.0 ns	40.0 ns	50.0 ns	60.0 ns	70.0 ns
0	a	B 0000	0100		0000		1111			0000
5	b	B 0000	0101		0000		0111			0000
10	c	B 000	000	001	010		100			000
14	aBTb	A 0								
15	aETb	A 0								
16	bBTa	A 0								

 

```

module com(num,a,b,c,d,e,f,g);
    //num is the input number
    //a,...,g are names of 7seg LED's
    input [3:0] num;
    output reg a,b,c,d,e,f,g;
    always @(*)
    begin
        case(num)
            0: {a,b,c,d,e,f,g} = 7'b1111110; //g is off
            1: {a,b,c,d,e,f,g} = 7'b0110000; //b,c are on
            2: {a,b,c,d,e,f,g} = 7'b1101101; //c,f are off
            3: {a,b,c,d,e,f,g} = 7'b1111001; //f,e are off
            4: {a,b,c,d,e,f,g} = 7'b0110011; //a,d,e are off
            5: {a,b,c,d,e,f,g} = 7'b1011011; //b,e are off
            6: {a,b,c,d,e,f,g} = 7'b1011111; //b is off
            7: {a,b,c,d,e,f,g} = 7'b1110000; //a,b,c are on
            8: {a,b,c,d,e,f,g} = 7'b1111111; //nothing is off
            9: {a,b,c,d,e,f,g} = 7'b1111011; //just e is off
        endcase
    end
endmodule


```

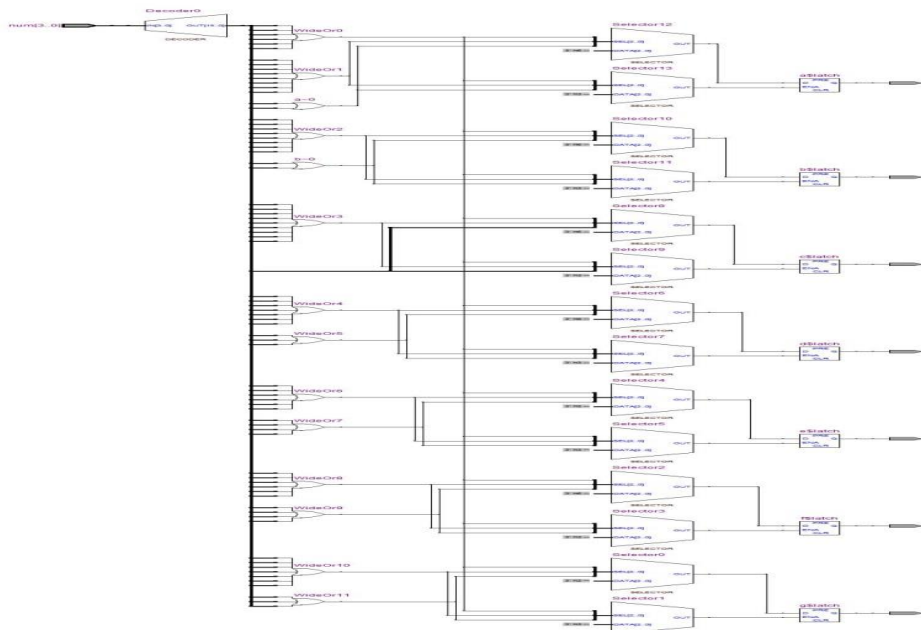

```

module com(a,b,Cin,Cout,s);
    //a,b are numbers
    //Cin is carry in
    //Cout is carry out
    //s is sum
    input [3:0] a,b;
    input Cin;
    output reg [3:0] s;
    output reg Cout;
    reg [4:0] x;
    always @(*)
    begin
        x = a+b+Cin;
        if (x<10)
            {Cout,s}=x;
        else
            {Cout,s}=x+6;
    end
endmodule

```

 

۵. آی سی 74LS85 یک مقایسه گر ۴ بیتی است. ورودی های ۴ بیتی به A و B وارد می شوند. (A3 و B3، MSB هستند). ورودی های Cascading inputs برای استفاده از چند آی سی متوالی هستند تا بتوانیم اعداد بزرگتر از ۴ بیت را مقایسه کنیم. (خروجی های less-significant باید به ورودی های cascade دیگری (more-significant) متصل شوند).

