

# Energy conversion I

## Lecture 18:


### Topic 5: Induction Motors (S. Chapman ch. 7)

- Induction Motor Construction
- Basic Induction Motor Concepts
- The Equivalent Circuit of an Induction Motor.
- Power and Torque in Induction Motor.
- **Induction Motor Torque-Speed Characteristics**
- Starting Induction Motors
- Speed Control of Induction Motor
- Determining Circuit Model Parameters

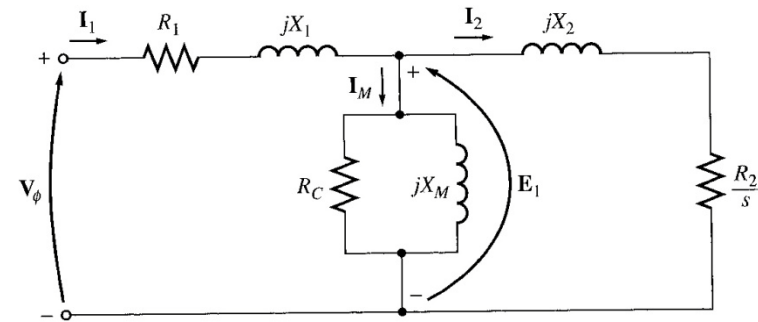
# Thevenin Equivalent Circuit

**Mechanical Torque:**  $T_{\text{ind}} = \frac{P_{\text{conv}}}{\Omega_m} = \frac{P_{\text{AG}}}{\Omega_s}$

**Air-gap Power :**  $P_{\text{AG}} = 3 \frac{R_2}{s} I_2^2$



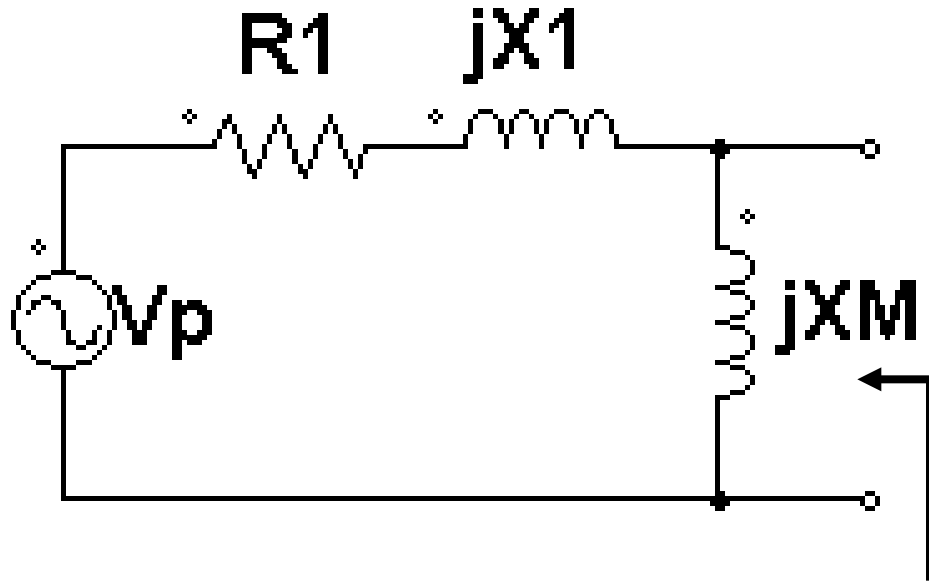$I_2$  can be calculated directly from Stator Thevenin equivalent Circuit:




$$V_{\text{th}} = V_p \frac{jX_M}{R_1 + j(X_1 + X_M)}$$

$$Z_{\text{th}} = R_{\text{th}} + jX_{\text{th}} = jX_M \parallel (R_1 + jX_1)$$

$$Z_{\text{th}} = \frac{jX_M (R_1 + jX_1)}{R_1 + j(X_1 + X_M)}$$
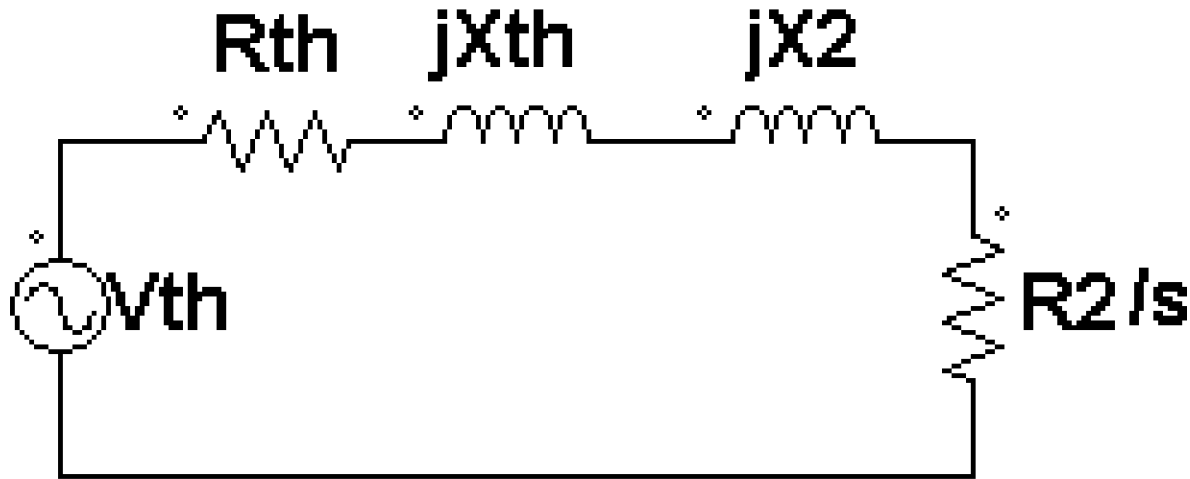
# Torque calculation using Thevenin equivalent circuit



$$\frac{V_{th}}{R_{th} + \frac{R_2}{s} + j(X_2 + X_{th})}$$

**Air-gap Power :**  $P_{AG} = 3 \frac{R_2}{s} \frac{V_{th}^2}{(R_{th} + \frac{R_2}{s})^2 + (X_2 + X_{th})^2}$

**Mechanical Torque:**  $T_{ind} = \frac{3}{2} \frac{p}{\omega_s} \frac{R_2}{s} \frac{V_{th}^2}{(R_{th} + \frac{R_2}{s})^2 + (X_2 + X_{th})^2}$

# Torque Speed Characteristic

Torque-slip for a given voltage and frequency :


$$T_{ind} = \frac{3}{2} \frac{p}{\omega_s} \frac{R_2}{s} \frac{V_{th}^2}{(R_{th} + \frac{R_2}{s})^2 + (X_2 + X_{th})^2}$$

$$s = \frac{n_s - n}{n_s}$$

For very small s( 0-more than rated)


$$T_{ind} \approx \frac{3}{2} \frac{p}{\omega_s} V_{th}^2 \frac{s}{R_2}$$

Linear torque-slip (/speed)

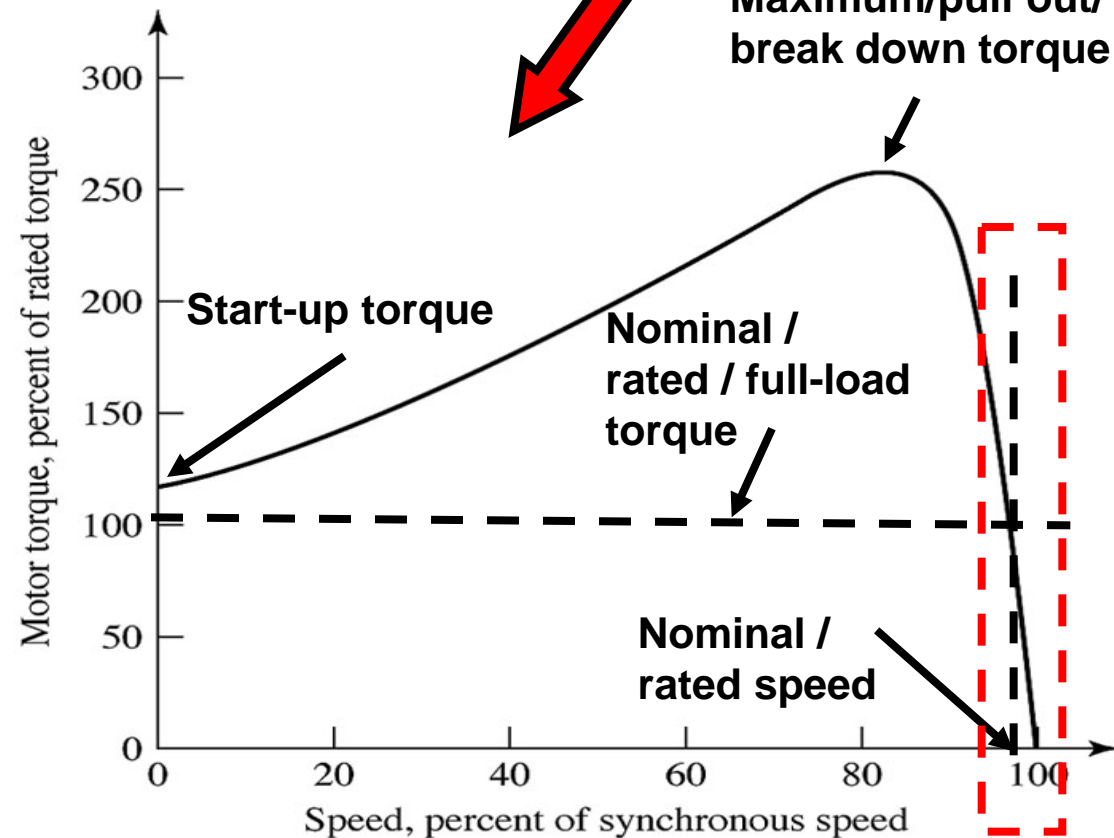
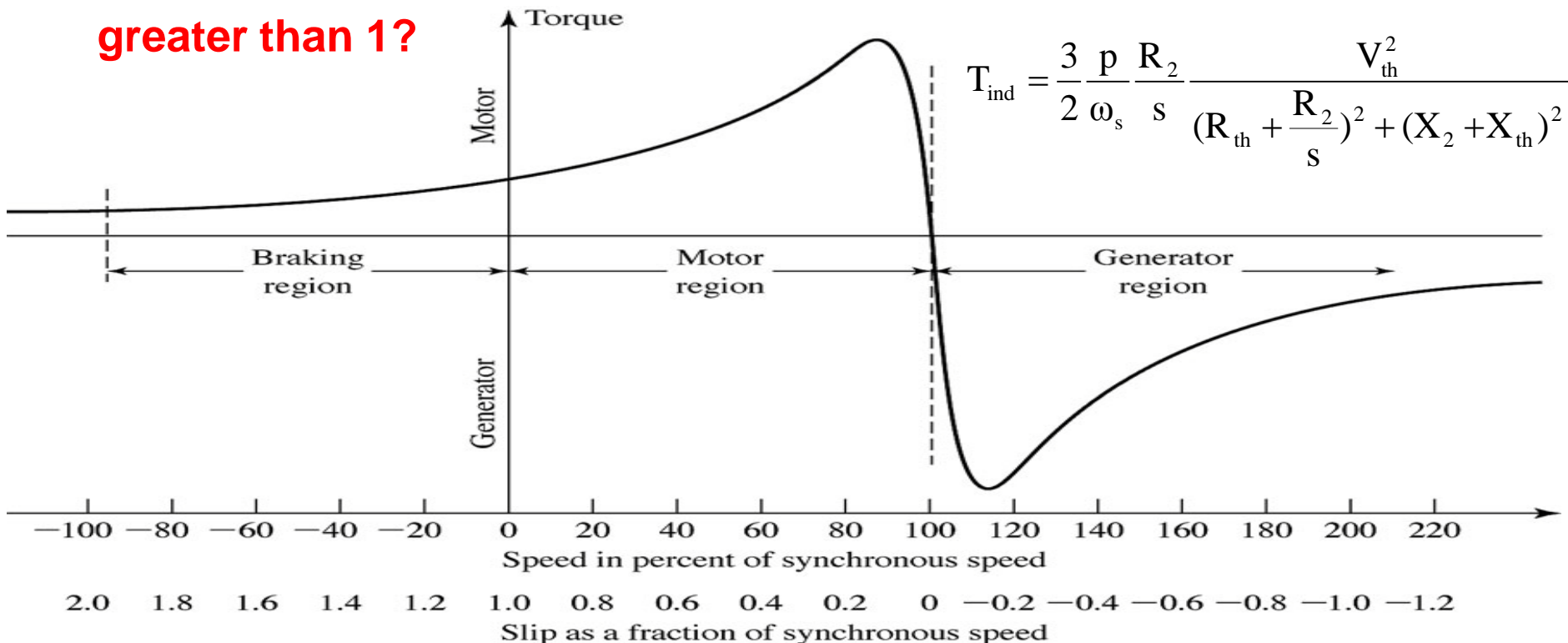
# Some comments on torque speed Characteristics

- Start-up torque ( $s=1$ ) is usually greater than rated torque
- Rated speed and no-load speed are very close to synchronous speed
- Pull-out torque is usually more than twice rated torque
- For  $s < 0$  torque is negative (generator mode). **what is the speed of rotation?**
- For  $s > 1$  torque is positive (Braking/ rotor plugging). **How can  $s$  be greater than 1?**



## Example:

A 2 pole, 50 Hz induction motor supplies 15kW to a load at a speed of 2950 r/min.

- A. What is the motor's slip?
- B. What is the induced torque in the motor under these conditions?
- C. What will the operating speed of the motor be if its torque is doubled?
- D. How much power will be supplied by the motor when the torque is doubled?

## Solution:

A.

$$n_{\text{sync}} = \frac{120f_e}{p} = \frac{120 \times 50}{2} = 3000 \text{ rpm}$$
$$s = \frac{n_{\text{sync}} - n}{n_{\text{sync}}} = \frac{3000 - 2950}{3000} = 0.0167$$

**B. What is the induced torque in the motor in Nm under these conditions?**

**Assuming  $P_{\text{conv}} = P_{\text{load}}$**

$$T_{\text{ind}} = \frac{P_{\text{conv}}}{\omega} = \frac{15 \times 10^3}{2950/60 \times 2\pi} = 48.6 \text{ N.m}$$

**C. What will the operating speed of the motor be if its torque is doubled?**

**Assuming a linear torque-slip relation close to rated torque**

$$s_2 = 2 \times s_1 = 0.033 \quad n_2 = (1 - s_2) \times n_{\text{sync}} = (1 - 0.033) \times 3000 = 2900 \text{ rpm}$$

**D. How much power will be supplied by the motor when the torque is doubled?**

$$P_{\text{conv}} = T_{\text{ind}} \omega_m = 2 \times 48.6 \times 2900/60 \times 2\pi = 29.5 \text{ kW} !!$$

# Pull-out Torque


Pull-out torque is the maximum torque:

$$\frac{\partial T_{\text{ind}}}{\partial s} = 0 \Rightarrow s_{T_{\text{max}}} \Rightarrow T_{\text{max}}$$

Looking air-gap power:  $T_{\text{ind}} = \frac{P_{\text{AG}}}{\Omega_s}$  maximum torque happens if air-gap power is maximum

Maximum power transfer theorem
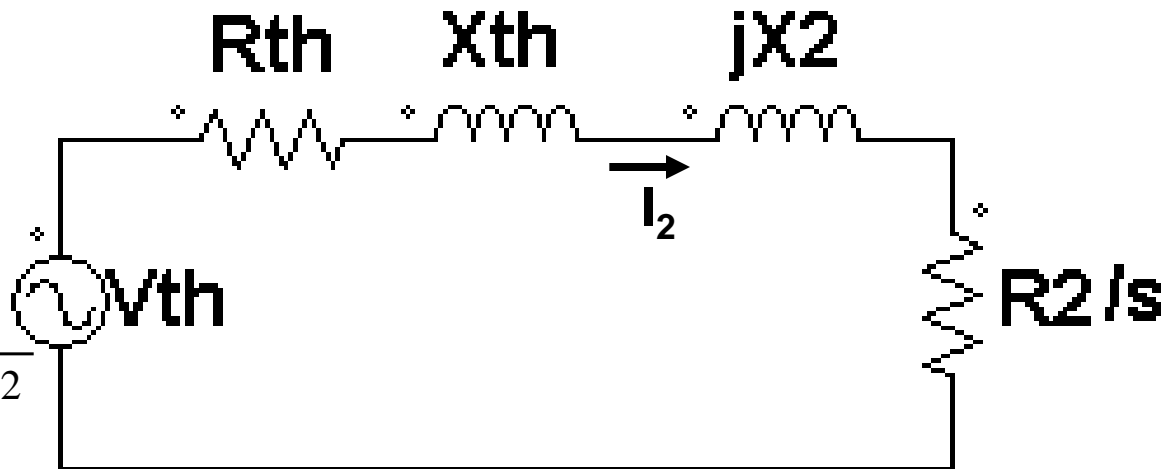
$$\frac{R_2}{s_{T_{\text{max}}}} = \sqrt{R_{\text{th}}^2 + (X_{\text{th}} + X_2)^2}$$



$$T_{\text{max}} = \frac{3}{4} \frac{p}{\omega_s} \frac{V_{\text{th}}^2}{R_{\text{th}} + \sqrt{R_{\text{th}}^2 + (X_{\text{th}} + X_2)^2}}$$

How  $R_2$  affects  $s_{T_{\text{max}}}$  and  $T_{\text{max}}$ ?




# Rotor Resistance Effects

$$\frac{R_2}{S_{T_{\max}}} = \sqrt{R_{th}^2 + (X_{th} + X_2)^2} \quad T_{\max} = \frac{3}{4} \frac{p}{\omega_s} \frac{V_{th}^2}{R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2)^2}}$$

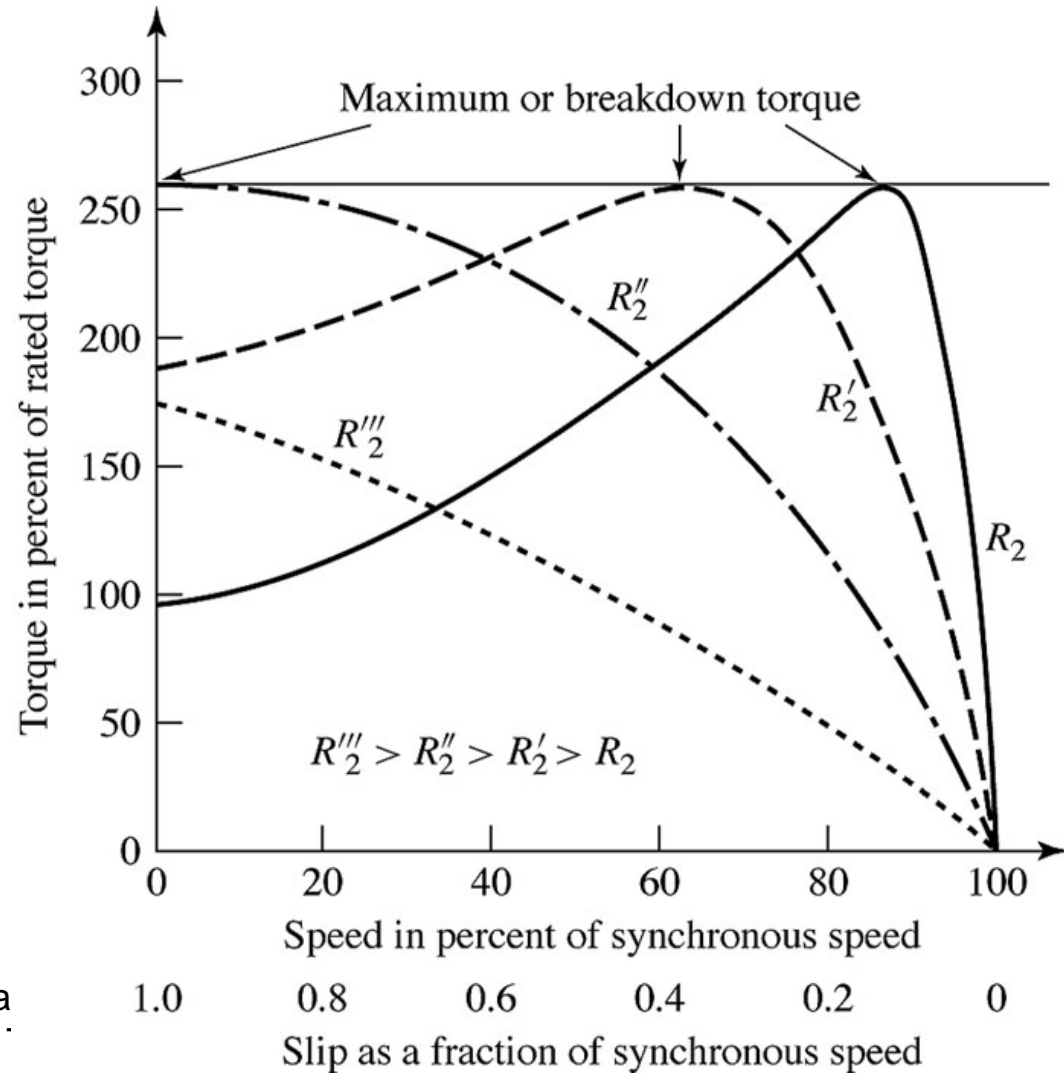**Increasing  $R_2$ ,**

- **Increases  $S_{T_{\max}}$**
- **Increases  $Z_{in}$**
- **Decreases start-up current !**
- **No effect on  $T_{\max}$**

**Can be implemented using  
external resistors in wound  
rotor motors**



## Example:

**A 460V, 25hp, 60Hz, 4-pole, Y-connected wound rotor induction motor has the following impedances in ohms per-phase referred to the stator circuit:**

$$R_1 = 0.641 \, \Omega$$

$$R_2 = 0.332 \, \Omega$$

$$X_1 = 1.106 \, \Omega$$

$$X_2 = 0.464 \, \Omega$$

$$X_m = 26.3 \, \Omega$$

- A. What is the maximum torque of this motor? At what speed and slip does it occur?**
- B. What is the starting torque?**
- C. When the rotor resistance is doubled, what is the speed at which the max torque now occurs? What is the new starting torque?**

$$V_{th} = V_p \frac{jX_M}{R_1 + j(X_1 + X_M)} = \frac{460}{\sqrt{3}} \frac{j26.3}{0.641 + j(26.3 + 1.106)} = 255.2 \angle \alpha$$

$$Z_{th} = \frac{jX_M(R_1 + jX_1)}{R_1 + j(X_1 + X_M)} = \frac{j26.3(0.641 + j1.106)}{0.641 + j(26.3 + 1.106)} = 0.59 + j1.10$$

**A. What is the max torque of this motor? At what speed and slip does it occur?**

$$T_{\max} = \frac{3}{4} \frac{p}{\omega_s} \frac{V_{th}^2}{R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2)^2}}$$

$$= \frac{3}{4} \frac{4}{120\pi} \frac{255.2^2}{0.59 + \sqrt{0.59^2 + (1.1 + 0.464)^2}} = 229 \text{ N.m}$$

$$s_{T_{\max}} = \frac{R_2}{\sqrt{R_{th}^2 + (X_{th} + X_2)^2}} = \frac{0.332}{\sqrt{0.59^2 + (1.1 + 0.464)^2}} = 0.198$$

$$n_{T_{\max}} = (1 - s_{T_{\max}}) n_{\text{sync}} = (1 - 0.198) \times 1800 = 1444 \text{ rpm}$$

**B. What is the starting torque? (s=1)**

$$T_{\text{ind}} = \frac{3}{2} \frac{p}{\omega_s} \frac{R_2}{s} \frac{V_{th}^2}{(R_{th} + \frac{R_2}{s})^2 + (X_R + X_{th})^2} = 104 \text{ N.m}$$

**C. When the rotor resistance is doubled, what is the speed at which the max torque now occurs? What is the new starting torque?**

**$s_{T_{\max}}$  is proportional to  $R_2$                        $s_{2,T_{\max}} = 0.396$**

$$\mathbf{N_{2,T_{\max}} = (1 - s_{2,T_{\max}}) \times 1800 = 1087 \text{ rpm}}$$

**For the starting torque:**

$$\mathbf{s = 1, R_2 = 2 \times 0.332 = 0.662 \, \Omega}$$

$$\mathbf{T_{ind} = \frac{3}{2} \frac{p}{\omega_s} \frac{R_2}{s} \frac{V_{th}^2}{(R_{th} + \frac{R_2}{s})^2 + (X_R + X_{th})^2} = 170 \text{ N.m}}$$

**How can maximum torque happen in start-up?**

**Compare start up currents!**