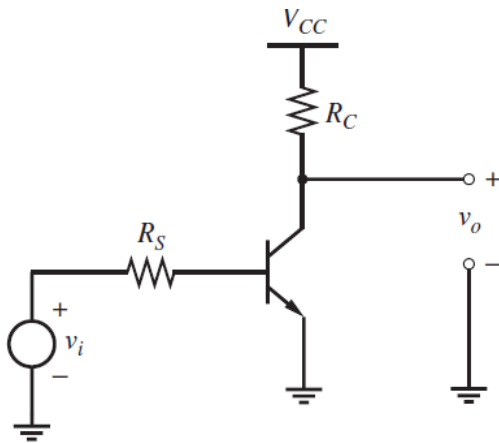


HOMework #4

Principles of Electronics- Winter 2015

Problem 1

- For CE transistor shown below, find the overall small signal gain (V_O/V_i) as a function of R_S , R_C and β , V_A , and I_C .
- Next, determine the value of DC collector current I_C that maximizes the small signal voltage gain.
- Explain qualitatively why the gain falls at very high and very low collector currents.
- What is the voltage gain at optimum I_C ? [Gray 3.2]




Problem 2

In Problem 1, assume $R_S=R_C= 50\text{ k}\Omega$, and calculate I_C . What is the DC voltage drop across R_C ? What is the voltage gain?

Problem 3

In the following circuits, assume $V_{CC}=3V$, $\beta=100$ and $I_S=10^{-15}A$. Calculate the bias current and bias voltage (I_C and V_{CE}).

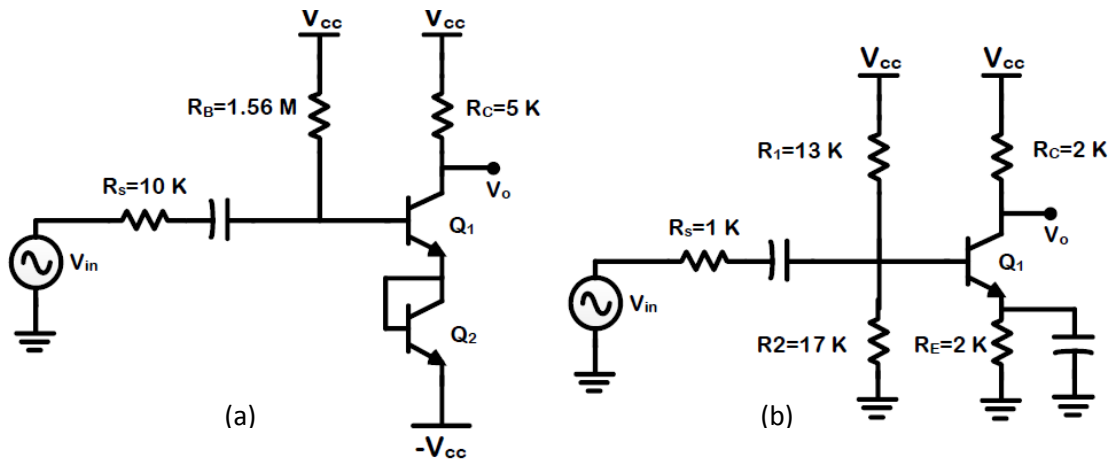

Problem 4

For the circuits in Problem 3, assuming capacitors are large,

- Draw the small signal (AC) equivalent circuit
- Calculate voltage gain $A_v = V_o/V_{in}$
- Calculate input resistance from source and from base
- Output resistance for $V_A = 50\text{ V}$