

# Logic Circuits

## The Problem Collection For Mid-term Exam

This collection consists of 20 questions and their answers which seem to cover all the topics the students may need to know for mid-term exam...

3/1/2011

Sharif University Of Technology  
Mahmoud Momtazpour

## A) Base Conversion, Binary Arithmetic Operations, Binary Codes :

1) Determine the value of x if  $(211)_x = (152)_8$ .

$$2x^2 + x + 1 = 8^2 + 5 \times 8 + 2 \rightarrow 2x^2 + x - 105 = 0 \rightarrow x = 7$$

2) In Gray Code system if we attribute the 0 code to the 0 value then what is the code which shows the value of 6?

Gray      Decimal

|     |   |
|-----|---|
| 000 | 0 |
| 001 | 1 |
| 011 | 2 |
| 010 | 3 |
| 110 | 4 |
| 111 | 5 |
| 101 | 6 |
| 100 | 7 |

→ ..... (101 → 6)

3) In the floating point system of showing the numbers what is the ratio of the biggest number to the very close number after that?

The biggest number is :  $(\text{FFFFFFFF})_{16} = (0.111...1) \times 2^{64} = a$

The next number is :  $(\text{FFFFFFFFE})_{16} = (0.111...10) \times 2^{64} = b$

$$a/b = (2^{64} - 2^{32}) / (2^{64} - 2^{33})$$

## B) Error Detection and Correction Using Parity, Hamming1, Hamming2:

4) In an odd parity system we have received the Hexadecimal number  $(6E)_{16}$ . Is there any error in the received number? If yes, in which digit? Correct the number.

$$(6E)_{16} = 1101110 \rightarrow S_0 = \text{odd parity}\{P_1, X_3, X_5, X_7\} = \{1, 0, 1, 0\} = 1$$

$$S_1 = \text{odd parity}\{P_2, X_3, X_6, X_7\} = \{1, 0, 1, 0\} = 1$$

$$S_2 = \text{odd parity}\{P_4, X_5, X_6, X_7\} = \{1, 1, 1, 0\} = 0$$

$(S_2 S_1 S_0)_2 = (011)_2 = 3 \rightarrow$  It is clear that there is an error in the 3rd bit so :

$$X_3 = 1 \rightarrow \text{The original correct number is : } (X_3 X_5 X_6 X_7)_2 = (1110)_2$$

5) Suppose that in a code the distance between the two closest codes is  $d$ , the numbers of error detection is  $s$  and the numbers of error correction is  $t$ , find the relationship between these parameters for any code depending on the number of digits which differ from a code to the nearest code. (neglect the probability of receiving two errors)

It can be seen from examination that a single error detection code ( $s=1, t=0$ ) requires a minimum distance of  $d_{\min}=2$ , a single error correction code ( $s=0, t=1$ ) requires a minimum distance of  $d_{\min}=3$  and a code with both single error correction and a double error detection ( $s=t=1$ ) requires  $d_{\min}=4$ . so by examination we can receive an empirical relationship like :

$$2t + s + 1 \leq d_{\min}$$

### **C) Boolean Function, Minimization Using both Karnaugh Map and QM Tables, Glitch-Free Design, Logic Circuits Timings, Logic Design of Several Interesting Problems :**

6) Simplify the following boolean expressions to the minimum number of literals :

a)  $ABC + \bar{A}B + AB\bar{C}$

b)  $xy + x(\bar{y}z + \bar{y}\bar{z})$

a)  $= AB(C + \bar{C}) + \bar{A}B = (A + \bar{A})B = B$

b)  $= xy + x(\bar{y}(z + \bar{z})) = xy + x\bar{y} = x(y + \bar{y}) = x$

7) For the Boolean function  $F$  given I the truth table, find the following :

a) List the minterms of the function.

b) List the minterms of  $\bar{F}$ .

c) Express F in sum of minterms in algebraic form.

d) Simplify the function to an expression with a minimum number of literals.

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

a)  $F = \sum m(2,3,6,7)$

b)  $\bar{F} = \sum m(0,1,4,5)$

c)  $F = m(2) + m(3) + m(6) + m(7) = \bar{X}Y\bar{Z} + \bar{X}YZ + XY\bar{Z} + XYZ$

d)  $F = \bar{X}Y(Z+\bar{Z}) + XY(Z+\bar{Z}) = \bar{X}Y + XY = Y(\bar{X}+X) = Y$

8) Write the following function in a SOP (sum of product) and simplest form using Karnaugh map :

$$f(A,B,C,D) = \sum m(0,1,3,4,6,7,9,11,15)$$


| CD \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  | 1  | 0  |
| 01      | 1  | 0  | 1  | 1  |
| 11      | 0  | 0  | 1  | 0  |
| 10      | 0  | 1  | 1  | 0  |

$$\rightarrow f = CD + \bar{B}D + \bar{A}B\bar{D} + \bar{A}\bar{C}\bar{D}$$

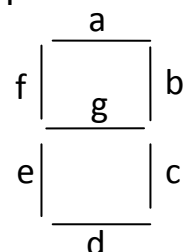9) For the following seven segment find the Boolean

Function for the d LED ( $f_d$ ) as a function of w,x,y,z?

$f_d = \sum m(0,2,3,5,6,8,9) + d(10,11,12,13,14,15)$



| wx \ yz | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 0  | 1  | 1  |
| 01      | 0  | 1  | 0  | 1  |
| 11      |    | X  |    |    |
| 10      | X  |    | X  | X  |
|         | 1  | 1  | X  | X  |


→  $f_d = w + y\bar{z} + \bar{x}y + x\bar{y}z + \bar{w}x\bar{z}$

10) Fabricate the following function with only NOR gates and plot the outcome.(Limitation: there have to be just two inputs)

$$f(A,B,C,D) = \sum m(1,3,4,5,8,11,12,14,15) \quad A=\text{LSB}$$


$$\bar{f} = \sum m(0,2,6,7,9,10,13) \rightarrow \bar{f} = \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C} + B\bar{C}\bar{D} + A\bar{B}D$$
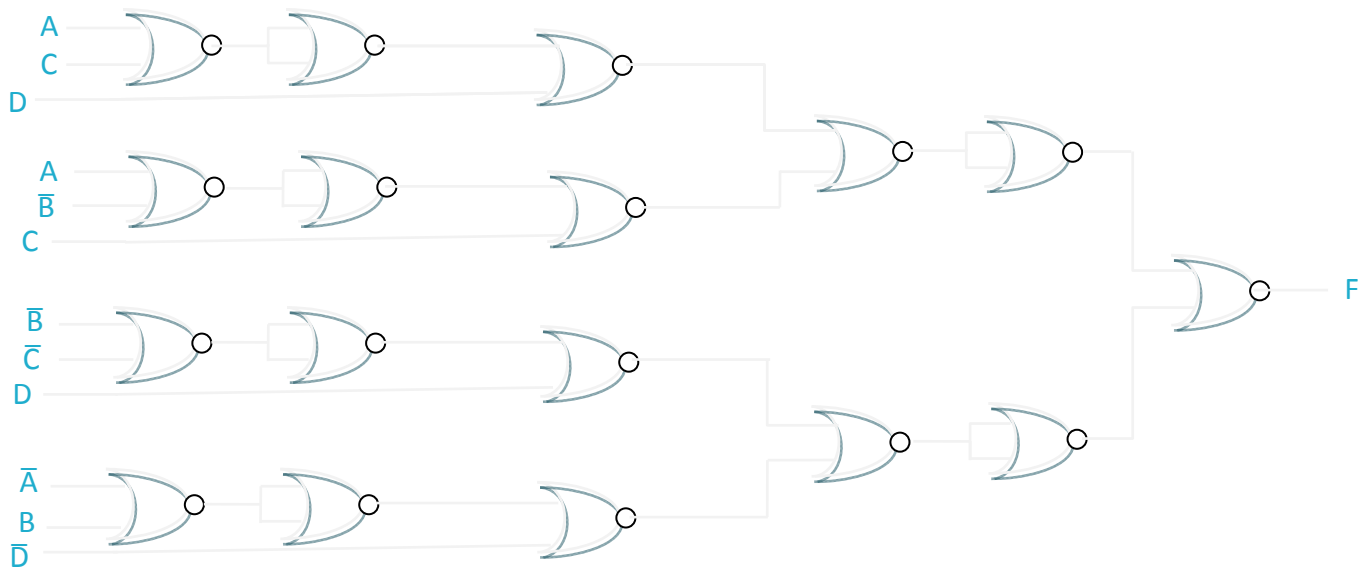
$$f = (A+C+D) \times (A+\bar{B}+C) \times (\bar{B}+\bar{C}+D) \times (\bar{A}+B+\bar{D})$$




## D) Modular combinational circuit design (MUX, ADDER, ENCODER,...) :

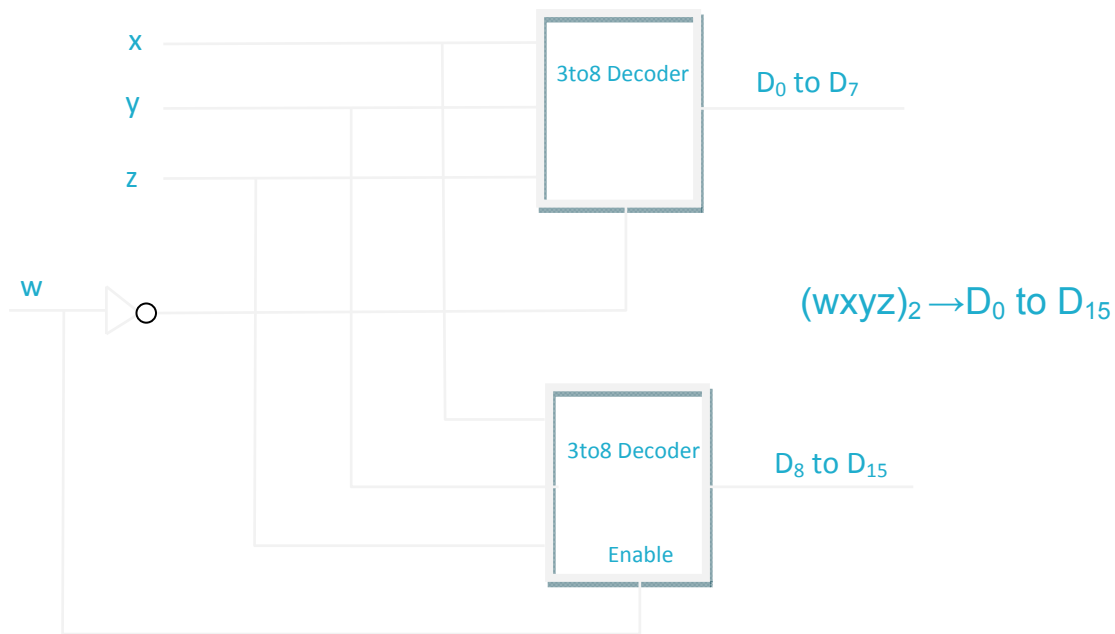11) Design a 4 to 16 Decoder by means of two 3 to 8 Decoder.(note that you can also use the Enable pins)



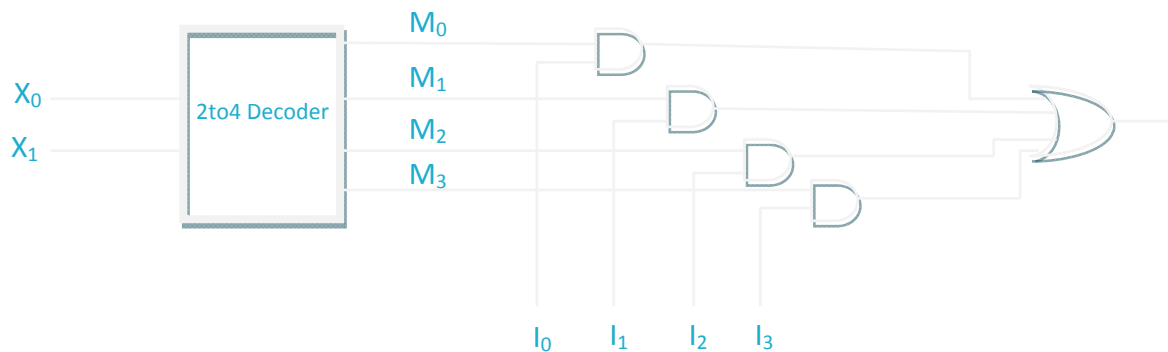12) Design and implant a MultiPlexer(with two selector) Using a 2 to 4 Decoder and minimum gates.




13) Desing a combinational circuit which can find the odd parity for 6 bits (A,B,C,D,E,F) Using just two 4 to 1 MUX and XOR gates.

odd parity :

For example if we have (ABCDEF) 001011 then the output should be 0.

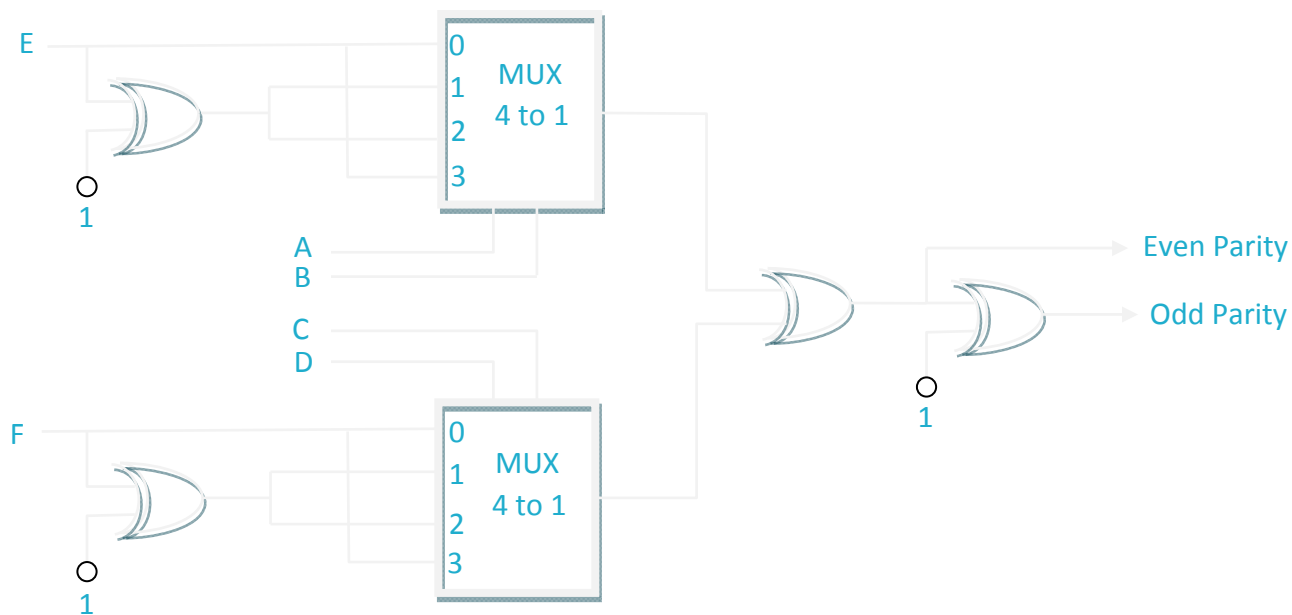Or if 000110 then the output should be 1.



14) Design a comparator (which compares two binary number A and B) by means of a 4 bit Adder and logic gates.

We can use the Adder as a comparator by inverting B's digits and adding A and B which leads to  $A-B$ . From the sign of  $A-B$  we can compare their magnitudes.

